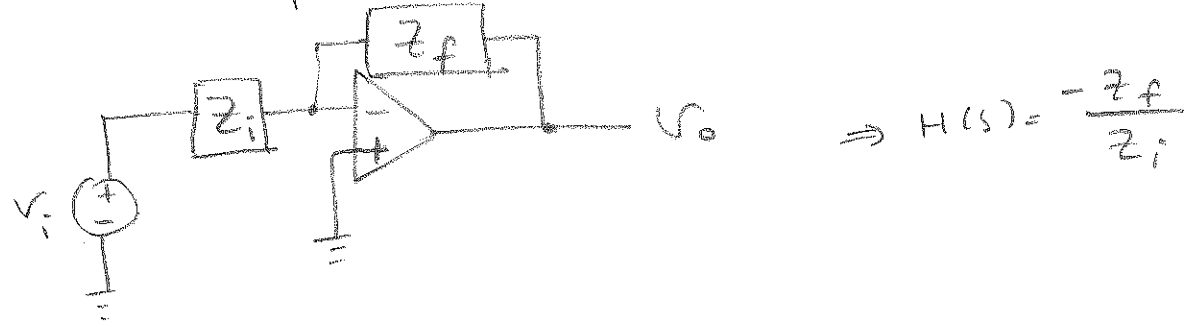



Active Filters:

General op-amp filter circuit is:



Low-Pass Filter:

Consider

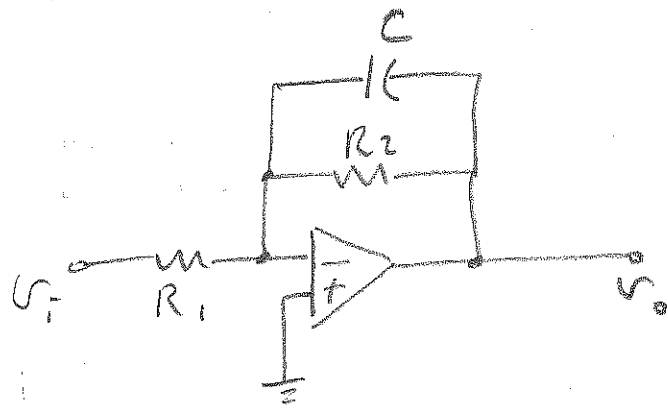

$$H(s) = \frac{-R_2 \parallel (\frac{1}{sC})}{R_1}$$

or $H(s) = -k \frac{\omega_c}{s + \omega_c}$ where $k = \frac{R_2}{R_1}$, $\omega_c = \frac{1}{R_2 C}$

Ex:

Find C and R_2 given that $R_1 = 1\Omega$ to have a LFF with a gain of 1 and cutoff frequency of 1 rad/sec.

Ans:

$$k = \frac{R_2}{R_1} \rightarrow R_2 = k R_1$$


$$R_2 = R_1$$

$$\boxed{R_2 = 1\Omega}$$

$$\omega_c = \frac{1}{R_2 C} \rightarrow C = \frac{1}{R_2 \omega_c}$$

$$\text{or } \boxed{C = \frac{1}{1 \cdot 1} = 1F}$$

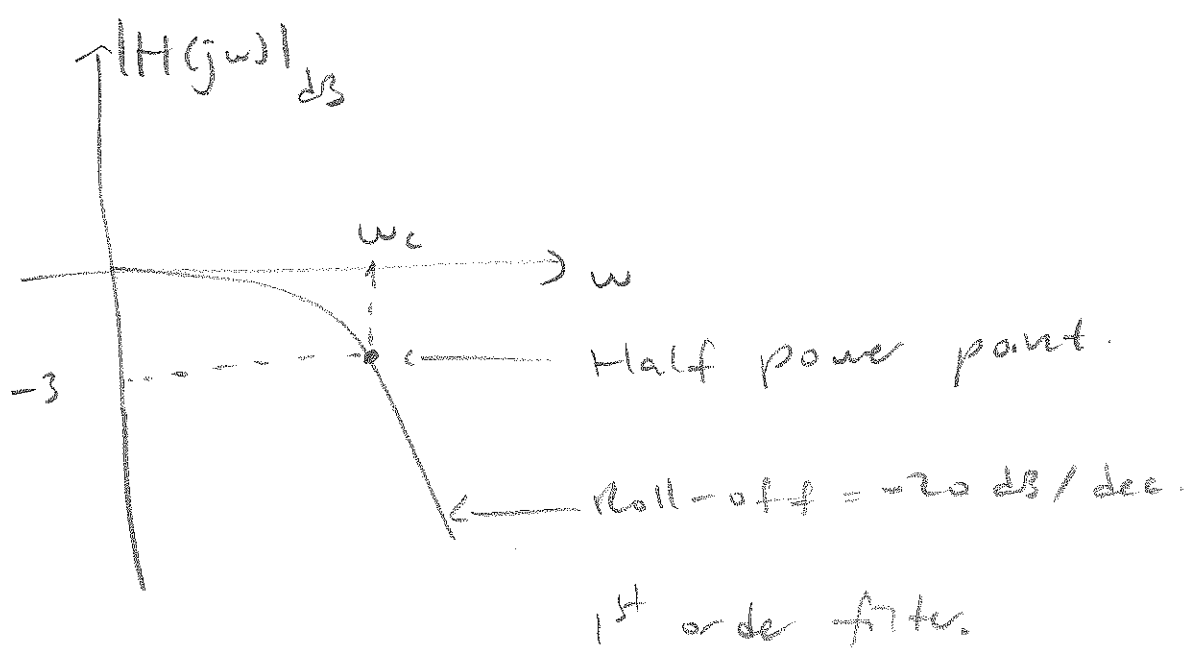$\Rightarrow H(s) = \frac{-1}{s+1}$, the minus sign affects the phase.




Also


$$H(j\omega) = \frac{-1}{1+j\omega} = \frac{1}{\sqrt{\omega^2+1}} \frac{e^{j \tan^{-1} 0}}{e^{j \tan^{-1} \omega}}$$

$|H(j\omega)|$ $\angle H(j\omega) = \theta(j\omega)$
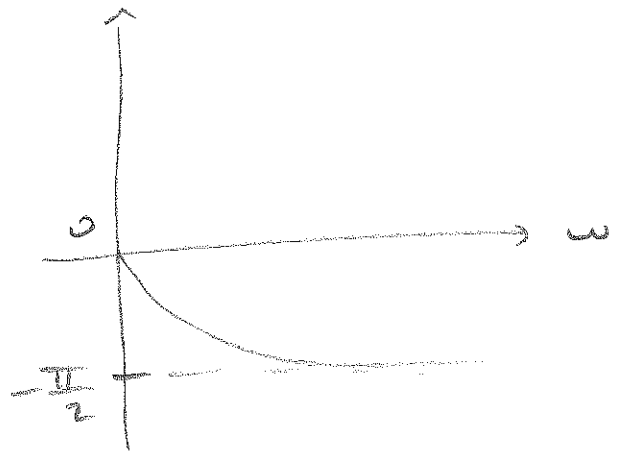
$$\theta(j\omega) = \frac{\tan^{-1} 0}{\tan^{-1} \omega} = -\tan^{-1} \omega$$



High-Pass Filter:

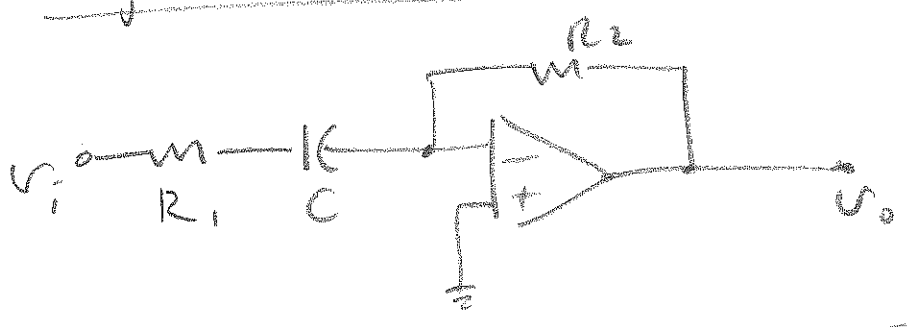


$$H(s) = \frac{-R_2}{R_1 + \frac{1}{sC}} = k \cdot \frac{s}{s + \omega_c}$$

where $k = \frac{R_2}{R_1} = \text{Gain}$, $\omega_c = \frac{1}{R_1 C} = \text{cut-off freq.}$

Band-Pass Filter:

This filter can be constructed as:

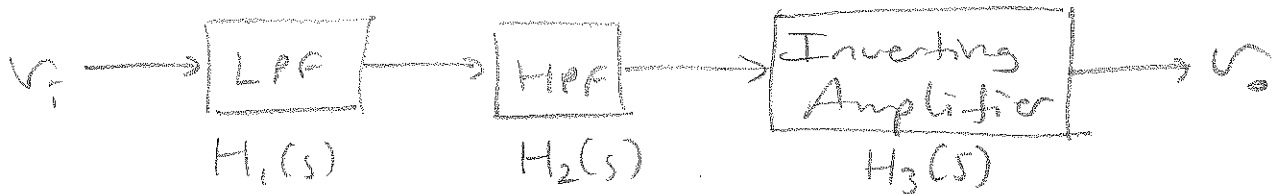

Total transfer function:

$$H(s) = H_1(s) H_2(s) H_3(s)$$

$$= \left(\frac{-\omega_{c2}}{s + \omega_{c2}} \right) \left(\frac{-s}{s + \omega_{c1}} \right) \cdot \left(-\frac{R_f}{R_i} \right)$$


$$= -k \frac{\omega_{c2} \cdot s}{s^2 + \omega_{c2} s + \omega_{c1} \omega_{c2}}$$

where



$$\omega_{c1} = \frac{1}{R_H C_H}$$

$$\omega_{c2} = \frac{1}{R_L C_L}$$

$$|H(j\omega)| = k = \frac{R_f}{R_i}$$

 

Band Reject Filter:

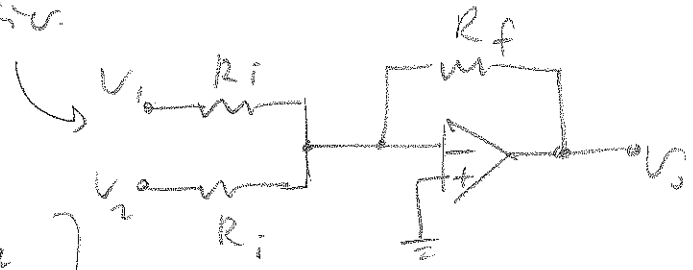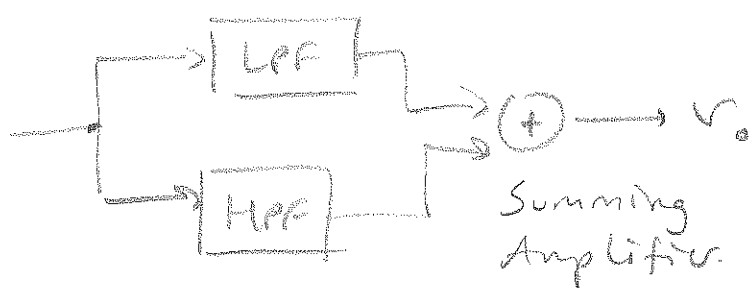

$$H(s) = \frac{R_f}{R_i} \left[\frac{s^2 + 2\omega_{c1}s + \omega_{c1}\omega_{c2}}{(s + \omega_{c1})(s + \omega_{c2})} \right]$$

where

$$\omega_{c1} = \frac{1}{R_L C_L}, \quad \omega_{c2} = \frac{1}{R_H C_H}, \quad k = \frac{R_f}{R_i}$$


High-Order Filters:



$$H(s) = \left(\frac{-1}{s+1} \right) \left(\frac{-1}{s+1} \right) \dots \left(\frac{-1}{s+1} \right) \quad (\text{for } \omega_c = 1 \text{ rad/sec})$$

$$\Rightarrow H(s) = \frac{(-1)^n}{(s+1)^n}$$

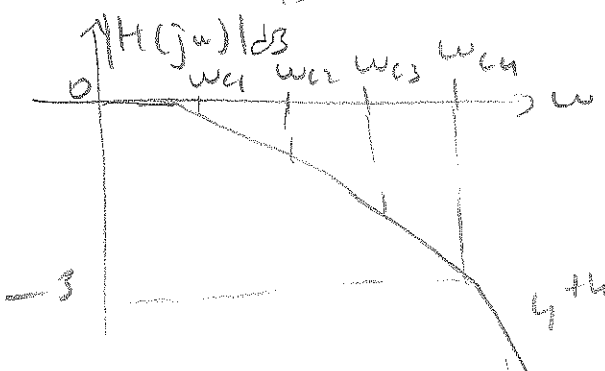where $n = \#$ of filters used & order of the filter




$$\omega_{cn} = \sqrt[n]{\sqrt{2} - 1} \quad (\text{n}^{\text{th}} \text{ order filter } \omega_{t\text{-off}} \text{ freq.})$$

4th order (-80dB/dec. roll-off)

Ex 1

Given the circuit

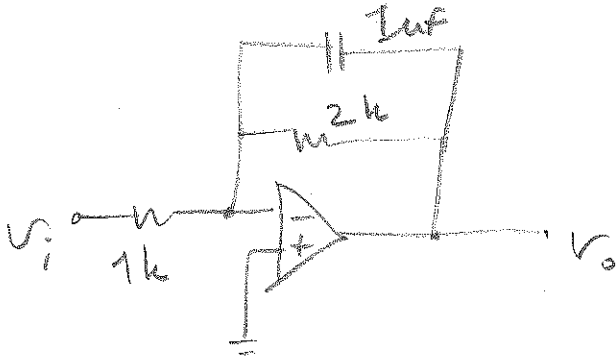


① Find the corner freq?

Ans: $\omega_c = \frac{1}{RC} = \frac{1}{(2k)(1\mu F)} = 500 \text{ rad/sec.}$


② Find the maximum gain?

Ans: $k = \frac{R_2}{R_1} = 2 //$

 

Ex:

Given the circuit

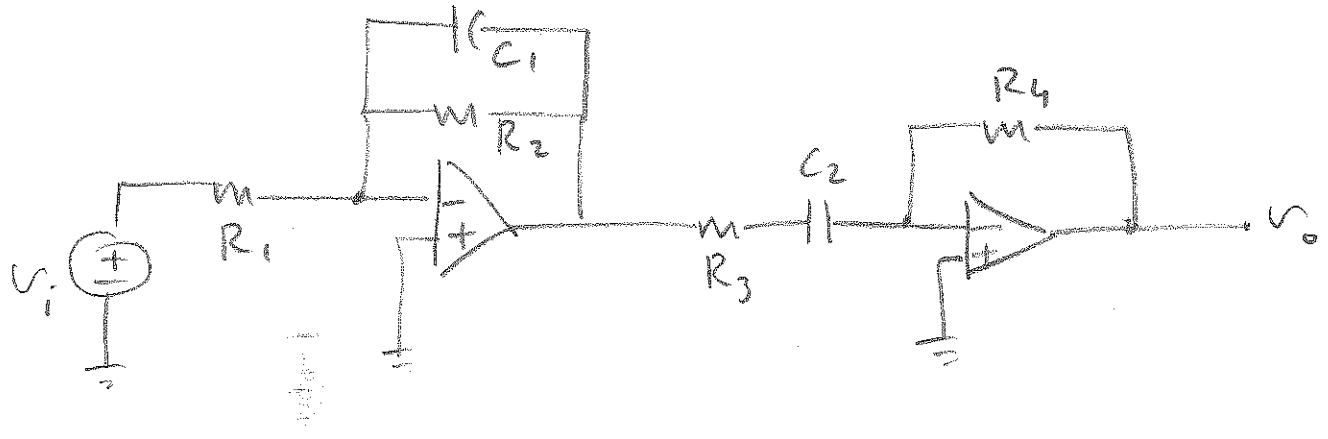

where $R_1 = R_2 = 80\Omega$, $C_1 = 0.2\mu F$
 $R_3 = R_4 = 8k\Omega$, $C_2 = 0.2\mu F$.

Question 1:

What is the type of this filter?

- a-) LP
- b-) BP**
- c-) HP
- d-) BR (Band Reject)

Question 2:

Find the corner frequencies?

Ans:

LP Stage:

$$\omega_c = \frac{1}{R_2 C} = \frac{1}{(80)(0.2 \times 10^{-6})} = 20000 \text{ rad/s}$$

$$2\pi f_{c2} = 20000 \text{ rad/s}$$

$$f_{c2} = 10 \text{ kHz}$$

HP Stage:


$$\omega_{c1} = \frac{1}{R_4 C} = \frac{1}{(8000)(0.2 \times 10^{-6})} = 200 \text{ rad/s}$$

$$\rightarrow f_{c1} = 100 \text{ Hz}$$

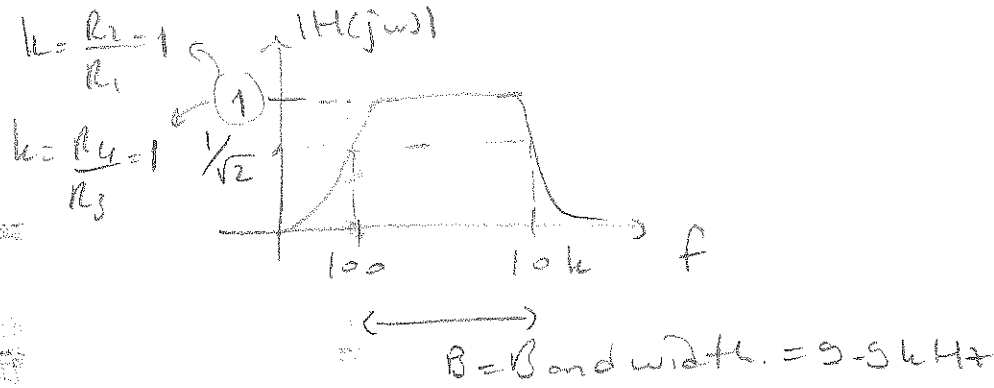Question 3 =


Find the bandwidth of this filter?

$$B = f_{c2} - f_{c1} = 10000 - 100 = 9900 \text{ Hz} = 9.9 \text{ kHz}$$



Oscillator Theory

Consider the following circuit

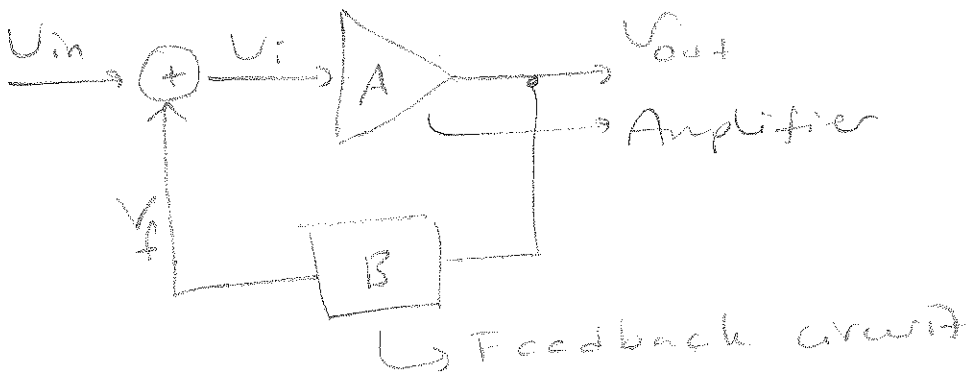

We aim to find $\frac{V_o}{V_{in}}$ = Closed Loop Gain

We have

$$V_o = AV_i \quad \text{--- (1)}$$

$$V_f = BV_o \quad \text{--- (2)}$$

$$V_{in} + V_f = V_i \quad \text{--- (3)}$$

Take eqn (3):

$$V_{in} + BV_o = \frac{V_o}{A}$$

$$\rightarrow V_{in} = \frac{V_o}{A} - BV_o = V_o \left(\frac{1}{A} - B \right)$$


$$\rightarrow \frac{V_o}{V_{in}} = \frac{V_o}{V_o \left(\frac{1}{A} - B \right)} = \frac{1}{\frac{1}{A} - B} = \frac{A}{1 - AB}$$

- If $V_{in} = V_f = V_i$ Then, $\frac{V_o}{V_{in}} = \frac{A}{1 + AB}$ (Negative feedback Closed Loop Gain)

- If $|AB| = 1$


$\frac{V_o}{V_{in}} = \infty$ (unstable) which means that the

signal inside the loop grows.

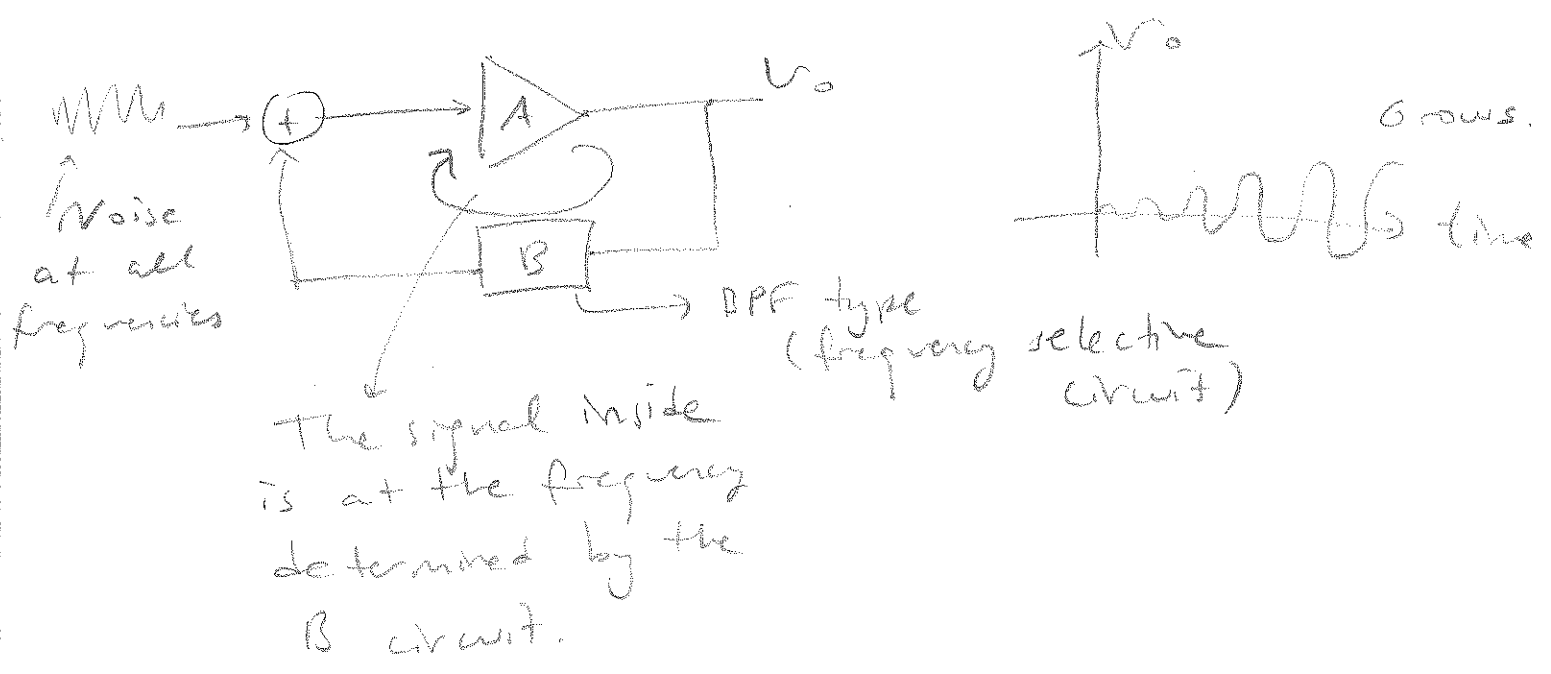

The signal inside is at the frequency determined by the B circuit.

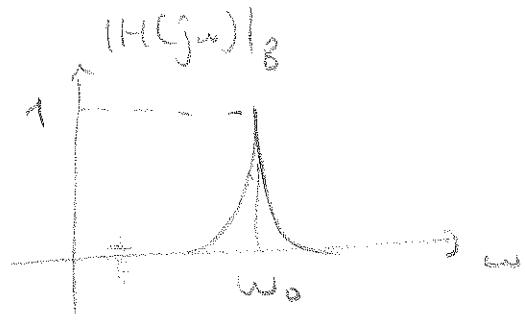- The oscillation starts from noise (V_{in}).
- B circuit determines the frequency of oscillation.
- B circuit is a frequency selective circuit.




- Consider $A_0 = \frac{A}{1-AB}$


- For $|AB|=1$, oscillation grows.

- As the frequency grows inside the loop the gain of the amplifier starts to decrease due to the fact that transistors enter the "SAT" region and the linearity is distorted.


As a result, $|AB| < 1$ and the gain is stabilized.

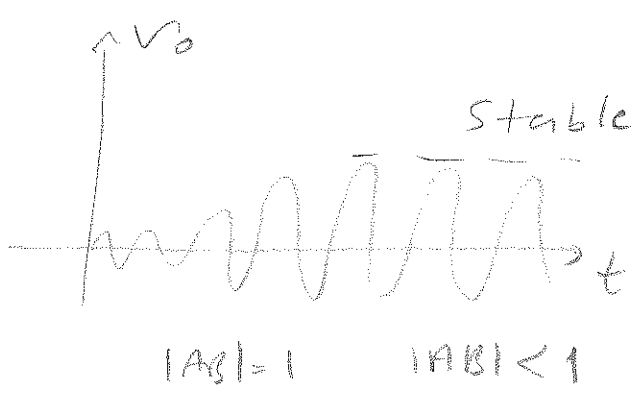

B-Circuit:

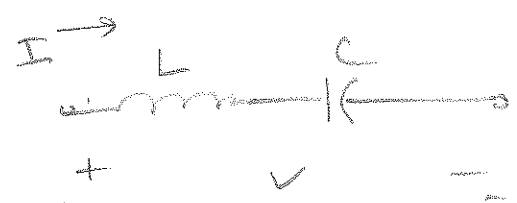


or

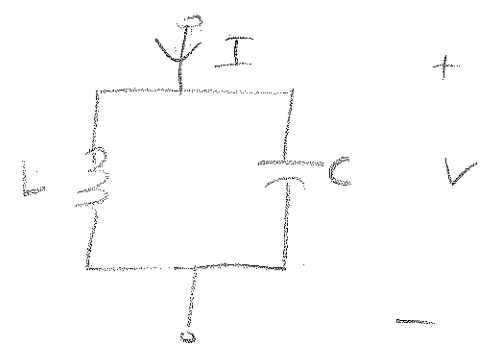

(Resonator circuit)

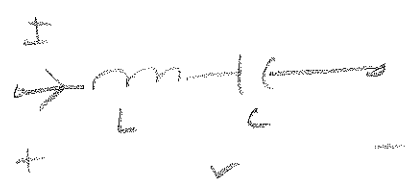- These circuits are in fact series RLC and parallel RLC circuits.
 - we have $R=0$ for series and $R=\infty$ for parallel circuits for zero energy dissipation.
- Let us consider the circuit



$$Z = \text{Impedance} = j\omega L + \frac{1}{j\omega C} = \frac{1 - \omega^2 LC}{j\omega C}$$

$Z=0$ (Resonance):


$$1 - \omega^2 LC = 0$$

$\rightarrow \omega = \frac{1}{\sqrt{LC}}$ is the resonance frequency.


or

$$f = \frac{1}{2\pi\sqrt{LC}} \text{ (Hz)}$$


is the Hz resonant frequency.

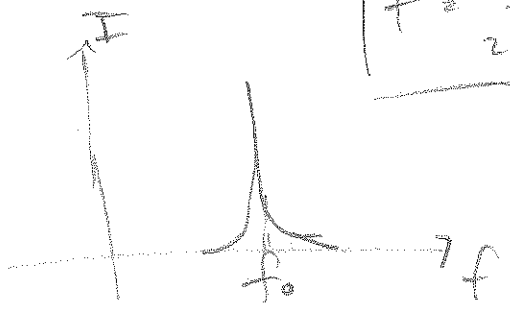

Implementation:

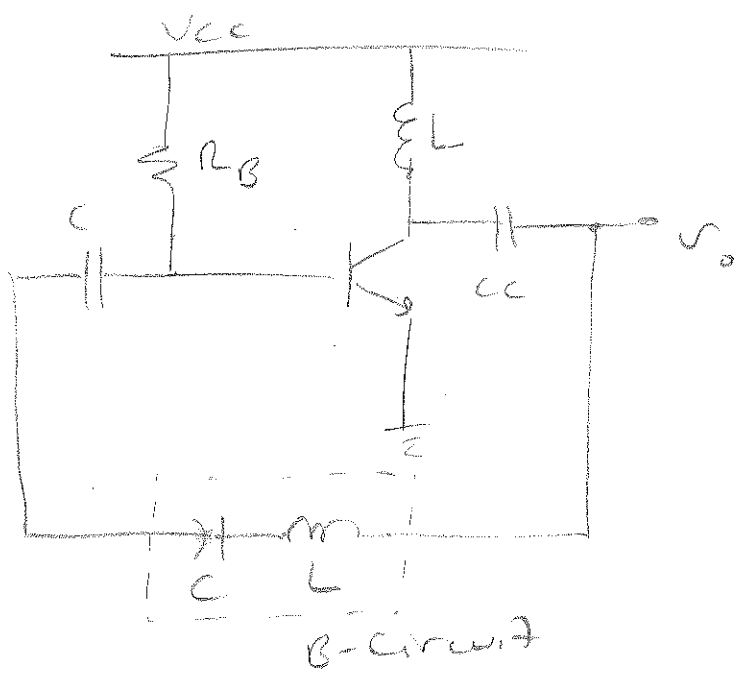


Sometimes we use:

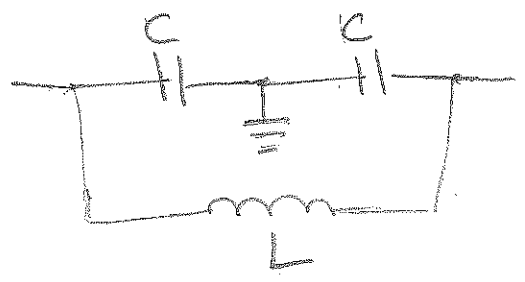

$$f_r = \frac{1}{2\pi \sqrt{\left(\frac{C}{2}\right)L}} \text{ (Hz)}$$

(Colpitts's oscillator)

or we use

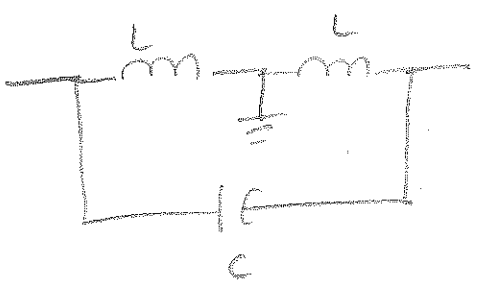

$$f_r = \frac{1}{2\pi \sqrt{(2L)C}} \text{ (Hz)}$$

(Hartley's Osc.)

Ex:

In oscillator theory, the gain factor $|AB| = 1$ grows the signal. After a while $|AB| < 1$ stabilizes the signal. What causes $|AB| < 1$?

Ans: Transistors enter the "saturation" as the signal grows.


Ex:

For Colpitts' oscillator, $C = 1\mu F$ and $L = 1mH$ in the feedback circuit. Find the oscillation frequency in Hz!

Ans:


$$f_r = \frac{1}{2\pi \sqrt{\frac{C}{2}} L} \Rightarrow f_r = \frac{1}{2\pi [(0.5 \times 10^{-6})(1 \times 10^{-3})]^{1/2}} = 7.1 \text{ kHz}$$

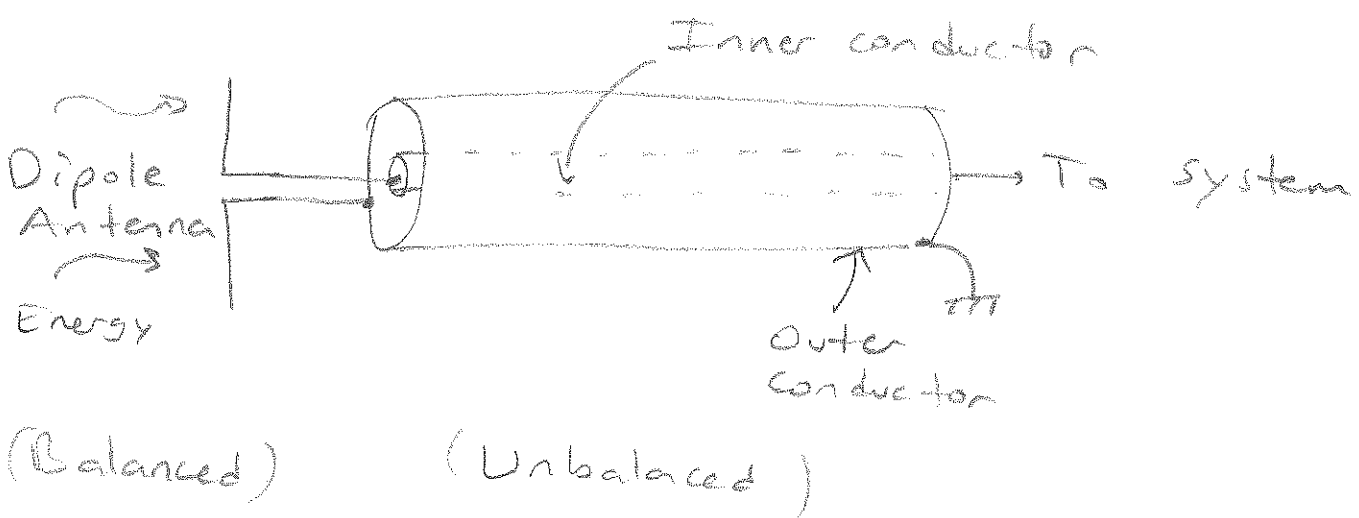Practical example is connecting a dipole antenna to a coaxial cable.



- Use of Transformers for Impedance Matching: -

Consider the following circuit:

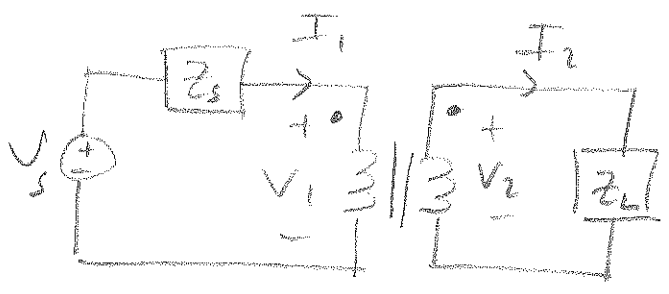

$$\underline{V}_1 = \frac{V_2}{a} \quad , \quad \underline{I}_1 = a \underline{I}_2$$

$\underline{V}_1, \underline{V}_2, \underline{I}_1, \underline{I}_2$ are phasors.

For matching:

$$\underline{Z}_m = \frac{1}{a} \underline{Z}_L$$