


Ex:

Match 150Ω dipole antenna to a 50Ω coaxial cable using a transformer balun.

Find $(N_1 : N_2)$

Turn ratio of the primary to secondary windings.

Ans:

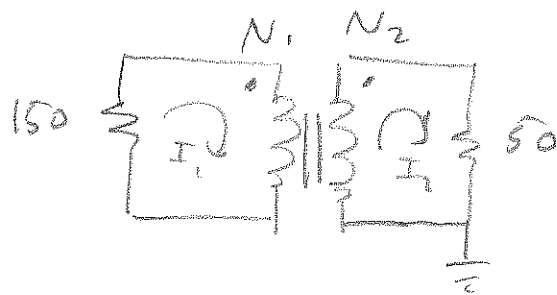

$N_1 : N_2 = ?$

$\frac{V_1}{N_1} = \frac{V_2}{N_2}$ and $N_1 I_1 = N_2 I_2$


$Z_{in} = \frac{1}{a^2} Z_L$

$\Rightarrow 150 = \frac{1}{a^2} 50 \Rightarrow a^2 = \frac{1}{3}$

$\frac{V_1}{V_2} = \frac{1}{a} = \frac{N_1}{N_2} \Rightarrow \frac{N_1}{N_2} = \sqrt{3}$


$\Rightarrow N_1 : N_2 = \sqrt{3} = 1$

$\Rightarrow N_1 : N_2 \approx 1.75 = 1$

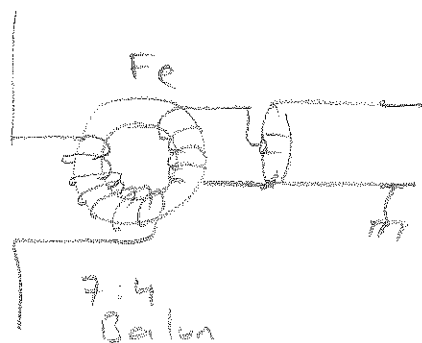


or $N_1 : N_2 = 7 : 4$

Note:

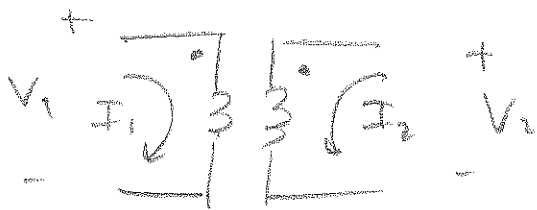


$$\frac{V_1}{N_1} = \frac{V_2}{N_2}$$

$$N_1 I_1 = -N_2 I_2$$

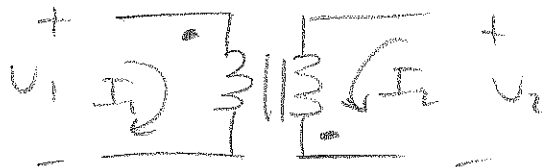


$$\frac{V_1}{N_1} = -\frac{V_2}{N_2}$$

$$N_1 I_1 = N_2 I_2$$

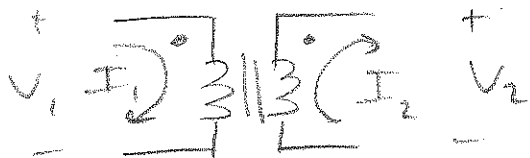


$$\frac{V_1}{N_1} = \frac{V_2}{N_2}$$

$$N_1 I_1 = N_2 I_2$$

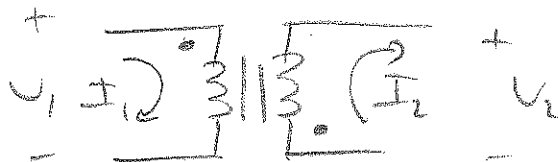


$$\frac{V_1}{N_1} = -\frac{V_2}{N_2}$$

$$N_1 I_1 = -N_2 I_2$$

 


- Two - Port Circuits -

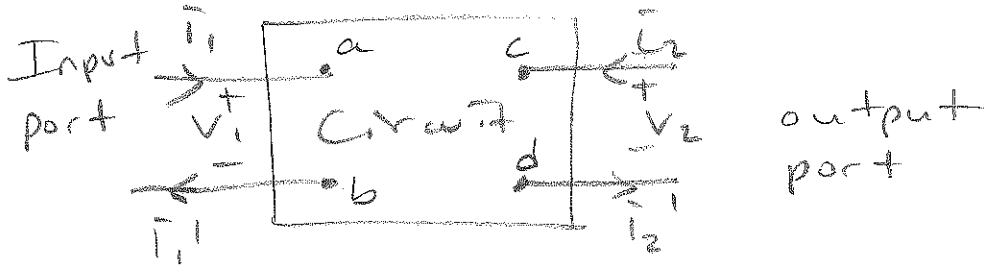Two port circuits are defined by the currents and voltages at two ports of the circuit.



or

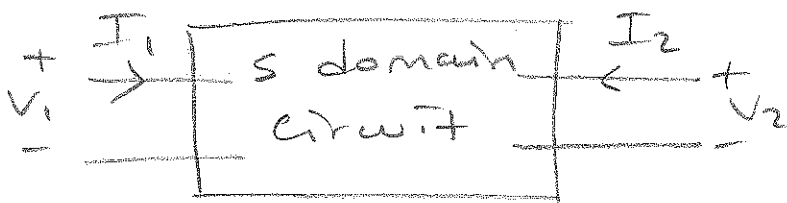

2 port equations:

$$\left. \begin{aligned} V_1 &= z_{11} I_1 + z_{12} I_2 \\ V_2 &= z_{21} I_1 + z_{22} I_2 \end{aligned} \right\} \underbrace{\begin{bmatrix} V_1 \\ V_2 \end{bmatrix}}_V = \underbrace{\begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix}}_{z\text{-parameters}} \underbrace{\begin{bmatrix} I_1 \\ I_2 \end{bmatrix}}_I$$

or

$$\left. \begin{aligned} I_1 &= Y_{11} V_1 + Y_{12} V_2 \\ I_2 &= Y_{12} V_1 + Y_{22} V_2 \end{aligned} \right\} \text{Y-parameters.}$$

or

$$\left. \begin{aligned} V_2 &= b_{11} V_1 - b_{12} I_1 \\ I_2 &= b_{21} V_1 - b_{22} I_1 \end{aligned} \right\} \text{b-param.}$$

$$\left. \begin{aligned} V_1 &= h_{11} I_1 + h_{12} V_2 \\ I_2 &= h_{21} I_1 + h_{22} V_2 \end{aligned} \right\} \text{h-param.}$$

or

$$\left. \begin{aligned} I_1 &= g_{11} V_1 + g_{12} I_2 \\ V_2 &= g_{21} V_1 + g_{22} I_2 \end{aligned} \right\} \text{g-param.}$$

z-Parameters:

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_Z \quad (\text{Input Impedance})$$

$$I_2 = 0$$

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_Z \quad (\text{Forward Transfer Impedance})$$

$$I_1 = 0$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_Z \quad (\text{Reverse Transfer Impedance})$$


$$I_2 = 0$$

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_Z \quad (\text{Output Impedance})$$

$$I_1 = 0$$

Ex:

Given the circuit

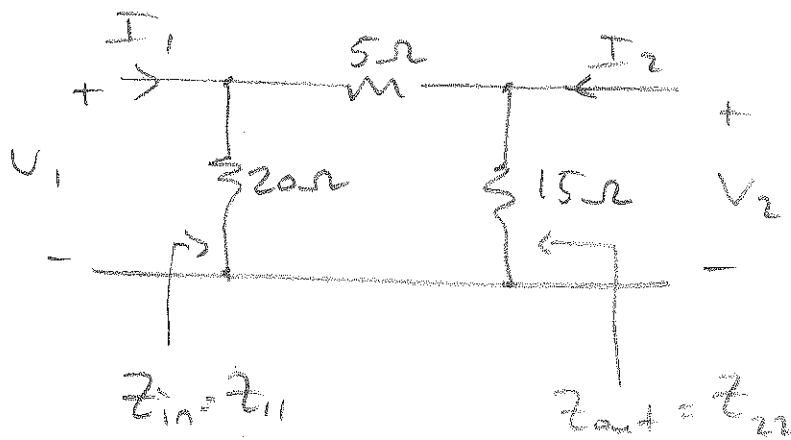

Find the Z -parameters of this 2-port circuit?

Ans:

Purely resistive circuit, thus it is also s -domain circuit.

$$\Rightarrow Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} = \frac{20 \cdot 20}{40} = 10\Omega$$

$$\rightarrow I_2 = 0$$

open circuit

when $I_2 = 0$

$$V_2 = \frac{V_1}{15+5} (15) = 0.75 V_1$$

$$\Rightarrow Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0} = \frac{0.75 V_1}{\frac{V_1}{10}} = 7.5\Omega$$

$$\Rightarrow Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0} = \frac{(15)(25)}{40} = 9.375\Omega$$

When port 1 is open,

$$V_1 = \frac{V_2}{5+20} (20) = 0.8 V_2 \quad \text{and} \quad I_2 = \frac{V_2}{9.375}$$

Thus,

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} = \frac{0.8 V_2}{\frac{V_2}{9.375}} = 7.5 \Omega$$

$$\Rightarrow Z = \begin{bmatrix} 10 & 7.5 \\ 7.5 & 9.375 \end{bmatrix} \Omega$$


Analysis of the Terminated Two-Port Circuit:

The important parameters of the terminated two-port circuits are:

- Input impedance $Z_{in} = \frac{V_1}{I_1}$ or the admittance $Y_{in} = \frac{I_1}{V_1}$
- The output current I_2 .
- Thevenin voltage and impedance (V_{th} , R_{th}) with respect to port 2.
- The current gain $\frac{I_2}{I_1}$.
- The voltage gain $\frac{V_2}{V_1}$.
- The voltage gain $\frac{V_2}{V_s}$.

Ex:

The two-port circuit is shown below.

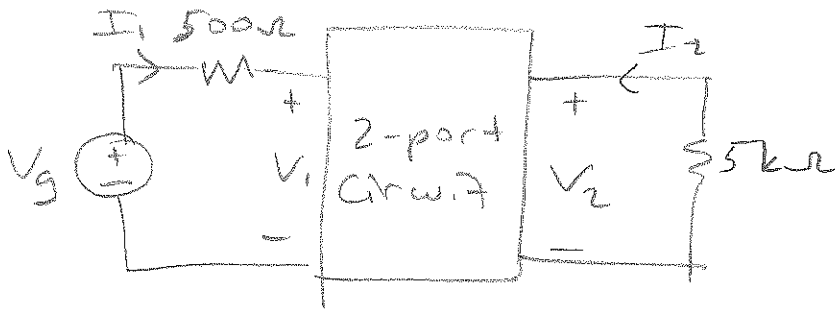

$$V_g = 500 \angle 0^\circ$$

Given $b_{11} = -20$

$$b_{12} = -3000 \Omega$$

$$b_{21} = -2 \text{ mS}$$

$$b_{22} = -0.2$$

Q1-

Find the phasor voltage V_2 ?

(From the table given)

Ans:

$$V_2 = I_2 (5k\Omega) \Rightarrow I_2 = \frac{-V_g \Delta b}{b_{11} z_g + b_{21} z_g z_L + b_{22} z_L + b_{12}}$$

$$I_2 = ?$$

where $z_g = 500 \Omega$, $z_L = 5k\Omega$

$$\text{and } \Delta b = (-20)(-0.2) - (-3000)(-2 \times 10^{-3}) = -2$$

Substitute all the parameters into the equation

$$I_2 = \frac{1}{13} \text{ A}$$

$$\Rightarrow V_2 = -I_2 (5000) = 263.16 \angle 0^\circ$$

Q2)

Find the average power delivered to the 5k Ω load?

Ans:

$$P = \frac{V_2^2}{2R} = \frac{263.16^2}{2(5000)} = 6.93 \text{ W}$$

Q3:

Find the average power delivered to the input port?

Ans:

$$P_i = \frac{1}{2} I_1^2 \cdot Z_{in} \quad (\text{From the table.})$$

where

$$Z_{in} = \frac{b_{22} Z_L + b_{12}}{b_{21} Z_L + b_{11}} = 133.33 \Omega$$

$$I_1 = \frac{500}{500 + 133.33} = 785.47 \text{ mA}$$

$$\Rightarrow P_i = \frac{1}{2} (785.47 \times 10^{-3})^2 \cdot (133.33) = \underline{44.55 \text{ W}}$$

TABLE 18.2 Terminated Two-Port Equations

z PARAMETERS		y PARAMETERS	
$Z_{in} = z_{11} - \frac{z_{12}z_{21}}{z_{22} + Z_L}$	$I_2 = \frac{-z_{21}V_s}{(z_{11} + Z_s)(z_{22} + Z_L) - z_{12}z_{21}}$	$Y_{in} = y_{11} - \frac{y_{12}y_{21}Z_L}{1 + y_{22}Z_L}$	$I_2 = \frac{y_{21}V_s}{1 + y_{22}Z_L + y_{11}Z_s + \Delta y Z_s Z_L}$
$I_1 = \frac{z_{21}}{z_{11} + Z_s} V_s$	$V_{Th} = \frac{z_{21}V_s}{z_{11} + Z_s}$	$V_{Th} = \frac{-y_{21}V_s}{y_{22} + \Delta y Z_s}$	$Z_{Th} = \frac{1 + y_{11}Z_s}{y_{22} + \Delta y Z_s}$
$Z_{Th} = z_{22} - \frac{z_{12}z_{21}}{z_{11} + Z_s}$	$I_1 = \frac{-z_{21}}{z_{22} + Z_L}$	$I_1 = \frac{y_{21}}{y_{11} + \Delta y Z_L}$	$V_2 = \frac{-y_{21}Z_L}{1 + y_{22}Z_L}$
$V_2 = \frac{z_{21}Z_L}{z_{11}Z_L + \Delta z}$	$V_1 = \frac{z_{21}Z_L}{(z_{11} + Z_s)(z_{22} + Z_L) - z_{12}z_{21}}$	$V_1 = \frac{y_{21}Z_L}{y_{12}y_{21}Z_s Z_L - (1 + y_{11}Z_s)(1 + y_{22}Z_L)}$	
a PARAMETERS		b PARAMETERS	
$Z_{in} = \frac{a_{11}Z_L + a_{12}}{a_{21}Z_L + a_{22}}$	$I_2 = \frac{-V_s \Delta b}{b_{11}Z_s + b_{21}Z_s Z_L + b_{22}Z_L + b_{12}}$	$Z_{in} = \frac{b_{22}Z_L + b_{12}}{b_{21}Z_L + b_{11}}$	$V_{Th} = \frac{V_s \Delta b}{b_{22} + b_{21}Z_s}$
$I_1 = \frac{V_s}{a_{11}Z_L + a_{12} + a_{21}Z_s Z_L + a_{22}Z_s}$	$Z_{Th} = \frac{b_{11}Z_s + b_{12}}{b_{22}Z_s + b_{22}}$	$V_{Th} = \frac{b_{11}Z_s + b_{12}}{b_{22}Z_s + b_{22}}$	$I_1 = \frac{-\Delta b}{b_{11} + b_{21}Z_L}$
$V_{Th} = \frac{V_s}{a_{11} + a_{21}Z_s}$	$I_2 = \frac{-\Delta b}{b_{11} + b_{21}Z_L}$	$Z_{Th} = \frac{b_{11}Z_s + b_{12}}{b_{22}Z_s + b_{22}}$	$V_2 = \frac{\Delta b Z_L}{b_{12} + b_{21}Z_L}$
$Z_{Th} = \frac{a_{12} + a_{22}Z_s}{a_{11} + a_{21}Z_s}$	$V_1 = \frac{\Delta b Z_L}{b_{12} + b_{21}Z_L}$	$I_1 = \frac{-1}{a_{21}Z_L + a_{22}}$	$V_1 = \frac{\Delta b Z_L}{b_{12} + b_{21}Z_L}$
$I_1 = \frac{V_s}{a_{21}Z_L + a_{22}}$	$V_2 = \frac{Z_L}{a_{11}Z_L + a_{12}}$	$V_2 = \frac{Z_L}{a_{11}Z_L + a_{12}}$	$V_2 = \frac{\Delta b Z_L}{b_{12} + b_{21}Z_L}$
$V_1 = \frac{Z_L}{a_{11}Z_L + a_{12}}$	$V_s = \frac{Z_L}{(a_{11} + a_{21}Z_s)Z_L + a_{12} + a_{22}Z_s}$		
h PARAMETERS		g PARAMETERS	
$Z_{in} = h_{11} - \frac{h_{12}h_{21}Z_L}{1 + h_{22}Z_L}$	$I_2 = \frac{h_{21}V_s}{(1 + h_{22}Z_L)(h_{11} + Z_s) - h_{12}h_{21}Z_L}$	$Y_{in} = g_{11} - \frac{g_{12}g_{21}}{g_{22} + Z_L}$	$I_2 = \frac{-g_{21}V_s}{(1 + g_{11}Z_s)(g_{22} + Z_L) - g_{12}g_{21}Z_s}$
$I_1 = \frac{-h_{21}V_s}{h_{22}Z_s + \Delta h}$	$V_{Th} = \frac{h_{21}V_s}{Z_s + h_{11}}$	$V_{Th} = \frac{g_{21}V_s}{1 + g_{11}Z_s}$	$Z_{Th} = g_{22} - \frac{g_{12}g_{21}Z_s}{1 + g_{11}Z_s}$
$Z_{Th} = \frac{h_{21}}{h_{22}Z_s + \Delta h}$	$I_1 = \frac{h_{21}}{1 + h_{22}Z_L}$	$I_1 = \frac{-g_{21}}{g_{11}Z_L + \Delta g}$	$V_2 = \frac{g_{21}Z_L}{g_{22} + Z_L}$
$V_2 = \frac{-h_{21}Z_L}{\Delta h Z_L + h_{11}}$	$V_1 = \frac{-h_{21}Z_L}{\Delta h Z_L + h_{11}}$	$V_1 = \frac{g_{21}Z_L}{g_{22} + Z_L}$	$V_2 = \frac{g_{21}Z_L}{(1 + g_{11}Z_s)(g_{22} + Z_L) - g_{12}g_{21}Z_s}$
$V_1 = \frac{-h_{21}Z_L}{(h_{11} + Z_s)(1 + h_{22}Z_L) - h_{12}h_{21}Z_L}$			

$z_{12} = z_{21} = 17 \Omega$

Two-Port Circuit

The circuit is driven at port 1 in the domain circuit diagram for Z_s represents the internal impedance of the source, and Z_L the load impedance expressing the terminal load of port 2. The two-port parameters V_s, Z_s, Z_L of the external circuit define its terminal characteristics. The input impedance $Z_{in} = I_1/V_1$ is the impedance (with respect to port 2)

Parameters

derived, we develop the external two-port portion of the circuit involving the y, a, b, h parameters.