

# EE 206 Circuit Theory

## Lab 2

### Average Power and Reactive Power

The aim of this lab is to analyze ac power for purely resistive, inductive and capacitive circuits.

Lab procedure

#### 1. Purely resistive circuit:

Connect an ac voltage source to a resistor as shown below:

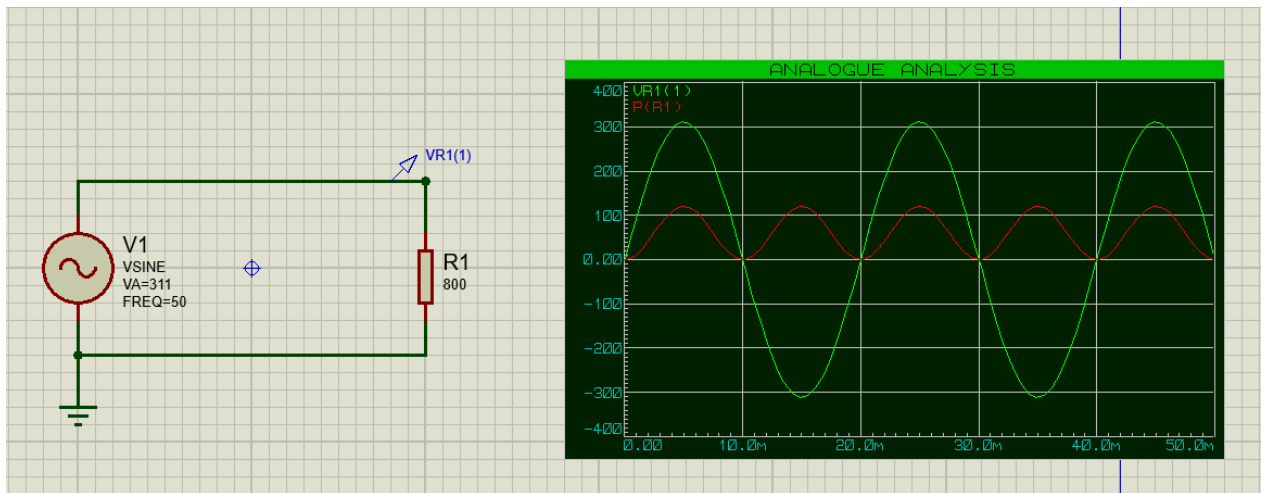


Figure 1. ac power

Plot the instantaneous power and measure the average power. Fill the table below. You can maximize the graph by right clicking and select “maximize”. Then, place a cursor to read the values on the average power. Remember, for resistive circuits,  $\theta_v = \theta_i$ .


Table 1.

$P_{avg} = V_m^2/2R$ (Calc.)	$P_{avg}$ (Measured)	$p = P_{avg} + P_{avg}\cos(2\omega t)$

#### 2. Purely inductive circuit:

Connect an ac voltage source to an inductor as shown below:

Note that we have to connect a series 1Ω resistor, otherwise the circuit doesn't work.

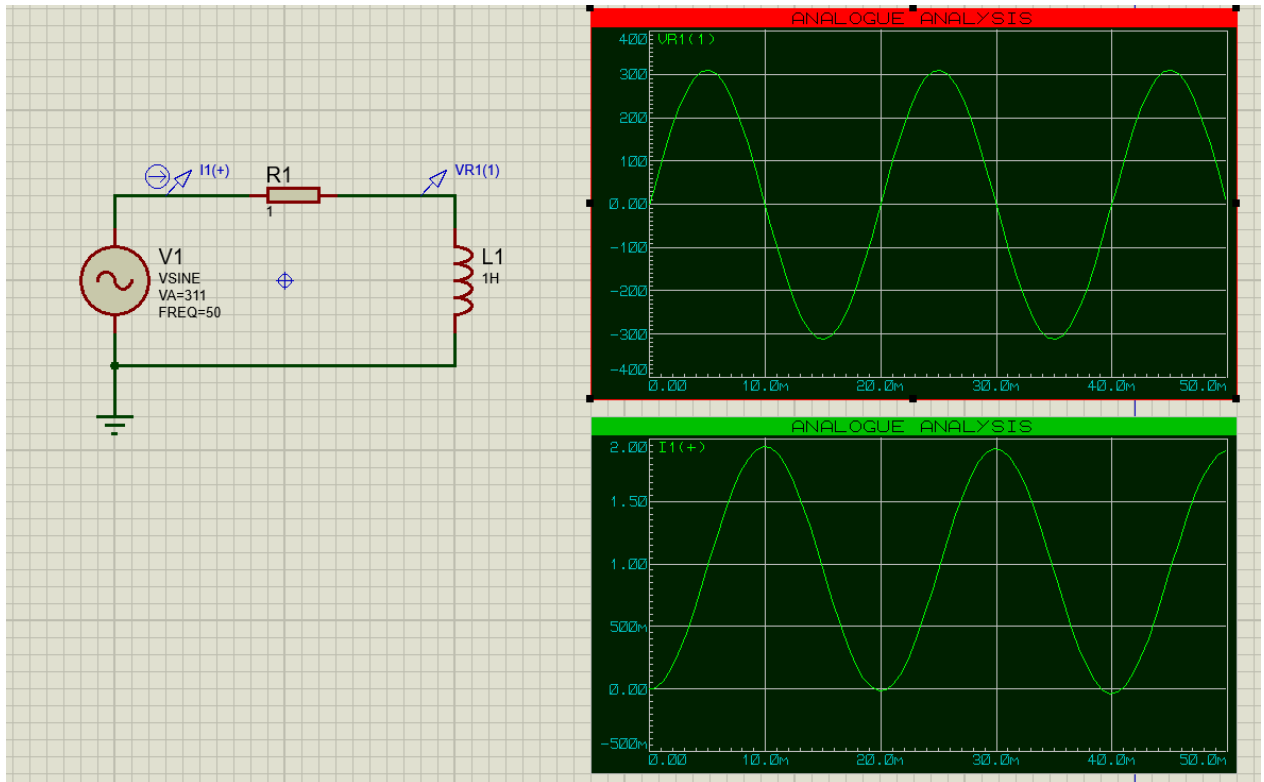

**Figure 1. ac power (purely inductive)**

Note that the current lags the voltage by  $90^\circ$ .

Fill the table below. Write the expressions for the voltage and the current. Write the expression for the reactive power  $Q$ , and the instantaneous power

$$p = -Q \sin(2\omega t)$$

where


$$Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i).$$

Table 2.

$v(t)$ (measured)	$i(t)$ (measured)	$Q$ (reactive power)	$p$ (inst. power)

### 1. Purely capacitive circuit:

Connect an ac voltage source to a capacitor as shown below:

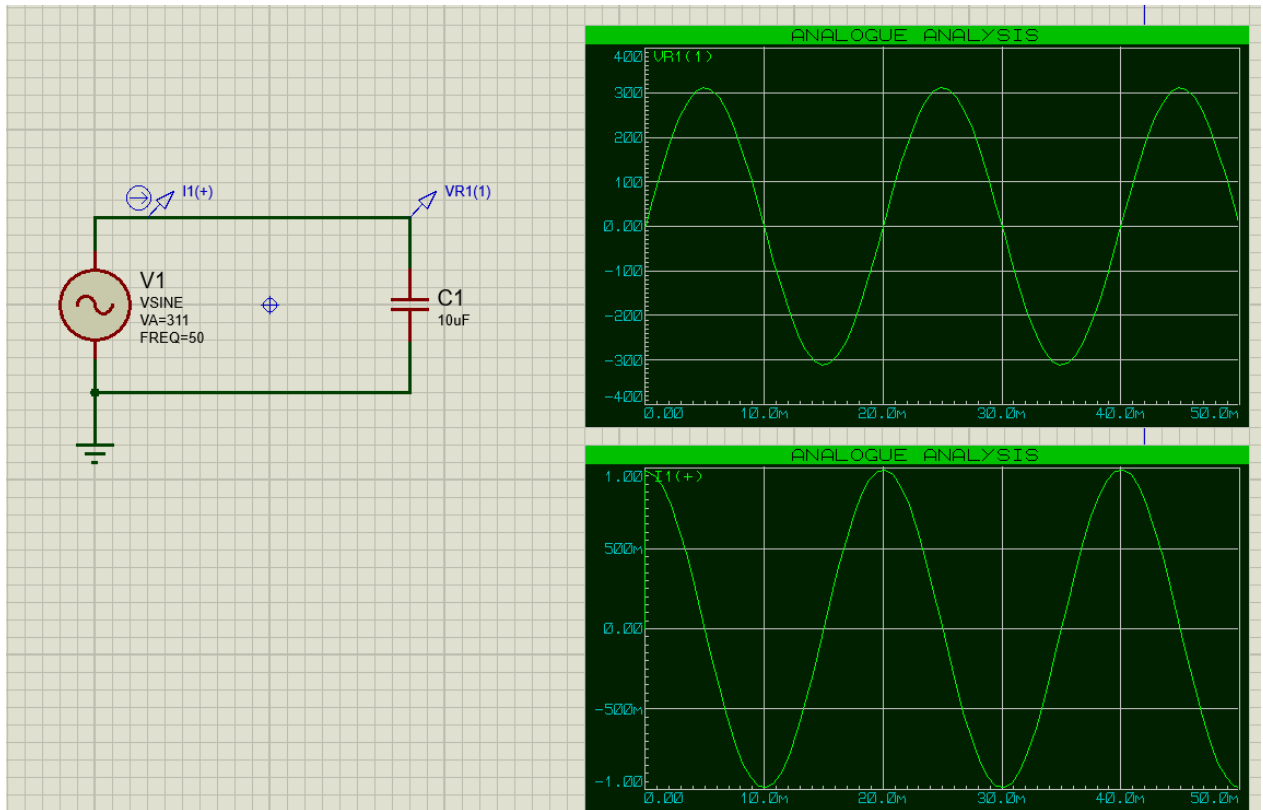

**Figure 1. ac power (purely capacitive)**

Note that the current leads the voltage by  $90^\circ$ .

Fill the table below. Write the expressions for the voltage and the current. Write the expression for the reactive power  $Q$ , and the instantaneous power

$$p = -Q \sin(2\omega t)$$

where

$$Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i).$$

Table 3.

$v(t)$ (measured)	$i(t)$ (measured)	$Q$ (reactive power)	$p$ (inst. power)

Results and Conclusion:

Write the summary of what you have learned in this lab.