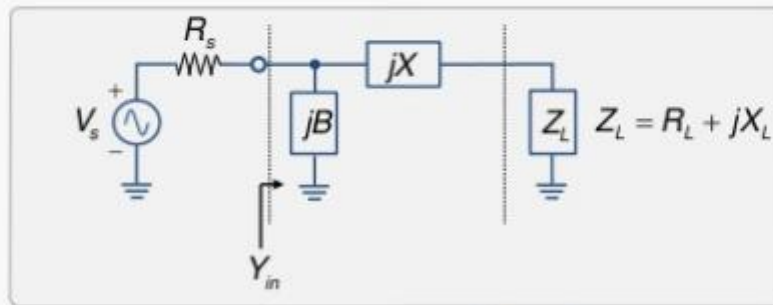


➤ Case (b) $R_s > R_L$



X : matching reactance
B : matching susceptance

Goal:

$$Y_{in} = \frac{1}{R_s} \quad \Gamma = \frac{\frac{1}{R_s} - Y_{in}}{\frac{1}{R_s} + Y_{in}} = 0$$

Again, we want to find X and B


$$Y_{in} = jB + \frac{1}{(R_L + jX_L) + jX} = \frac{1}{R_s}$$

Real part: $BR_s(X + X_L) = R_s - R_L$

Imaginary part: $(X + X_L) - BR_s R_L = 0$

Use resonator concept:

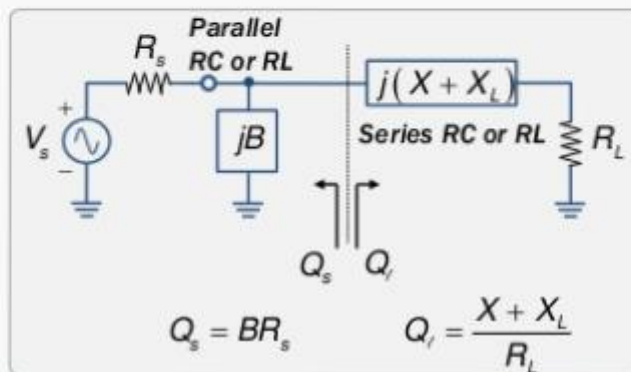When the impedances are matched, the imaginary part of the input admittance looking into the matching network is equal to zero.



Imaginary part: $(X + X_L) - BR_s R_L = 0$ $\frac{X + X_L}{R_L} = Q = BR_s = Q_s = Q$

Real part: $BR_s(X + X_L) = R_s - R_L$

→ $Q^2 R_L = R_s - R_L$ $Q = \pm \sqrt{\frac{R_s}{R_L} - 1}$



Choose $Q = Q_s = Q_v = +\sqrt{\frac{R_s}{R_L} - 1}$

When Q is chosen, X and B are also decided.

$B = \frac{Q}{R_s} = \frac{1}{R_s} \sqrt{\frac{R_s}{R_L} - 1}$ (>0 , capacitance)

$X = R_L Q - X_L = R_L \sqrt{\frac{R_s}{R_L} - 1} - X_L$ (>0 , inductance)
(<0 , capacitance)

• Series-to-Parallel transformation

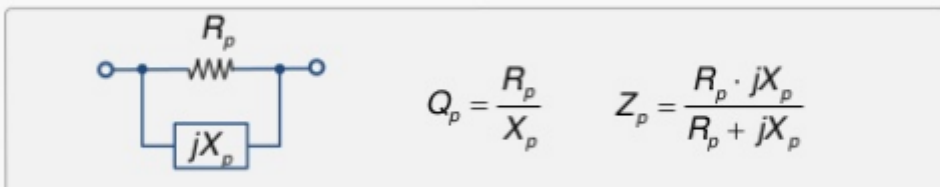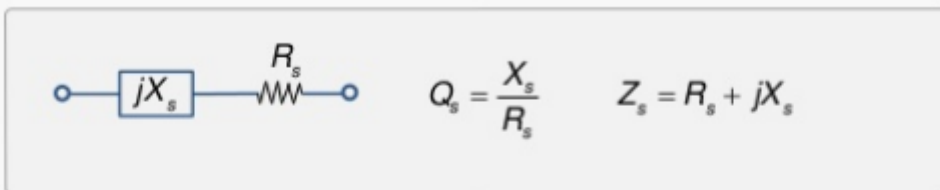

$Q_s = Q_p = Q = \frac{X_s}{R_s} = \frac{R_p}{X_p}$ } $R_s(1+Q^2) = R_p$
 $Z_s = Z_p = R_s + jX_s = \frac{R_p \cdot jX_p}{R_p + jX_p}$