

26 Eylül 2020 Cumartesi 17:16

Electric potential (voltage): Work done by 1C charges. $= \frac{E}{q}$

E = Electric potential energy. (Joules)

q = charge. (Coulombs)

$$\text{Current} = \frac{q}{t} \text{ (A)} = I$$

q = charge.



t = time. (sec.)

$$\text{Power} = \frac{E}{t} \text{ (watts)} = \frac{E}{q} \cdot \frac{q}{t} = V \cdot I \text{ (W)}.$$

I deal Basic Circuit Elements:

It is an electrical component with the following Properties:

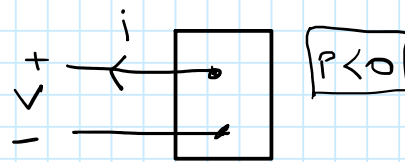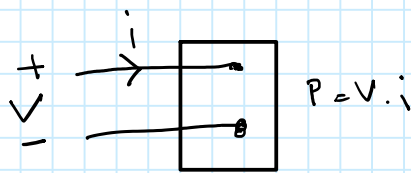- 1-) Two terminals.
- 2-) Can be described as voltage or current.
- 3-) Can not be subdivided into other elements.



If the current is going out of the circuit element, this refers to the existence of an energy source (generator).

If the power consumption by the element is positive, ($P > 0$), the power is being delivered to the circuit inside the box.

If the power is negative, $P < 0$, the power is being extracted from the circuit inside the box.


Chapter 2: Circuit Elements:

There are two circuit elements: voltage and current sources.


- Ideal voltage source: Provides a constant voltage across its terminals regardless of the current.
- Ideal current source: Similar to the voltage source. It provides current across its terminals regardless of the voltage.

If circuit elements do not depend on any other parameter, they are called "independent sources."

Circuit symbols:

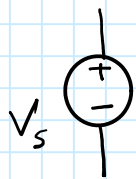


Ideal Independent voltage source.

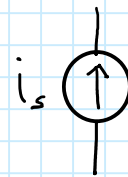


Ideal indep. current source.

$$v_s = \mu \cdot v_x$$

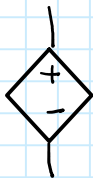

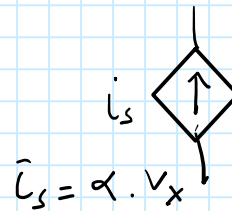
Ideal dependent voltage controlled voltage source.



$$i_s = \alpha \cdot v_x$$


Ideal dependent voltage controlled current source.

$$v_s$$

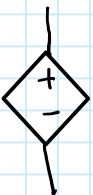

Ideal dependent current controlled voltage source.

$$v_s = \beta \cdot i_x$$

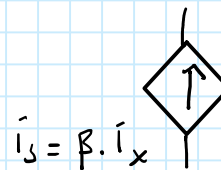


$$i_s = \beta \cdot i_x$$

Ideal dependent current controlled current source.


Constraints for the Connection of Circuit Elements:

- Two voltage sources:

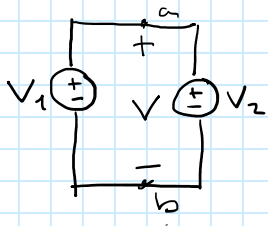


$$\Rightarrow V_1 = V_2 = V$$


Also, the polarities must be the same.

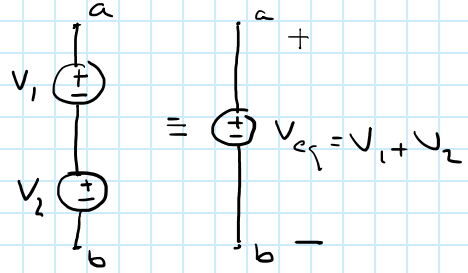

- Two current sources:

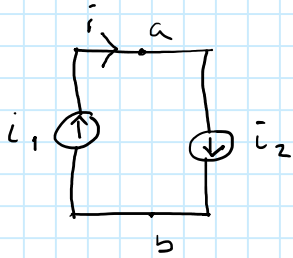



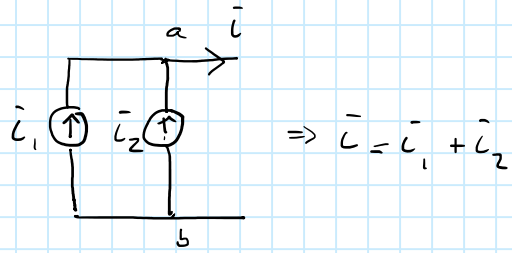
$$\Rightarrow \bar{i}_1 = \bar{i}_2 = \bar{i}$$



$$\Rightarrow \bar{i} = \bar{i}_1 + \bar{i}_2$$


Ex:

Determine which connections are valid.

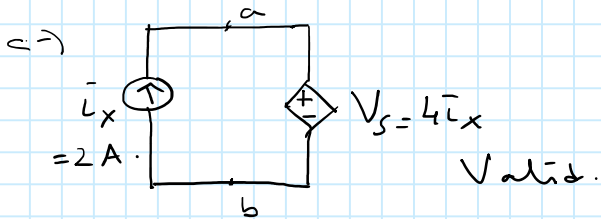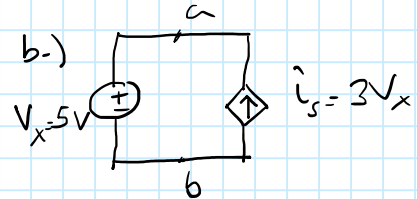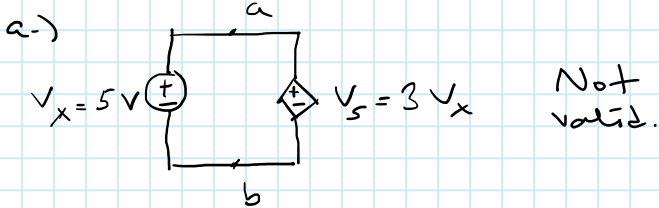

\Rightarrow Ideal voltage source supplies the same voltage regardless of the current, and vice versa. Thus, this is valid.

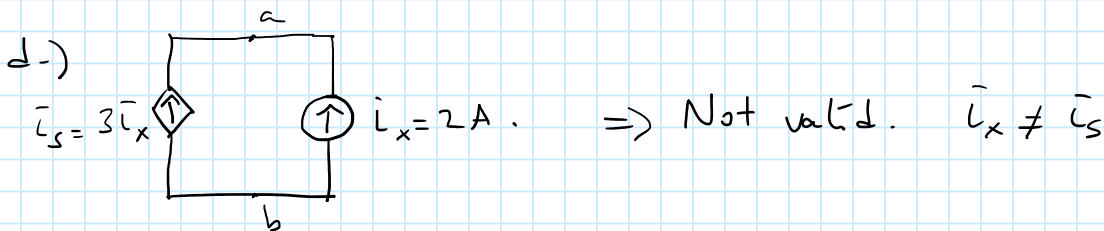\Rightarrow Because of the same reason in part b.



Two important concepts:

- Active element: A device capable of generating electrical energy. ($P < 0$)
- Passive element: A device that can not generate electrical energy. ($P > 0$). Examples: Resistors, inductors, capacitors. (lumped elements).



Resistance:

is the capacity of materials to resist the current flow. (impede, oppose)

Ohm's law: $V = I \cdot R$

Reciprocal of resistance is called "conductance" with a symbol "G".

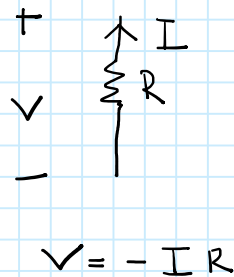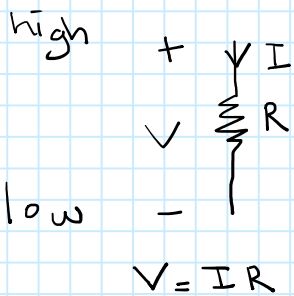$\Rightarrow G = \frac{1}{R}$ (Siemens or S) \hookrightarrow "mho" $R (\Omega = \text{ohm})$



$G = \frac{1}{R} \cdot (S)$





$P = VI = I^2 R (W)$

Also, $P = \frac{V^2}{R} (W)$

$I = VG$ $P = V^2 \cdot G$

Ex:

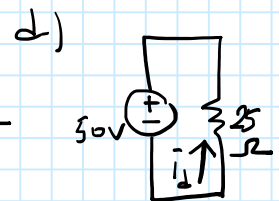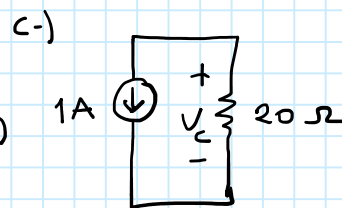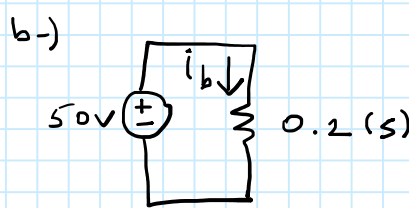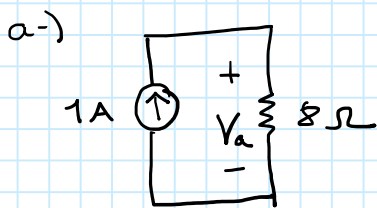Calculate the values of v and i , and determine the power dissipated in each resistor.



Ans:

a-) $V_a = I \cdot R = (1A)(8\Omega) = 8V$, $P_{8\Omega} = \frac{V^2}{R} = \frac{8^2}{8} = 8 \text{ Watts}$.

b-) $i_b = \frac{V}{R} = V \cdot G = (50V)(0.2) = 10A$, $P_{0.2} = V^2 G = 500W$.

$$c \rightarrow V_c = i \cdot R = \underbrace{(-1A)}_i (20 \Omega) = -20V; \quad P_{20\Omega} = \frac{V^2}{R} = \frac{(-20)^2}{20} = 20W.$$

$$d \rightarrow V_c = -i \cdot R$$


$$\Rightarrow 50 = -i_d (25)$$

$$\Rightarrow i_d = -2A$$

, $P = \frac{V^2}{R} = (-50)^2 / 25 = 100W.$
 - sign indicates that the original selection of the current direction is really the opposite.

Kirchoff's Laws:

Suppose we have the following circuit,

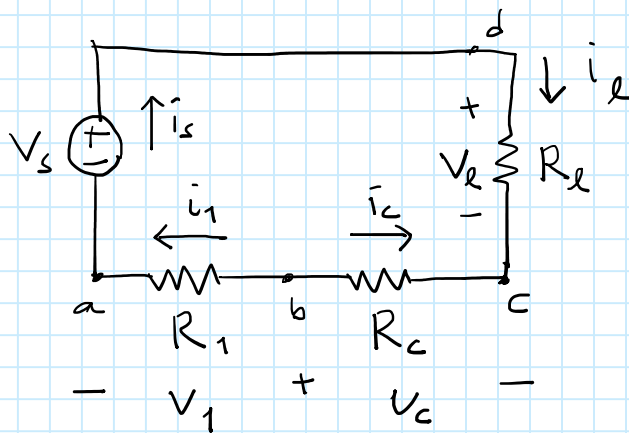

$$V_1 = i_1 R_1$$

$$V_c = i_c R_c$$

$$V_l = i_l R_l$$

We consider leaving currents positive, and entering currents negative.

Kirchoff's Current Law (KCL):

The algebraic sum of the currents at any point in a circuit is zero.

At point a:

$$i_s - i_1 = 0$$

At point b:

$$i_1 + i_c = 0$$

At point c:

$$-i_c - i_l = 0$$

At point d:

$$i_l - i_s = 0$$

Note that initial assumption of currents and voltages are not important. At the end of the solution, we get results which are + or -, indicating the real directions.

Kirchoff's Voltage Law (KVL):

The algebraic sum of all the voltages around any closed path in a circuit is zero.

Closed path: dcba (we follow clockwise direction.)

$$V_L - V_C + V_1 - V_S = 0 \quad (\text{KVL equation.})$$


(+ \rightarrow - is always positive.)

Closed path: dabcd (ccw)

$$V_S - V_1 + V_C - V_L = 0 \quad (\text{The same equation as before.})$$

Ex:

Given the circuit below:

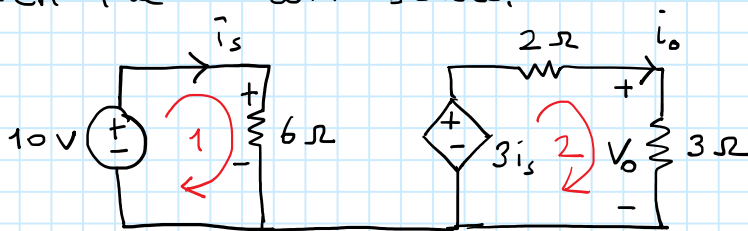

a-) Find V_o from KVL and Ohm's law.

b-) Show that $P_{\text{total}} \Big|_{\text{dissipated}} = P_{\text{total}} \Big|_{\text{developed}}$ (Conservation of energy.)

Ans:

a-) KVL in loop 1:

$$-10V + 6i_s = 0$$

$$\Rightarrow i_s = \frac{10}{6} = \frac{5}{3} \text{ A.}$$

Also, KVL for loop 2:

$$-3i_s + 2i_o + V_o = 0$$

$$-5 + 2i_o + V_o = 0$$

Ohm's law:

$$V_o = 3i_o$$

Thus,

$$-5 + 2i_o + 3i_o = 0$$

$$5i_o = 5$$

$$\Rightarrow i_o = 1 \text{ A.}$$

$$\text{Then, } V_o = 3i_o = 3 \text{ V.}$$

b-) Power for indep. voltage source:

$$P = Vi = (10V) \cdot i_s = 10 \cdot \left(\frac{5}{3}\right) = -16.7 \text{ W}$$

Also,

$$P_{6\Omega} = v\bar{i} = (10V) \bar{i}_s = 16.7 \text{ W}$$

$$P_{2\Omega} = \bar{i}^2 R = i_o^2 (2) = (1)^2 (2) = 2 \text{ W}$$

$$P_{3\Omega} = \bar{i}^2 R = i_o^2 (3) = (1)^2 (3) = 3 \text{ W}$$


HW2

P7

Thursday, March 9, 2023 9:32 AM


Resistive Circuits:

Resistors in Series:

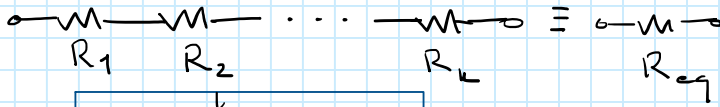

$$R_{eq} = \sum_{i=1}^k R_i \quad (\Omega)$$


Resistors in Parallel:

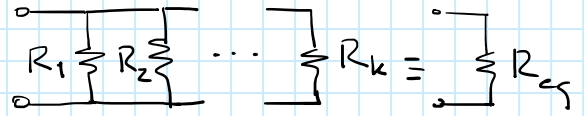

$$R_{eq} = \frac{1}{\sum_{i=1}^k \left(\frac{1}{R_i}\right)} \quad (\Omega)$$

Voltage Divider:

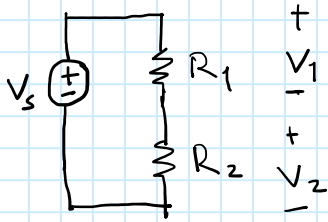
- Short method to find voltages when several resistors are connected in series.



$$V_1 = V_s \cdot \frac{R_1}{R_1 + R_2}$$

$$V_2 = V_s \cdot \frac{R_2}{R_1 + R_2}$$

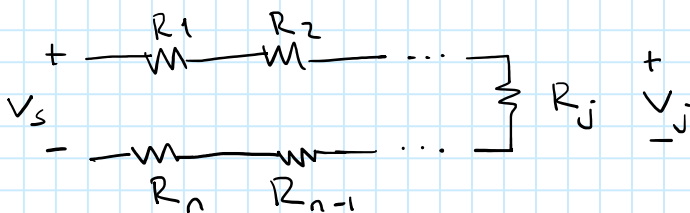In case of n resistors connected in series:




$$V_j = V_s \cdot \frac{R_j}{R_{eq}}$$

$$R_{eq} = R_1 + R_2 + \dots + R_n$$

Current Divider:

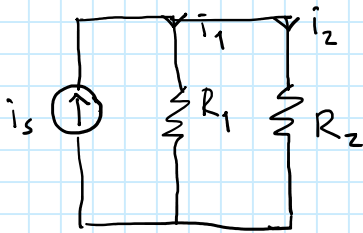
It is a rule for finding the current passing through the resistors which are connected in parallel.



$$i_1 = \bar{i}_s \cdot \frac{R_2}{R_1 + R_2}$$

$$i_2 = \bar{i}_s \cdot \frac{R_1}{R_1 + R_2}$$

For general current division, we have:

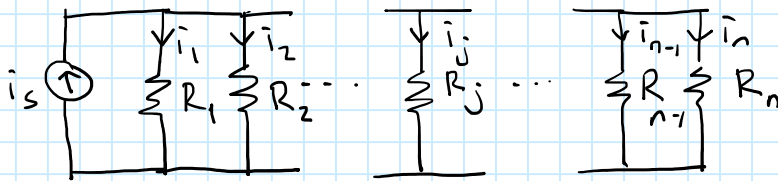


$$i_j = \bar{i}_s \cdot \frac{R_{eq}}{R_j}$$

where

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}}$$

Ex:

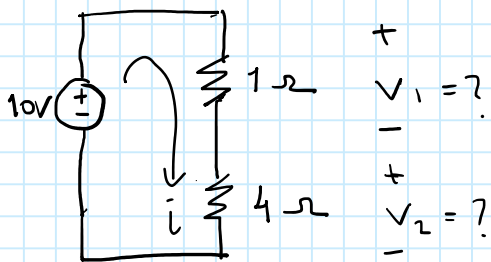


Ans:

By using the voltage division rule:

$$V_1 = 10 \cdot \frac{1}{1+4} = \frac{10}{5} = 2V$$

$$V_2 = 10 \cdot \frac{4}{1+4} = \frac{40}{5} = 8V$$

Ex:

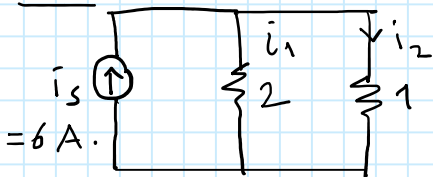

Find \bar{i}_1, \bar{i}_2 .

Ans:

By using the current division

$$\bar{i}_1 = \bar{i}_s \cdot \frac{(1\Omega)}{(2+1)\Omega} = (6A) \cdot \frac{1}{3} = 2A$$


$$\bar{i}_2 = \bar{i}_s - \bar{i}_1 = 6 - 2 = 4A$$

Also, $\bar{i}_2 = \bar{i}_s \cdot \frac{2}{2+1} = 6 \cdot \frac{2}{3} = 4A$ as before.

Cp. 4. Techniques of Circuit Analysis:

1-) Node - Voltage Method:


Suppose we have the following circuit:

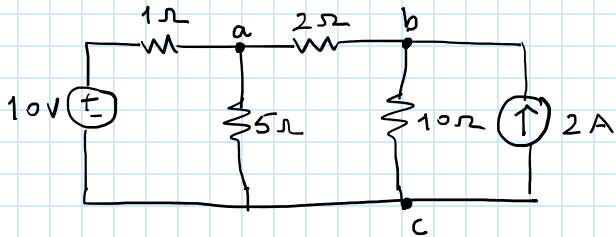

Step 1: Simplify the circuit.


Step 2:

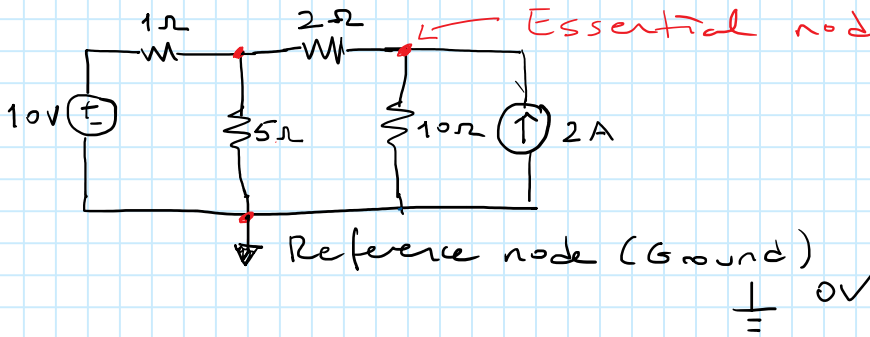Select one of the nodes as a reference node.



Step 3:

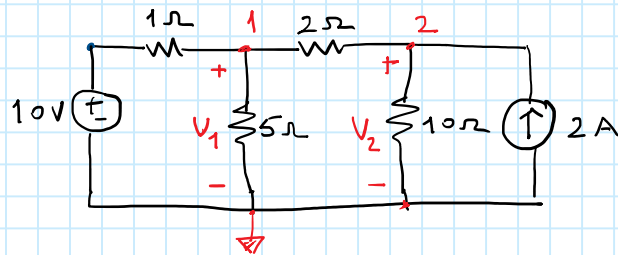Define node voltages w.r.t the reference node.




Step 4:

Generate node - voltage equations by:

P10

Tuesday, March 14, 2023 12:47 PM

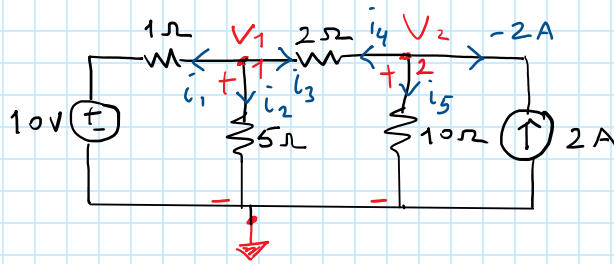Writing the node equations (KCL) for each node employing the leaving current convention.



KCL at node 1 gives:

$$i_1 + i_2 + i_3 = 0$$

$$\frac{V_1 - 10}{1\Omega} + \frac{V_1}{5\Omega} + \frac{V_1 - V_2}{2\Omega} = 0 \quad (1)$$

KCL at node 2 gives: (2)

$$\frac{V_2 - V_1}{2} + \frac{V_2}{10} - 2A = 0$$

Equations (1) and (2) can be solved simultaneously

Let us re-write (1)

$$\frac{V_1}{1} + \frac{V_1}{5} + \frac{V_1}{2} - \frac{V_2}{2} = 10$$

(10) (2) (5) (5)

$$10V_1 + 2V_1 + 5V_1 - 5V_2 = 100$$

$$17V_1 - 5V_2 = 100 \quad (3)$$

Re-write (2) as

$$\frac{V_2}{2} - \frac{V_1}{2} + \frac{V_2}{10} = 2$$

(5) (5) (1)

$$5V_2 - 5V_1 + V_2 = 20$$

$$-5V_1 + 6V_2 = 20 \quad (4)$$

$$\begin{aligned} 6/17V_1 - 5V_2 &= 100 &\Rightarrow 102V_1 - 30V_2 &= 600 &\Rightarrow 77V_1 &= 700 \\ 5/-5V_1 + 6V_2 &= 20 &\Rightarrow -25V_1 + 30V_2 &= 100 && V_1 = 9.09 \text{ and } V_2 = 10.9 \end{aligned}$$


2-) Mesh-Current Method:

For example, consider the following circuit:

For mesh-current analysis, we write the KVL equations for each mesh, and solve the equations simultaneously.

Ex:

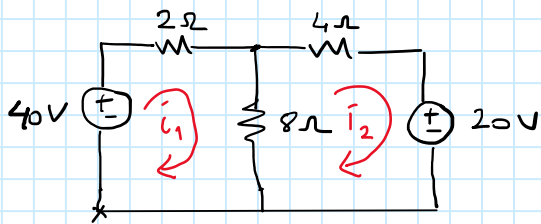Use the mesh-current method to determine the power associated with each voltage source.



Ans:

KVL for mesh 1:

$$-40 + 2i_1 + 8(i_1 - i_2) = 0 \quad (1)$$

KVL for mesh 2:

$$4i_2 + 20V + 8(i_2 - i_1) = 0 \quad (2)$$

Solve (1) and (2) simultaneously as

$$3/10i_1 - 8i_2 = 40 \quad (4)$$

$$2/-8i_1 + 12i_2 = -20 \quad (5)$$

$$30i_1 - 24i_2 = 120$$

$$+ \quad -16i_1 + 24i_2 = -40$$

$$14i_1 = 80$$

$$\Rightarrow i_1 = 5.7 \text{ A. end}$$

$$57 - 8i_2 = 40$$

$$\Rightarrow 8i_2 = 57 - 40 = 17$$

$$\Rightarrow i_2 = \frac{17}{8} = 2.125 \text{ A.}$$

To find the power generated by 40V source:

$$P_{40V} = (-40V)(i_1) = (-40)(5.7) = -228 \text{ W.}$$

$$P_{20V} = (20V)(i_2) = (20)(2.125) = 42.5 \text{ W. (This may damage the source.)}$$

Solve the following questions. (The answers should be shown in the video recordings.)

1-) For the circuit in Fig.2, if the power delivered by the source is 20 mW, find R and V_s .


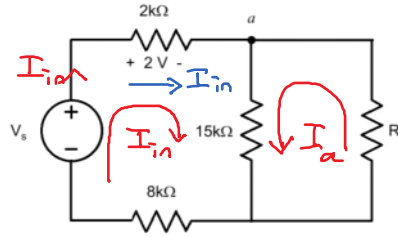


Figure 2: Circuit for question 2.



2-) Find i and R_{eq} if $V_{ab} = 40V$

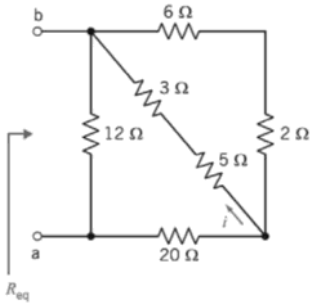

HW 3

Thévenin and Norton Equivalents:

Consider the following circuit:

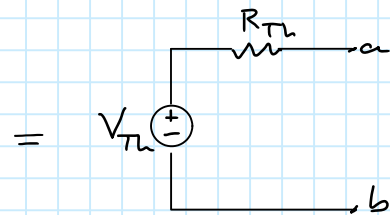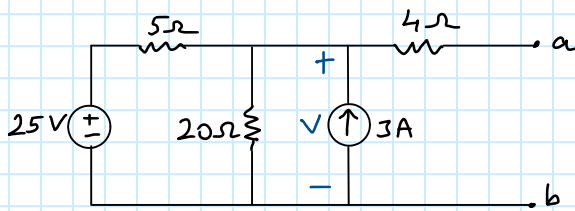

Thévenin Equivalent Circuit.

- If we connect another circuit to the given circuit at points a and b, this other circuit sees no difference if it is connected to Thévenin equivalent circuit.


V_{Th} = Open circuit voltage btw. the terminals a and b, and we short circuit a and b, and find the current btw a and b (I_{sc}).

$$R_{Th} = \frac{V_{Th}}{I_{sc}}$$

P13

Thursday, March 16, 2023 9:44 AM

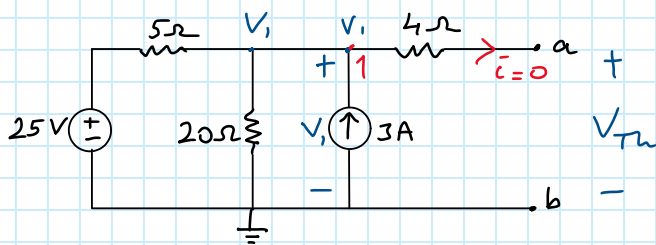For the given circuit; using the node-voltage method:



The current passing through the 4Ω resistor is zero.

$$V = i \cdot R = 0$$

$$V_1 - V_{Th} = 0$$

$$\Rightarrow V_1 = V_{Th}$$


KCL at node 1:

$$\frac{V_1 - 25}{5} + \frac{V_1}{20} - 3 = 0$$

$$\Rightarrow V_1 = 32 \text{ V.}$$

$$V_{Th} = 32 \text{ V.}$$

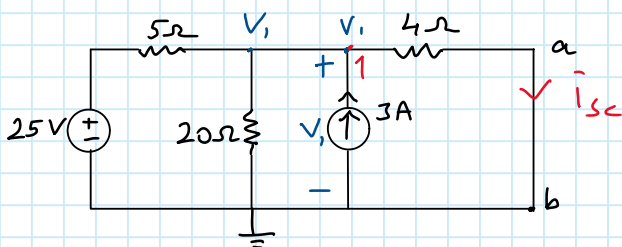- In order to find R_{Th} , we short circuit points a and b, and find i_{sc} .



KCL at node 1:

$$\frac{V_1 - 25}{5} + \frac{V_1}{20} - 3 + i_{sc} = 0 \quad (1)$$

Also, V_1 is the voltage across the 4Ω resistor.

$$\Rightarrow V_1 = 4 i_{sc} \quad (2) \text{ (Ohm's law across the 4Ω resistor)}$$

Thus, (1) and (2) can be solved simultaneously and

$$\frac{V_1 - 25}{5} + \frac{V_1}{20} + \frac{V_1}{4} = \frac{3}{1}$$

(4) (1) (5) (20)

$$4V_1 - 100 + V_1 + 5V_1 = 60$$


$$10V_1 = 160$$

$$\Rightarrow V_1 = 16 \text{ V.}$$

$$\text{and } i_{sc} = \frac{V_1}{4} = \frac{16}{4} = 4 \text{ A and}$$

$$R_{Th} = \frac{V_{Th}}{i_{sc}} = \frac{32}{4} = 8 \Omega.$$

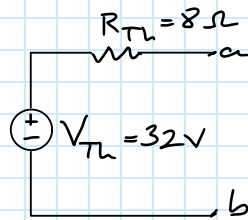Thus, the Thévenin equivalent circuit is:




In order to obtain the "Norton Equivalent Circuit", we can make "source transformation", where

$$R_{Th} \Big|_{\text{Thévenin}} = R_{Th} \Big|_{\text{Norton}}$$

The current source of Norton circuit is the short circuit current, that is

$$i_{sc} = \frac{V_{Th}}{R_{Th}} = \frac{32}{8} = 4A$$

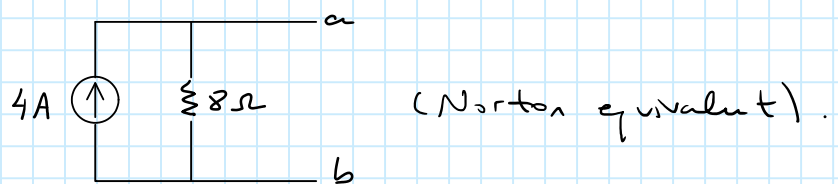Then, for this example, the Norton equivalent circuit is




Alternative technique to find Thévenin equivalent resistance:

If there are only independent sources, to find the Thévenin equivalent resistance:


- Short circuit voltage sources and
 - Open circuit current sources.
- } Deactivating the indep sources
- Then, evaluate the resistance R_{Th} w.r.t a and b.

Ex:

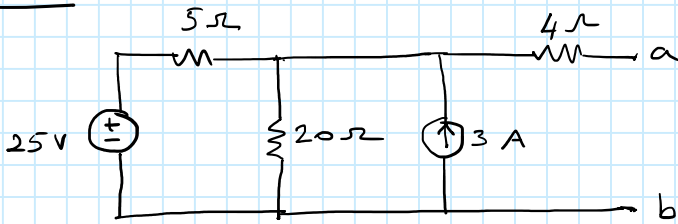

Find $R_{Th} = ?$ w.r.t points a and b.

Ans:

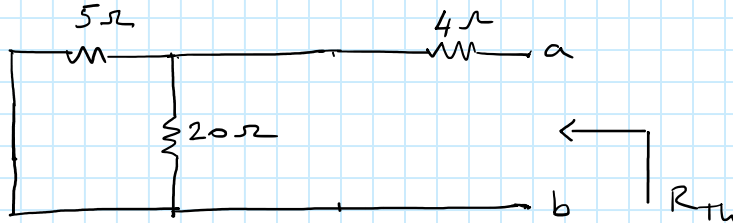

$$\begin{aligned} \Rightarrow R_{Th} &= 4 + (5 \parallel 20) \\ &= 4 + \frac{20 \cdot 5}{20 + 5} = 4 + \frac{20 \cdot 5}{25} \\ &= 4 + 4 = 8 \Omega. \end{aligned}$$


Another alternative technique to find The Thevenin resistance:

If the circuit contains dependent sources:

- First, deactivate all indep. sources
- Apply a test voltage " V_T " btw. the terminals a and b.
- $R_{Th} = \frac{V_T}{i_T}$, where i_T is the current passing through V_T .


Ex:

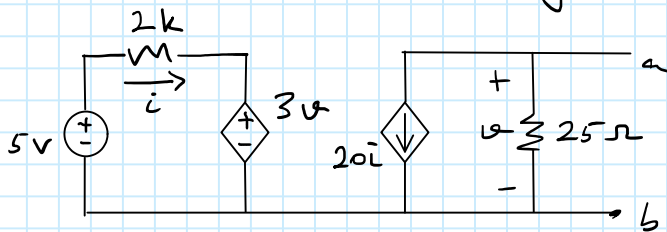Find the Thevenin resistance R_{Th} for the circuit below using the method that was just described.




Ans:

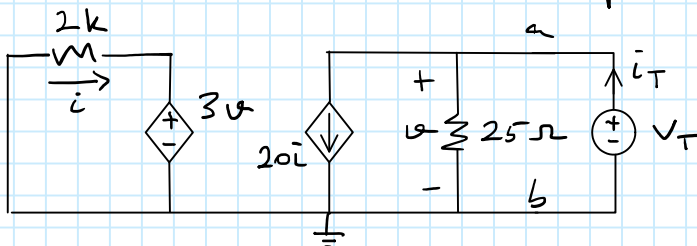- First, we de-activate all indep. sources:



- Apply the test voltage V_T

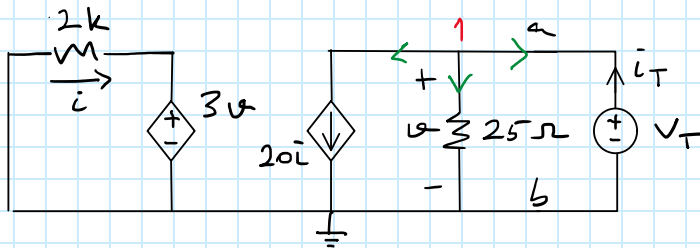- We need to find $\frac{V_T}{\bar{i}_T} = R_{Th}$. Let us use the node-voltage method:



KCL at node 1:

$$20\bar{i} + \frac{V}{25} = \bar{i}_T \quad (1)$$

where $\bar{i} = \frac{-3V}{2k} = \frac{-3V_T}{2000}$ (since $V = V_T$)

Then,

$$20 \cdot \left(\frac{-3V_T}{2000} \right) + \frac{V_T}{25} = \bar{i}_T \quad (2)$$

Solve equation (2) for $\frac{V_T}{\bar{i}_T}$.

$$\frac{-3V_T}{100} + \frac{V_T}{25} = \bar{i}_T$$

(1) (4)

$$-3V_T + 4V_T = 100\bar{i}_T$$


$$V_T = 100\bar{i}_T$$

$$\Rightarrow R_{Th} = \frac{V_T}{\bar{i}_T} = 100\Omega.$$

Prefix	Value
T (tera)	10^{12}
G (giga)	10^9
M (mega)	10^6
k (kilo)	10^3
c (centi)	10^{-2}
m (milli)	10^{-3}
μ (micro)	10^{-6}
n (nano)	10^{-9}
p (pico)	10^{-12}
f (femto)	10^{-15}

Maximum Power Transfer:

Consider the following circuit:

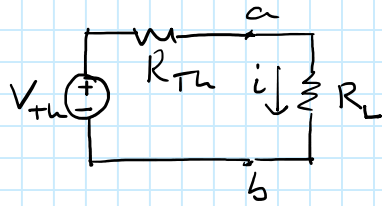

— The power consumed by the resistor R_L is:

$$P_{R_L} = i^2 \cdot R_L \text{ (W)}$$

— We want to find a value for R_L such that P_{R_L} is maximum. This is called "maximum power transfer".

— The power consumed by R_L , P_{R_L} , is a function of R_L .

$$\Rightarrow P_{R_L}(R_L) = i^2 R_L = \left(\frac{V_{Th}}{R_{Th} + R_L} \right)^2 \cdot R_L$$

To find the max. $P_{R_L}(R_L)$

$$\frac{\downarrow P_{R_L}(R_L)}{\downarrow R_L} = 0.$$

$$2 \left(\frac{V_{Th}}{R_{Th} + R_L} \right) \cdot \left[\frac{-V_{Th}}{(R_{Th} + R_L)^2} \right] R_L + \left(\frac{V_{Th}}{R_{Th} + R_L} \right)^2 = 0$$

Re-arrange the equation,

$$2 \left(\frac{V_{Th}}{R_{Th} + R_L} \right) \cdot \frac{1}{(R_{Th} + R_L)} \cdot R_L = \left(\frac{V_{Th}}{R_{Th} + R_L} \right)^2$$


$$2R_L = R_{Th} + R_L$$

$$\Rightarrow \boxed{R_L = R_{Th}} \text{ (Condition for max. power transfer).}$$

$$P_{RL} = \left(\frac{V_{Th}}{R_{Th} + R_L} \right)^2 \cdot R_L = \frac{V_{Th}^2}{4R_L} \cdot R_L = \frac{V_{Th}^2}{4} \text{ (W)} \quad (\text{Power consumed by } R_L \text{ when } R_L = R_{Th})$$

Ex:


For the given circuit below:

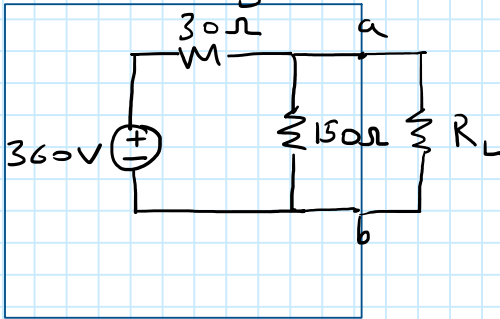


- i) Find R_L for max. power transfer
- ii) Find $P_{RL} |_{max}$

First, find the Thevenin equivalent circuit for the circuit inside the blue box.


Using the source transformation

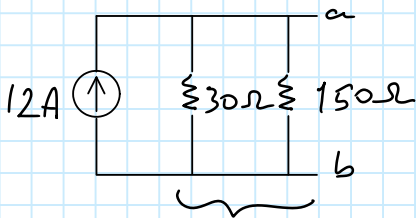
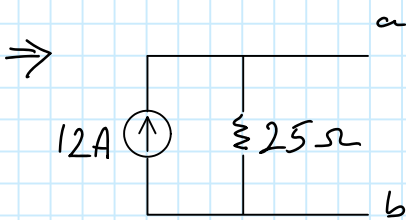
$$(30 \parallel 150) = \frac{150 \times 30}{150 + 30} = \frac{150 \times 30}{180} = 25 \Omega$$



Source Transfr. →

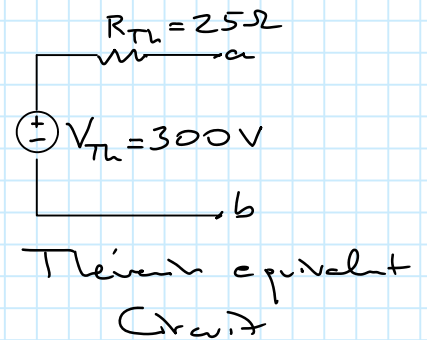

Thus, for max. power transfer $R_L = R_{Th} = 25 \Omega$.

and
$$P_{RL} = \frac{V_{Th}^2}{4R_L} = \frac{300^2}{4 \times 25} = \frac{300 \cdot 300}{100} = 900 \text{ W.}$$

↓ HW #4 ↓


Complex Numbers

Let us first consider the real numbers


$$\mathbb{R} = \{\dots, -1, 0, 1, \dots\}$$

Addition & Subtraction:

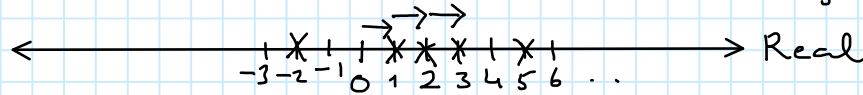
$$\left. \begin{matrix} 1+2=3 \\ 5-3=2 \end{matrix} \right\} \text{Translation (motion)}$$



Consider $3-5=-2$

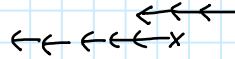

Multiplication & Division

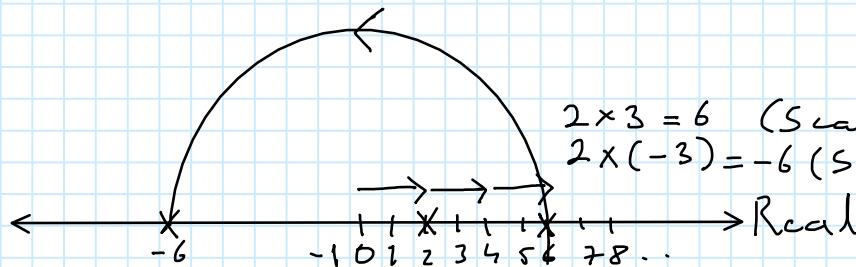


$$\begin{matrix} 2 \times 3 = 6 \text{ (Scaling)} \\ 2 \times (-3) = -6 \text{ (Scaling + Rotate)} \end{matrix}$$

⇒ Multiplication is scaling + rotating (if - numbers)

Also, division is similar It is a (Down scaling + rotation)

Can we rotate a quarter of a turn (90°)?

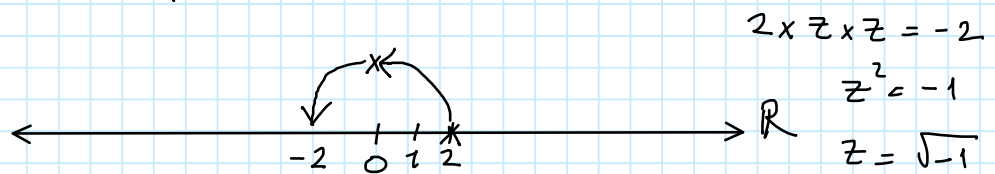

$$\begin{matrix} z \times z = -2 \\ z^2 = -1 \\ z = \sqrt{-1} \end{matrix}$$

- Therefore, multiplying any real number by $z = \sqrt{-1}$ rotates the number by a $\frac{1}{4}$ of a turn.

We call this number "Complex number" and use the following notation

$$z = i = \sqrt{-1}$$

or

$$z = j = \sqrt{-1}$$


P20

Friday, March 24, 2023 10:31 AM


$\Rightarrow z = j = \sqrt{-1}$, where is this number on the number line

$$1 \times \sqrt{-1} = \sqrt{-1} = j$$

$$2 \times \sqrt{-1} = 2\sqrt{-1} = 2j$$

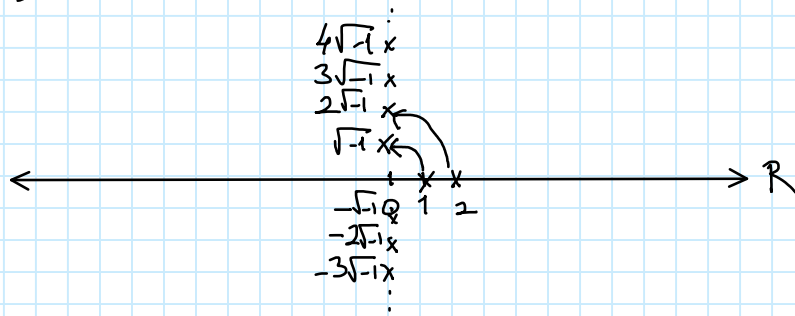

\Rightarrow We can draw a vertical line.

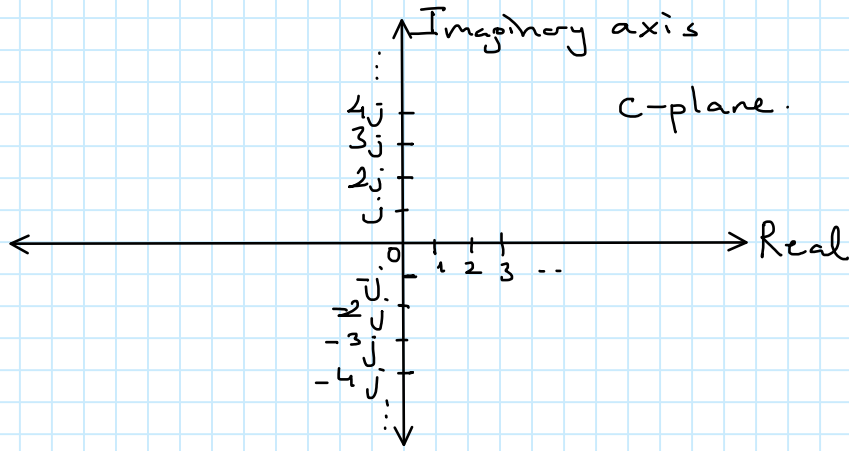

- This plane is called "complex plane" (C-plane) and any number on this plane is called a "complex number"

Ex


Suppose $z = -3$, what should be done to rotate this number a $\frac{1}{4}$ of a turn cw and ccw?

Ans


$$z \times (j) = (-3) \times (j) = -3j \text{ (ccw)}$$

$$z \times (-j) = (-3) \times (-j)$$

$$= 3j \text{ (cw)}$$

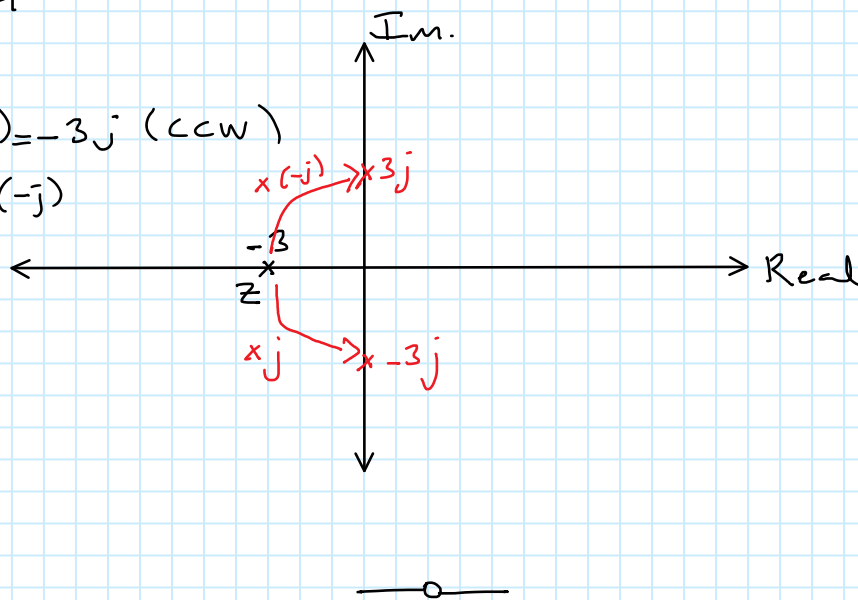

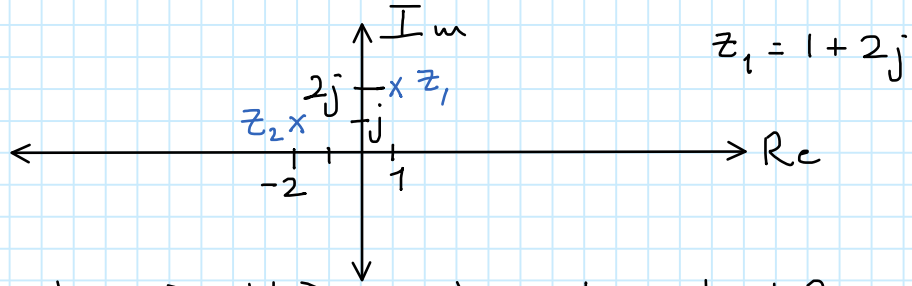Writing a Complex Number in terms of its Real and imaginary parts (components):




$z_2 = z_1 \times j = ?$ where is this number located?

$j = \sqrt{-1}$
 $j^2 = -1$

Ans

Algebraic solution: $z_1 \times j = (1 + 2j) \times (j) = j + 2j^2 = -2 + j$

Graphical solution:

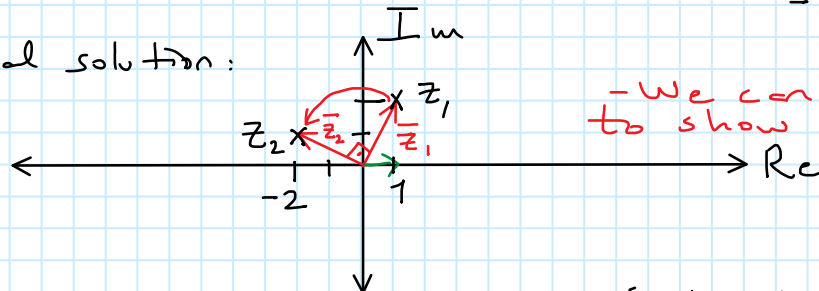

⇒ Up to this point, we have the following notations:

$z = a + jb$ (component notation)
 ↳ Real ↳ Imaginary.


$\vec{z} = \vec{a} + j\vec{b}$ (vector notation, used in geometric analysis)

What if we multiply z_1 by $2j$.

$z_3 = z_1 \times (2j) = ?$

Algebraic Sol:

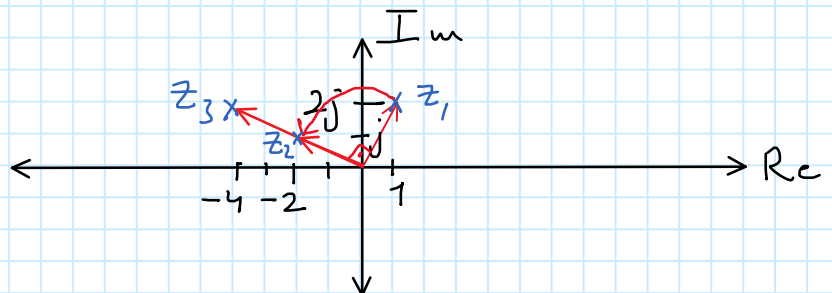$(1 + 2j) \cdot (2j)$
 $= 2j + 4j^2$
 $z_3 = -4 + 2j$




⇒ $z_1 \times (2j) =$ (rotation + scaling by 2.)


Power of a Complex Number:

$$j^n = ?$$


$1 \times j = j$	(j^1)
$j \times j = -1$	(j^2)
$-1 \times j = -j$	(j^3)
$-j \times j = 1$	(j^4)
$1 \times j = j$	(j^5)

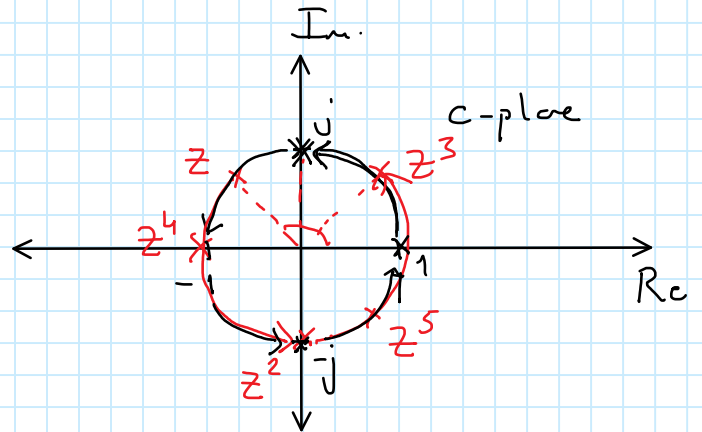

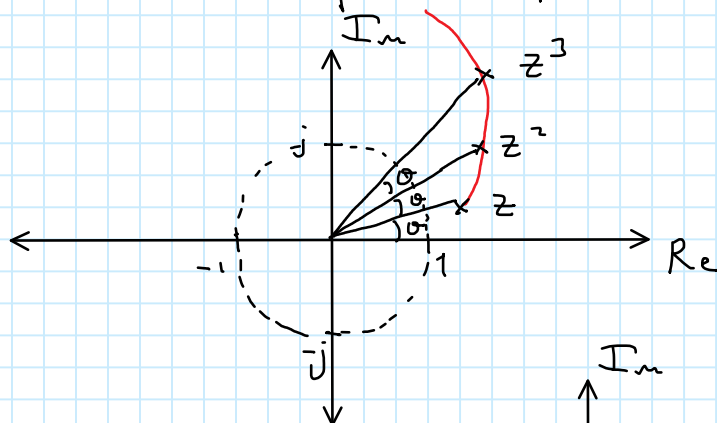- ⇒ Taking the power of (j) rotates ccw on the unit circle
- Taking the power of any complex number z which is on the unit circle rotates the number ccw by the same angle that z makes with the real axis
- What if z is outside the unit circle? Then, what happens when we take the power of z




- If z is inside the unit circle.

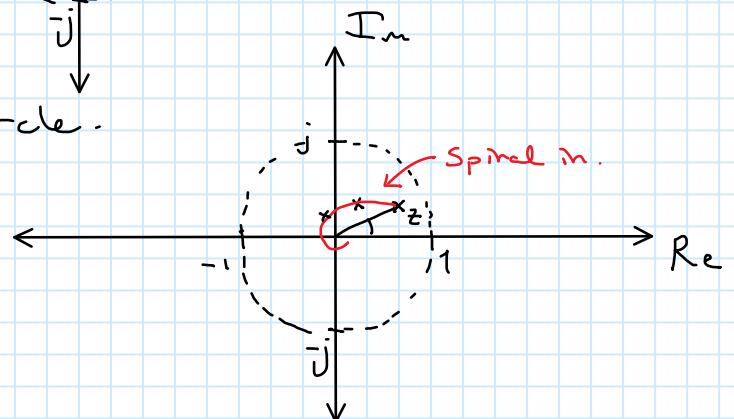


Complex Exponential:

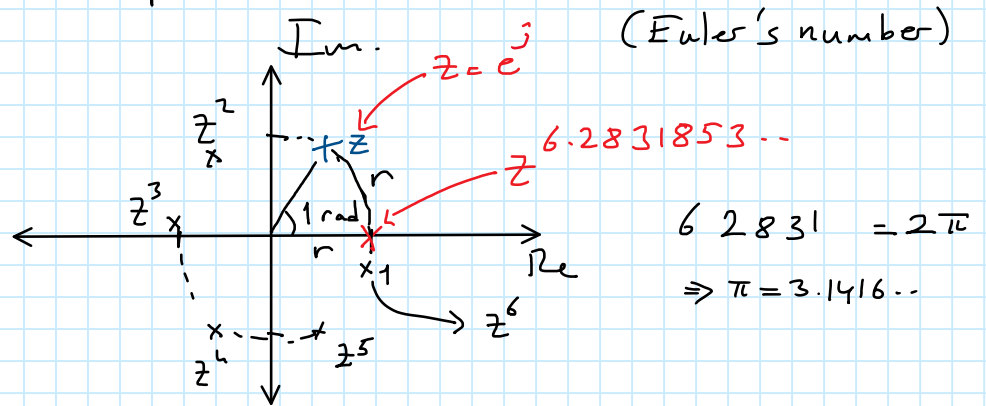
$z = e^{j\theta}$ (Complex exponential), $e = 2.71828\dots$



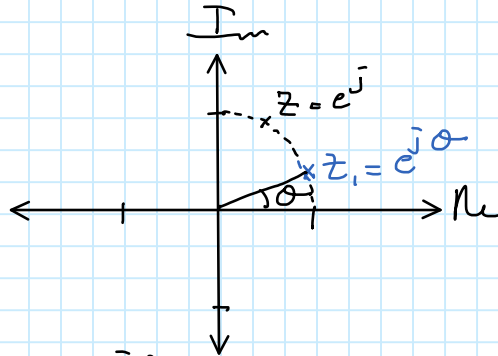— Also, $z_1 = e^{j\theta}$ is on the unit circle with angle θ in radians



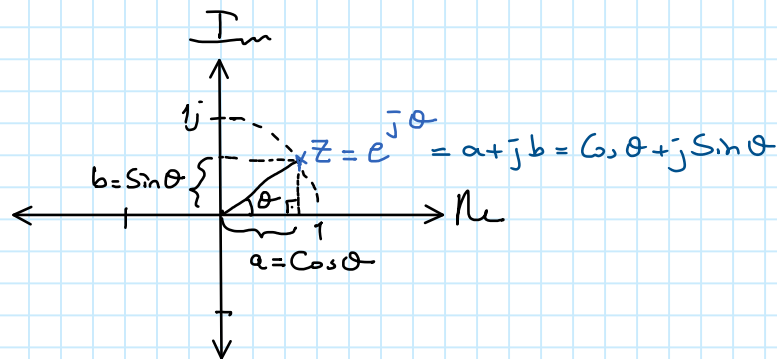
Let us observe $z = e^{j\theta}$ closely:




$\Rightarrow z = e^{j\theta} = a + jb = \cos \theta + j \sin \theta$

$\underbrace{\hspace{2em}}$ Exponential notation $\underbrace{\hspace{2em}}$ Rectangular notation

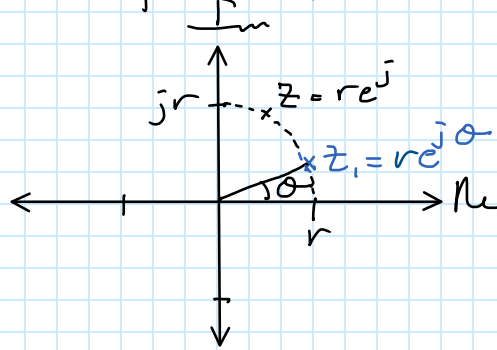Let us analyze the complex exponential $z = re^{j\theta}$ where r is a constant.




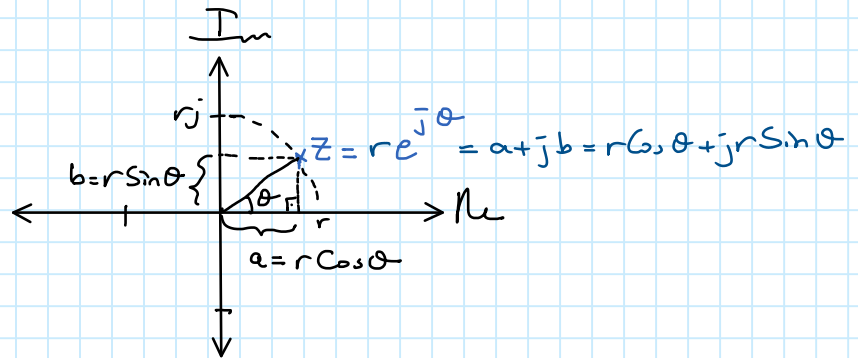- $z_1 = re^{j\theta}$ is on the circle whose radius is r .
- Also, let us observe $z = re^{j\theta}$ closely:



$$\Rightarrow \underbrace{z = re^{j\theta}}_{\text{Exponential notation}} = \underbrace{a + jb}_{\text{Rectangular notation}} = r \cos \theta + jr \sin \theta \text{ (Euler's formula.)}$$

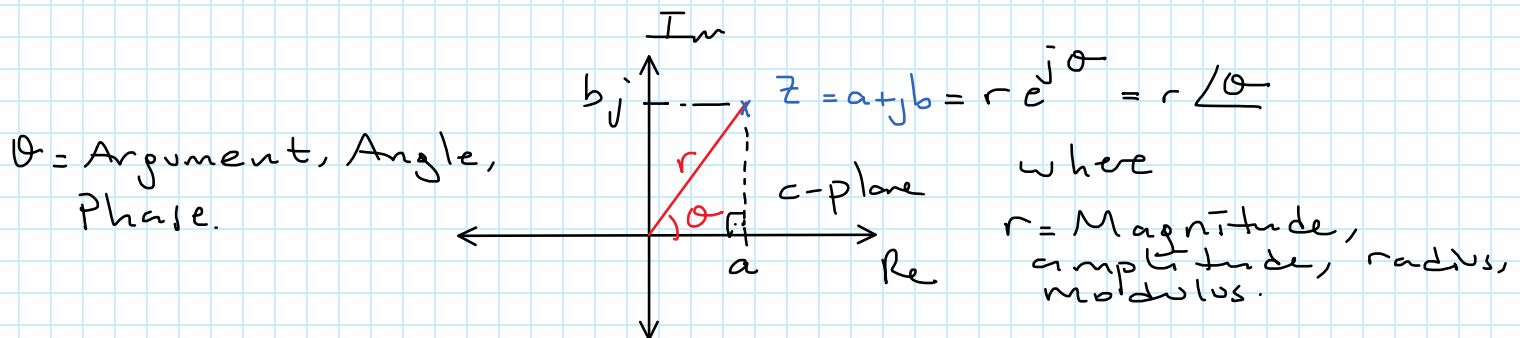Until now: The formats for complex numbers.
 $z = a + jb = \text{rectangular}$, $\bar{z} = \text{vectorial}$,
 3rd format. exponential form (Polar form)



Rectangular to Polar Form Transformation:

$$r^2 = a^2 + b^2, \quad \theta = \tan^{-1} \frac{b}{a}$$

Polar to Rectangular Transformation:

$$a = r \cos \theta$$

$$b = r \sin \theta$$

Ex:

Given $z = 3 + j4$, find its polar representation.

Ans:


$$a = 3, \quad b = 4$$

$$\Rightarrow r = \sqrt{a^2 + b^2} = \sqrt{3^2 + 4^2} = \sqrt{25} = 5.$$

$$\text{and } \theta = \tan^{-1} \frac{b}{a} = \tan^{-1} \frac{4}{3} = 0.9273 \text{ rad.} = 53.13^\circ.$$

$$\Rightarrow z = 5e^{j0.9273}$$

$$= 5e^{j53^\circ} = 5 \angle 53^\circ$$

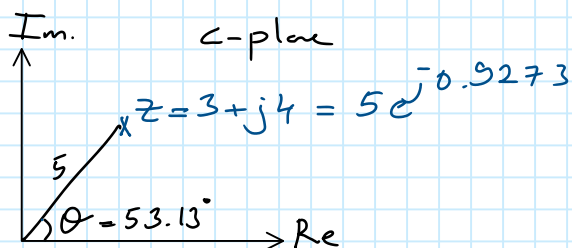

Complex Algebra:Addition & Subtraction of Complex Numbers:

- Using rectangular notation is easier
- Add or subtract the Real and imaginary parts among themselves.

Ex:

$$z_1 = 3 + 4j$$

$$z_2 = 2 - 2j$$

a.) $z_1 + z_2 = ?$

b.) $z_1 - z_2 = ?$

Ans

$$\begin{aligned} z_1 + z_2 &= (3 + 4j) + (2 - 2j) \\ &= (3 + 2) + (4j - 2j) \\ &= 5 + 2j \end{aligned}$$

$$\begin{aligned} z_1 - z_2 &= (3 + 4j) - (2 - 2j) \\ &= (3 + 4j) - 2 + 2j \\ &= (3 - 2) + (4j + 2j) \\ &= 1 + 6j \end{aligned}$$

Multiplication & Division

- Polar form is easier.
- Multiply the magnitudes and sum the angles.

Ex

$$z_1 = 3 + 4j, \quad z_2 = 8 - 6j$$

a.) $z_1 \cdot z_2 = ?$

b.) $\frac{z_2}{z_1} = ?$

Ans

$$\begin{aligned} z_1 \cdot z_2 &= (3 + 4j) \cdot (8 - 6j) \\ &= 24 - 18j + 32j - 24j^2 \\ &= 24 - 18j + 32j + 24 \\ &= 48 + 14j \end{aligned}$$

Alternatively, converting these complex numbers into polar form:


$$z_1 = 3 + 4j = 5e^{j0.93}$$

$$z_2 = 8 - 6j = \sqrt{8^2 + (-6)^2} e^{j \tan^{-1} \left(\frac{-6}{8} \right)} = 10 e^{-j0.64}$$

$$\Rightarrow z_1 \cdot z_2 = 5e^{j0.93} \cdot 10e^{-j0.64} = 50e^{j(0.93-0.64)} = 50e^{j0.29}$$

Using the Euler's theorem: $z_1 \cdot z_2 = 50 \cos 0.29 + j50 \sin 0.29$
 $= 48 + j14$. which is the same as before.
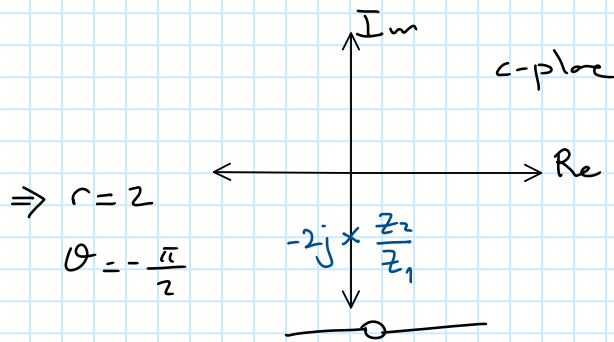
$$\frac{z_2}{z_1} = \frac{10e^{-j0.64}}{5e^{j0.93}} = 2 \cdot e^{-j0.64-j0.93} = 2e^{-j1.57} = 2e^{-j\frac{\pi}{2}} = -2j$$



- Why do we need complex numbers?

↓ HW #5 ↓

Ans: Mathematical Computations with sin or cos functions are difficult. To make them easier, we use complex numbers.

Ex:

Given $f_1(t) = \sin(4\pi t + \frac{\pi}{2})$, $f_2(t) = \sin(4\pi t + \frac{3\pi}{2})$

$$f_1(t) \times f_2(t) = ?$$

Ans:

This computation is not very easy.

First, we need the trigonometric identity

$$\sin a \times \sin b = -\frac{1}{2} [\cos(a+b) - \cos(a-b)]$$

Using this identity, we get

$$\begin{aligned}\sin\left(4\pi t + \frac{\pi}{2}\right) \times \sin\left(4\pi t + \frac{3\pi}{2}\right) &= \frac{-1}{2} \left[\cos(8\pi t + 2\pi) - \cos(-\pi) \right] \\ &= \frac{-1}{2} \left[\cos(8\pi t) - (-1) \right] \\ &= -0.5 \cos(8\pi t) - 0.5\end{aligned}$$

Similarly, if we wanted to find $\frac{f_1(t)}{f_2(t)}$, or any other algebraic expression, it is not so easy to find the solution.

The sinusoidal Function:

$$V(t) = V_m \cos(\underbrace{\omega t + \phi}_{\theta = \text{Angle (rad)}}$$

$t = \text{time,}$


$V_m = \text{Amplitude,}$

$\omega = 2\pi f = \text{Radian freq.}$

$\phi = \text{Phase (rad.),}$


Amplitude:

$$V(t) = V_m \cos(\omega t + \phi)$$

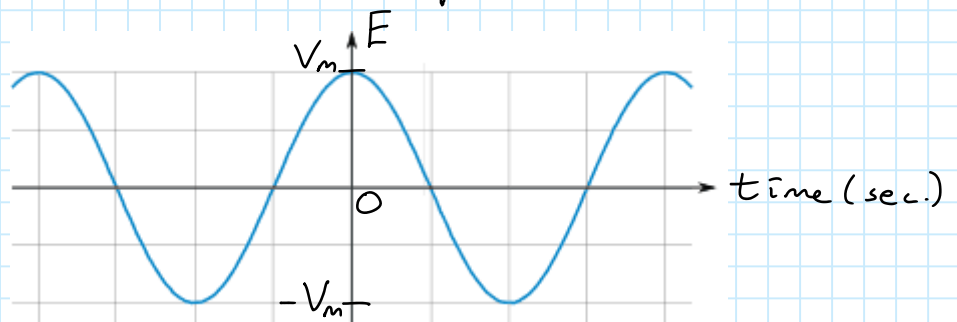

Radian Frequency (ω):

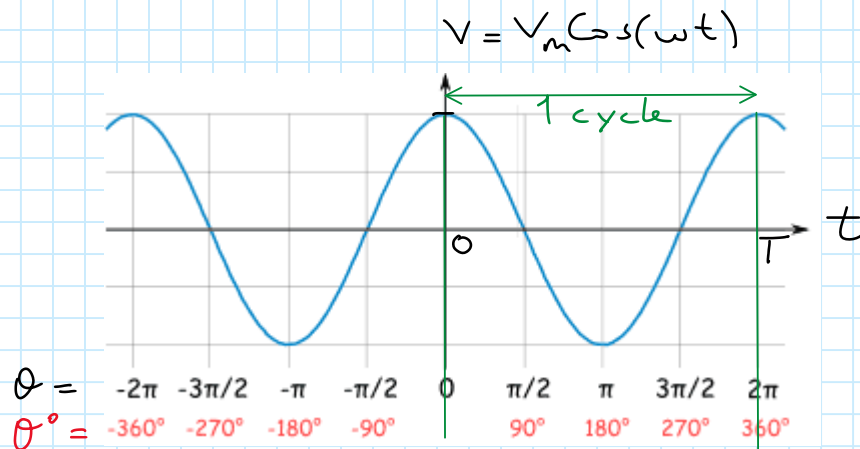Let us consider $\phi = 0$ for simplicity, then we have




When $t=0$, $V=V_m$, $\theta=0$

When $t=T$, $V=V_m$, $\theta=2\pi$

$$\Rightarrow \omega T = 2\pi$$

$$\omega = \frac{2\pi}{T} \quad \left(\frac{\text{rad}}{\text{sec}} \right)$$

where

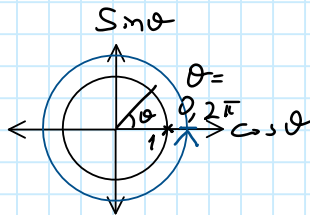

T = Time for 1 turn of θ or time for 1 cycle

Then, ω = number of 2π radians in 1 sec.

$\omega = 2\pi$ means there is 2π rad in 1 sec.

$\omega = 4\pi$ means there are $2 \times 2\pi$ rad. (2 turns around the unit circle)

$\omega = 6\pi$ means there are $3 \times 2\pi$ rad (3 turns " " " ")
 f ;

$$\Rightarrow \omega = 2\pi f \quad \text{where } f = \text{number of turns in 1 sec.}$$

and $T = \frac{1}{f}$.

Ex:

$V(t) = \cos(2000\pi t)$ is given. Find the Hertz frequency f ?
Also find T , and draw $v(t)$.


Ans:

$$\omega = 2000\pi \frac{\text{rad}}{\text{sec}}$$


$$T = \frac{1}{f} = \frac{1}{1000} = 1 \times 10^{-3} = 1 \text{ ms.}$$

$$2000\pi = 2\pi f$$
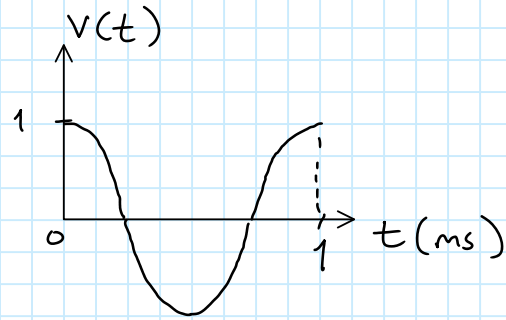
$$\Rightarrow f = 1000 \text{ Hz} = 1 \text{ kHz.}$$



Phase (ϕ):

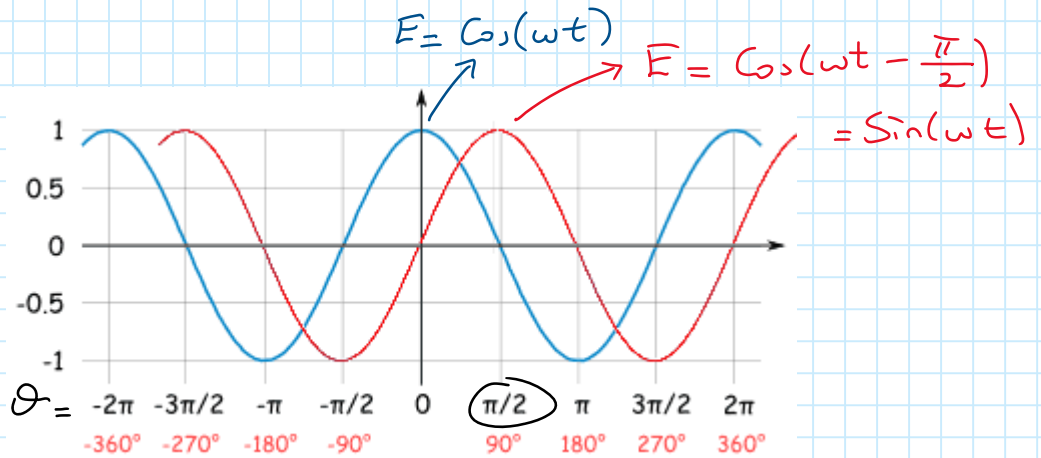

Thus, the phase ϕ makes the cos function shift right or left depending on its sign. "+" shifts left and "-" shifts right.





- Sinusoidal State State Response -

Sinusoidal means sine or cosine functions.

Steady state means that the circuit's initial response has finished, and everything has been settled.

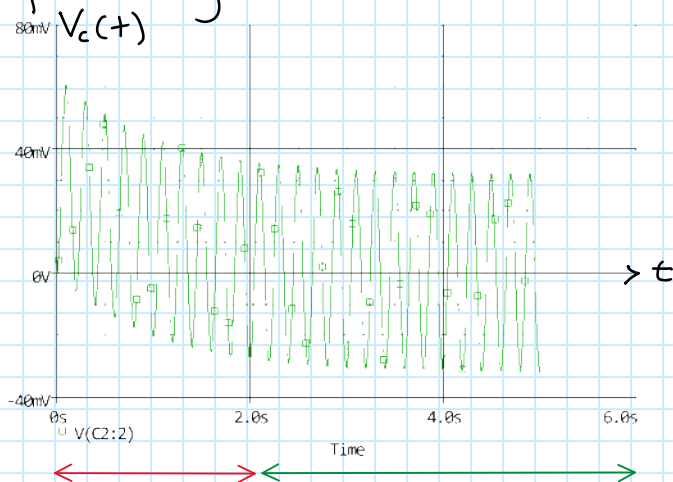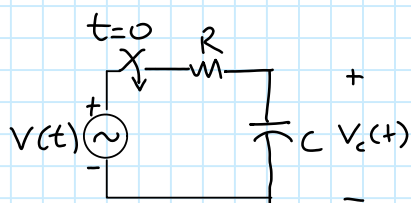For example, consider the following circuit



Transient Response

Steady State Response

Transient Response: Time interval for all capacitor and/or inductors to charge or discharge.

Steady State: The time after everything is settled down.

To find the steady state response of a given circuit with sinusoidal sources, we use "Phasors" as follows.

$$V(t) = V_m \cos(\omega t + \phi) \xrightarrow{\text{Phasor Transform}} \bar{V} = V_m e^{j\phi} \quad (\text{Phasor})$$

(Time expression)

- The major difference in phasor expression is that we exclude the " ωt " term. Thus, the circuit must have the same frequency. This implies linearity.

$$\bar{V} = V_m e^{j\phi} \xrightarrow[\text{Inverse Phasor Transform}]{} V(t) = \text{Re}[\bar{V} e^{j\omega t}]$$

If we use the "sine" function as the reference, then

$$v(t) = V_m \sin(\omega t + \phi) \xrightarrow{\text{Phasor Transform}} \bar{V} = V_m e^{j\phi} \text{ (Phasor)}$$

(Time expression)

$$\bar{V} = V_m e^{j\phi} \xrightarrow{\text{Inverse Phasor Transform}} v(t) = \text{Im}[\bar{V} e^{j\omega t}]$$

Ex:

Given $f_1(t) = \sin(4\pi t + \frac{\pi}{2})$, $f_2(t) = \sin(4\pi t + \frac{3\pi}{2})$
 $f_1(t) \times f_2(t) = ?$ using phasors.

Ans:

When we multiply $f_1(t)$ by $f_2(t)$, the frequency is doubled. In this case $\omega t = 4\pi$, however $\omega t = 8\pi$ for $f_1(t) \cdot f_2(t)$. Thus, this is a non-linear system and can not be solved by phasors.

Ex:

Given $f_1(t) = \sin(4\pi t + \frac{\pi}{2})$, $f_2(t) = \sin(4\pi t)$
 $y_1(t) = f_1(t) + f_2(t) = ?$ using phasors.

Addition of sinusoids is a linear operation, thus we can use phasors.

Ans: $\bar{f}_1 = 1 \cdot e^{j\frac{\pi}{2}} = e^{j\frac{\pi}{2}} = \cos\frac{\pi}{2} + j\sin\frac{\pi}{2} = j$

$$\bar{f}_2 = 1 \cdot e^{j0} = 1$$

$$\Rightarrow \bar{y}_1 = \bar{f}_1 + \bar{f}_2 = 1 + j = \sqrt{2} e^{j\tan^{-1}1} = \sqrt{2} e^{j0.78} = \sqrt{2} / 0.78 = \sqrt{2} / 45^\circ$$

$$y_1(t) = \text{Im}[\bar{y}_1 e^{j4\pi t}] = \text{Im}[\sqrt{2} e^{j0.78} \cdot e^{j4\pi t}]$$

$$= \sqrt{2} \sin(4\pi t + 0.78)$$

Ex:

$$\sin(2000\pi t) + \cos(2000\pi t) = ?$$

Ans:

$$y(t) = \cos\left(2000\pi t - \frac{\pi}{2}\right) + \cos(2000\pi t)$$

In phasor domain,

$$\bar{y} = \underbrace{e^{-j\frac{\pi}{2}}}_{-j} + \underbrace{e^{j0}}_1 = 1 - j$$

Converting to a polar form

$$\bar{y} = \sqrt{2} e^{j\theta} = \sqrt{2} e^{-j0.78}$$

Then

$$y(t) = \operatorname{Re}[\bar{y} \cdot e^{j\omega t}] = \operatorname{Re}[\sqrt{2} e^{-j0.78} \cdot e^{j2000\pi t}]$$

$$= \sqrt{2} \cos(2000\pi t - 0.78)$$


- In circuit theory, all equations (Ohm's law, KVL, KCL) of circuits having sinusoidal sources are linear and can be solved by phasors.

↓ HW#6 ↓

- Sinusoidal Steady State Response -

- Passive Circuit Elements (R, L, C) in Frequency Domain -

1) V-I Relation for a Resistor:

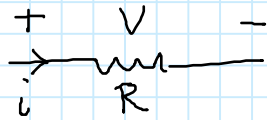

$$v = R [I_m \cos(\omega t + \phi)] \\ = R I_m \cos(\omega t + \phi) \text{ (V)}$$

$$\Rightarrow \bar{v} = R I_m e^{j\phi} = R \underbrace{I_m e^{j\phi}}_{\bar{I}}$$

or $\boxed{\bar{v} = R \bar{I}}$

Phasor domain

2) V-I Relation for an Inductor.

$$v = L \frac{di}{dt} \text{ assuming that } i = i(t) = I_m \cos(\omega t + \phi)$$

or

$$v = L (-\omega) I_m \sin(\omega t + \phi) \\ = -\omega L I_m \sin(\omega t + \phi)$$

or


$$v = -\omega L I_m \cos(\omega t + \phi - \frac{\pi}{2})$$

Thus,

$$\bar{v} = -\omega L I_m e^{j(\phi - \frac{\pi}{2})}$$

and
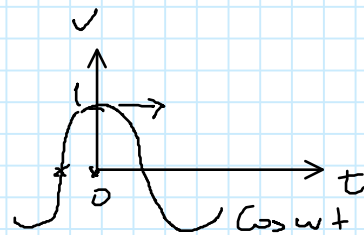
$$\bar{v} = -\omega L I_m e^{j\phi} \underbrace{e^{-j\frac{\pi}{2}}}_{-j} = j\omega L \underbrace{I_m e^{j\phi}}_{\bar{I}}$$



Thus,

$$\boxed{\bar{v} = j\omega L \bar{I}}$$

$$\Rightarrow v(t) = L \frac{di(t)}{dt} \xrightarrow{P} \bar{v} = j\omega L \bar{I}$$

$$\Rightarrow \frac{d}{dt} \xrightarrow{P} j\omega$$

- Kirchoff's Laws in Frequency Domain -

1-) KVL in Phasor domain:


$$\bar{V}_1 + \bar{V}_2 + \dots + \bar{V}_n = 0$$

2-) KCL in Phasor domain:

$$\bar{I}_1 + \bar{I}_2 + \dots + \bar{I}_n = 0$$


3-) Series and Parallel Connections:

a-) Series Connection

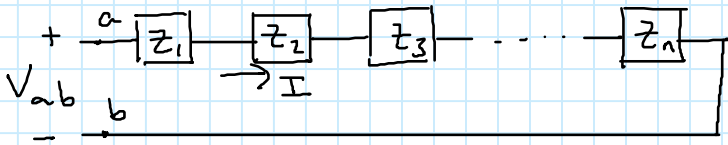

$$z_{ab} = \frac{\bar{V}_{ab}}{\bar{I}} = z_1 + z_2 + \dots + z_n$$

b-) Parallel Connection:

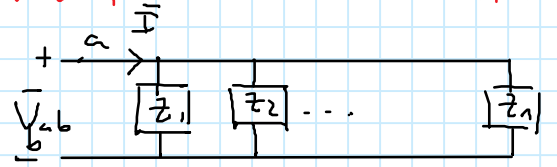

$$z_{ab} = \frac{\bar{V}_{ab}}{\bar{I}} \Rightarrow$$


$$\frac{1}{z_{ab}} = \frac{1}{z_1} + \frac{1}{z_2} + \dots + \frac{1}{z_n}$$

However,

$$Y_{ab} = \text{Admittance} = G + jB$$

$$Y_{ab} = Y_1 + Y_2 + \dots + Y_n$$


Ex:

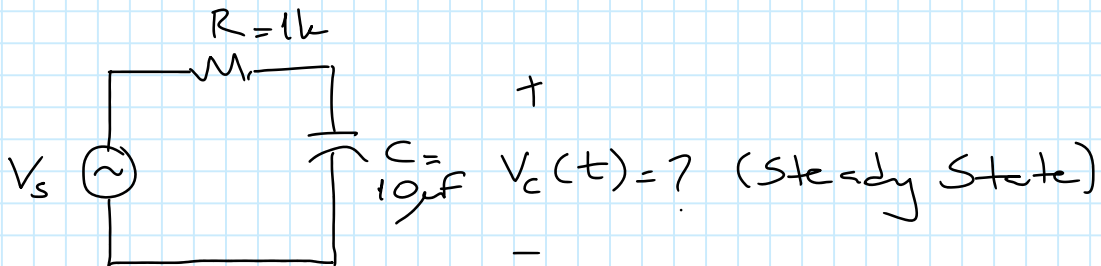


Given $V_s = 10 \cos(2000\pi t) \text{ V}$.

Ans:

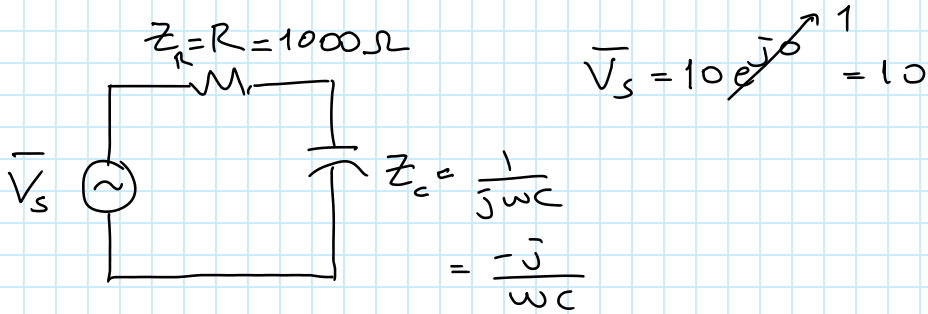Step 1: Transform the circuit into phasor domain



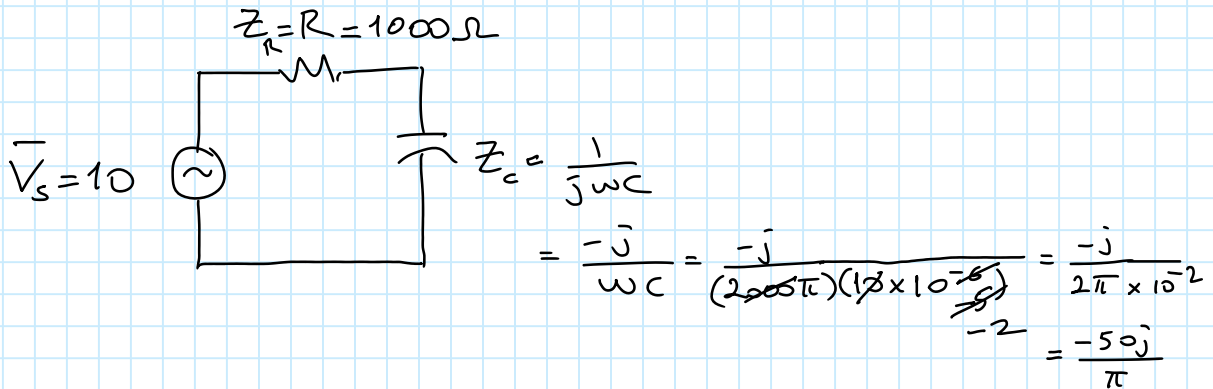Step 2: Use the circuit analysis techniques to solve the unknown voltage or current.



From the voltage division:

$$\bar{V}_c = \bar{V}_s \cdot \frac{Z_c}{Z_c + Z_R} = 10 \cdot \frac{-50j/\pi}{\frac{-50j}{\pi} + 1000} = 10 \cdot \frac{-50j/\pi}{1000\pi - 50j} =$$


$$\bar{V}_c = 10 \cdot \frac{-50j/\pi}{1000\pi - 50j} = 10 \cdot \frac{-j}{20\pi - j} =$$

$$= 10 \cdot \frac{-j}{60 - j} = \frac{1}{6} (-j) \approx 0.17 (-j)$$

$$\Rightarrow \bar{V}_c = 0.17 e^{-j\pi/2}$$

$$v_c(t) = \text{Re}[\bar{V}_c \cdot e^{j\omega t}] = 0.17 \cos(2000\pi t - \frac{\pi}{2}) \text{ V.}$$


Ex:

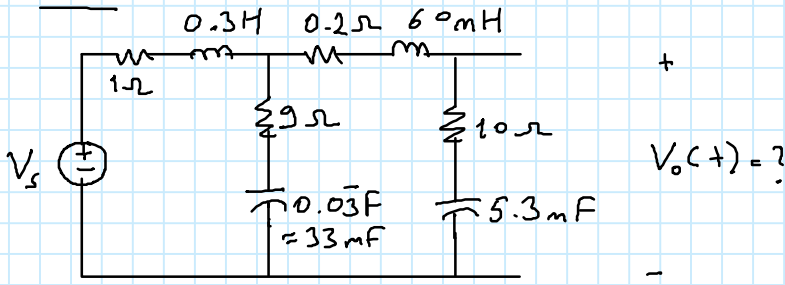

$$V_s = 40 \cos\left(\frac{10}{7}t\right) \text{ (V)}$$

Ans:

Phasor domain equivalent circuit is:

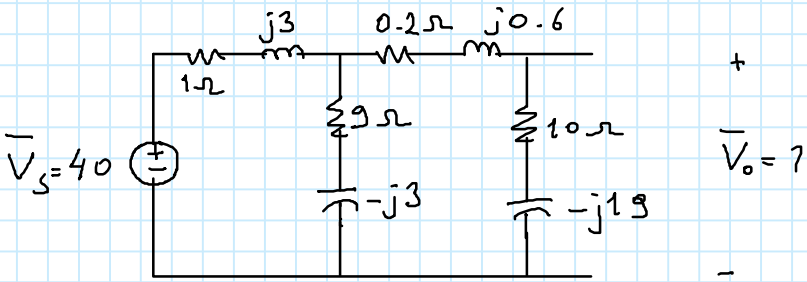


$$Z_{0.3H} = j\omega L = j(10)(0.3) = j3 (\Omega)$$

$$Z_{33mF} = \frac{-j}{\omega C} = \frac{-j}{10(0.03)} = -j3 (\Omega)$$


$$Z_{60mH} = j\omega L = j(10)(60 \times 10^{-3}) = j0.6 (\Omega)$$
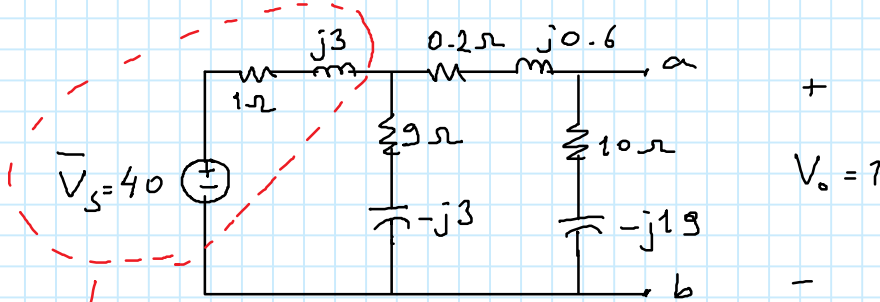
$$Z_{5.3mF} = \frac{-j}{\omega C} = \frac{-j}{(10)(5.3 \times 10^{-3})} = -j19 (\Omega)$$



Replace by its Norton equivalent $\Rightarrow \bar{I} = \frac{40}{1+j3} = \frac{40(1-j3)}{10} = 4 - j12 \text{ (A)}$

Then, we have

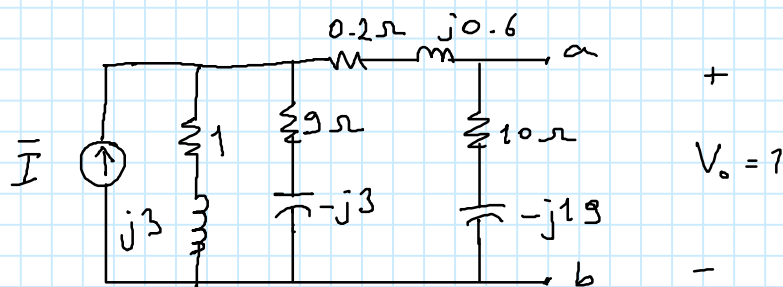


Parallel

$$z_1 = 1 + j3 \Omega \quad z_2 = 9 - j3 \Omega$$

$$\Rightarrow \bar{z}_1 || z_2 = z_t$$

$$\Rightarrow z_T = \frac{z_1 z_2}{z_1 + z_2} = \frac{(1+j3)(9-j3)}{10} = 1.8 + j2.4 \Omega$$


Now, we have:

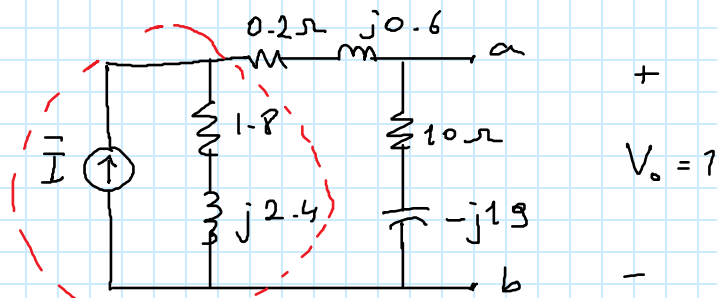

→ Transform to Thevenin equivalent

$$\bar{V}_{Th} = (4 - j12)(1.8 + j2.4) = 36 - j12 \text{ (V)}$$

Then,

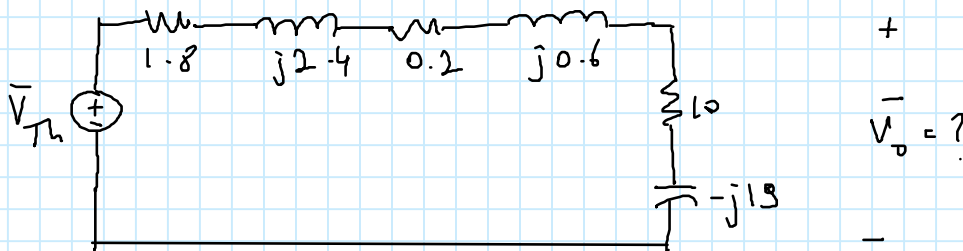


Using the voltage divider:

$$\begin{aligned} \bar{V}_o &= \bar{V}_{Th} \cdot \frac{(10 - j13)}{12 - j16} = 36 - j12 - j18.84 \text{ V} \\ &= 40.74 e^{j0.48} \text{ (V)} \end{aligned}$$

Time expression of \bar{V}_o :
 
$$\begin{aligned} v_o(t) &= \text{Re}[\bar{V}_o \cdot e^{j\omega t}] \\ &= 40.74 \cos(10t - 0.48) \text{ (V)} \end{aligned}$$




↓ HW 7 ↓

- Sinusoidal Steady State Power Calculations - (Chp. 10)

Instantaneous power = The power at any instant of time.

$p = v \cdot i$ for the circuit

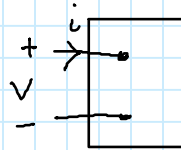

where

$v = V_m \cos(\omega t + \theta_v)$ and $i = I_m \cos(\omega t + \theta_i)$

- If we set our start time such that the system requires shift of both the voltage and current by " θ_i ", then:

$V = V_m \cos(\omega t + \theta_v - \theta_i)$ and $i = I_m \cos(\omega t + \theta_i - \theta_i)$
or $i = I_m \cos(\omega t)$

Then, instantaneous power becomes.

$p = v \cdot i = V_m \cos(\omega t + \theta_v - \theta_i) \cdot I_m \cos(\omega t)$ (w)

Then, using the identity,

$\cos A \cdot \cos B = \frac{1}{2} [\cos(A+B) + \cos(A-B)]$


$\Rightarrow p = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + \frac{V_m I_m}{2} \cos(2\omega t + \theta_v - \theta_i)$

Now, we use the identity: $\cos(A+B) = \cos A \cos B - \sin A \sin B$

\Rightarrow

$$p = \underbrace{\frac{V_m I_m}{2} \cos(\theta_v - \theta_i)}_{P_{avg}} + \underbrace{\frac{V_m I_m}{2} \cos(\theta_v - \theta_i) \cos(2\omega t)}_{P_{avg} \cos(2\omega t)} - \underbrace{\frac{V_m I_m}{2} \sin(\theta_v - \theta_i) \sin(2\omega t)}_{Q \sin(2\omega t)}$$

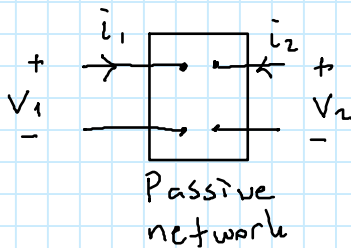Passive Network: one that contains resistors, capacitors, and/or inductors. Passive networks have a power gain less than 1.



$$\frac{V_2}{V_1} = \text{Voltage gain} = G_v$$

$$\frac{i_2}{i_1} = \text{Current gain} = G_i$$

$$\Rightarrow P_1 = V_1 \cdot i_1 = \text{input power}$$

$$\text{and } P_2 = V_2 \cdot i_2 = \text{output power}$$

$$\text{Then, } \frac{P_2}{P_1} = \text{Power gain} = G, \quad 0 < G < 1$$

Active network: is the one that

$G > 1$. Thus, it contains amplifiers,
or sources

For passive circuits (networks).

- When $p > 0 \Rightarrow$ this means the circuit is consuming power
- When $p < 0 \Rightarrow$ this means that the capacitors and/or the inductors give their stored energy into the circuit.

Real (Average) and Reactive Power

Real power or average power is given as:

$$P_{avg} = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) \quad (\text{1st term of } p)$$

and

$$Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i) \quad \text{is defined as the "reactive power"}$$

Thus, the instantaneous power can be re-written as:

$$p = P_{avg} + P_{avg} \cos(2\omega t) - Q \cdot \sin(2\omega t)$$

Power for Purely Resistive Circuits:

In these circuits, we have only resistors. Therefore,

$$\theta_v = \theta_i, \text{ and}$$


$$p = P_{avg} + P_{avg} \cos(2\omega t) \quad (\text{instantaneous power}$$

for purely resistive circuits.)

Ex:

$$V_{Th} = 10 \cos(\omega t)$$
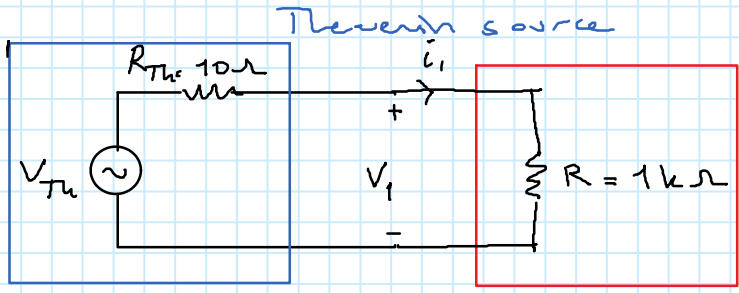
$$\omega = 2000\pi \left(\frac{\text{rad}}{\text{sec}}\right)$$



Purely resistive circuit (network)


Ans: For this circuit, find P_{avg} and p (instantaneous power)

$$V_{Th} = \frac{10 \cos(\omega t)}{2}, \Rightarrow V_1 \approx V_{Th}, \quad i_1 \approx \frac{V_{Th}}{R} = \frac{10 \cos(\omega t)}{2} \text{ mA}$$

$$\Rightarrow V_m = 10, \quad I_m = 10 \times 10^{-3}$$

$$\Rightarrow P_{avg} = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) = \frac{V_m I_m}{2} = \frac{10 \times 10 \times 10^{-3}}{2} = 50 \text{ mW}$$
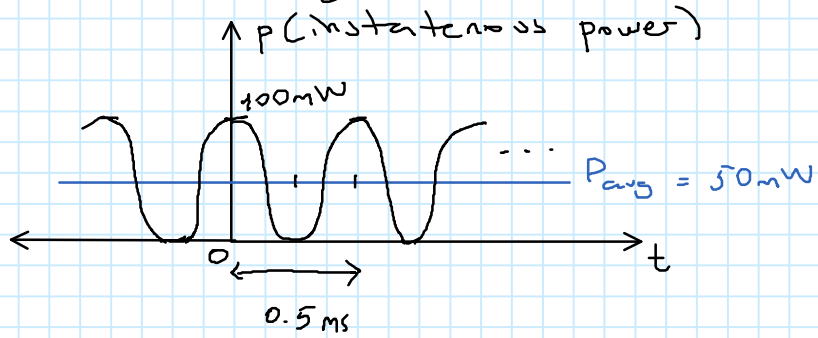
$$p = P_{avg} + P_{avg} \cos(2\omega t) = [50 + 50 \cos(2\omega t)] \text{ mW}$$



Purely Inductive Circuit.

If purely inductive $\Rightarrow \theta_i = \theta_v - 90^\circ$ or $\theta_v - \theta_i = 90^\circ$

\Rightarrow Current lags voltage


and $p = -Q \sin(2\omega t)$ (instantaneous power for purely inductive circuit)

The average power is zero. $P_{avg} = 0$, and we only have the reactive power Q .

To distinguish, for average power, we use the unit "watts", and for reactive power, we use the unit "volt-amp reactive" (VAR).


Ex:

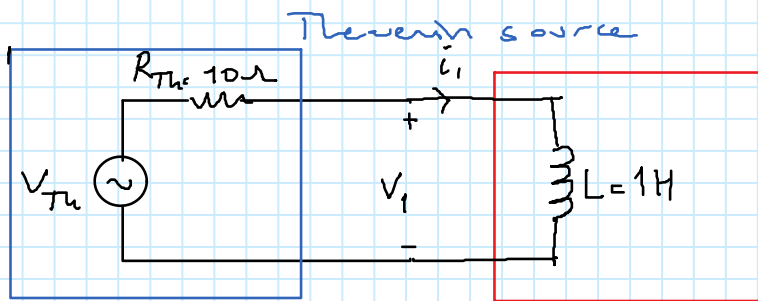$V_{Th} = 10 \cos(\omega t)$
 $\omega = 2000 \pi \text{ (rad/sec)}$



Purely inductive circuit

Find Q and p .

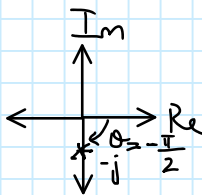

Ans.

$V_1 \approx V_{Th}, \bar{i}_1 \approx \frac{\bar{V}_{Th}}{Z} = \frac{10}{j\omega L} = \frac{10}{j(2000\pi)} = -j1.6 \times 10^{-3} = 1.6 e^{-j\frac{\pi}{2}} \text{ mA} = 1.6 \angle -\frac{\pi}{2} \text{ mA}$


$\Rightarrow i_1(t) = \text{Re}[\bar{i}_1 e^{j\omega t}] = 1.6 \cos(2000\pi t - \frac{\pi}{2}) \text{ mA}$

$V_1(t) = 10 \cos(2000\pi t), \theta_v = 0$

$\Rightarrow \theta_v - \theta_i = \frac{\pi}{2}$ (purely inductive)

$\Rightarrow Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i) = \frac{10(1.6 \times 10^{-3})}{2} \sin(\frac{\pi}{2}) = 8 \text{ mVAR}$

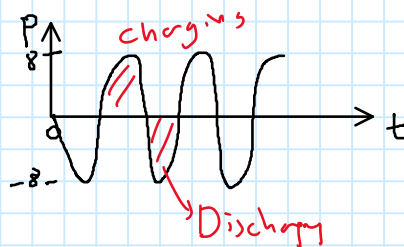and $p = -Q \sin(2\omega t) = -8 \sin(4000\pi t) \text{ (mW)}$




AC Power for Purely Capacitive Circuits.

In this case, $\theta_i = \theta_v + 90^\circ$ or $\theta_v - \theta_i = -90^\circ$ (Current leads voltage)
 and $p = -Q \sin(2\omega t)$
 $P_{avg} = 0 \text{ W.}$

Ex:

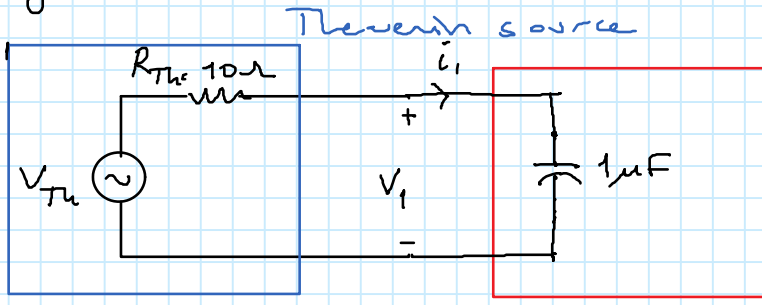$V_{Th} = 10 \cos(\omega t)$
 $\omega = 2000\pi \text{ (rad/sec)}$



Purely inductive circuit

Ans:

Find Q and P.

$V_i \approx V_{Th}$, To find $i_1(t)$:
 $\Rightarrow i_1(t) = 63 \cos(2000\pi t + \frac{\pi}{2})$

$\tilde{i}_1 \approx \frac{10}{\frac{-j}{\omega C}} = \frac{10}{\frac{-j}{(2000\pi)(10^{-6})}} = 63 \text{ mA } e^{j1.57}$

$Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i) = \frac{10(63 \times 10^{-3})}{2} \sin(-\frac{\pi}{2}) = -315 \text{ mVAR}$

$p = -Q \sin(2\omega t) = 315 \sin(4000\pi t) \text{ mW.}, P_{avg} = 0 \text{ W.}$

Power Factor. \downarrow HW 8 \downarrow

- The angle $(\theta_v - \theta_i) =$ Power factor angle.
- The cosine of this angle is called "power factor"
 i.e. $pf = \cos(\theta_v - \theta_i)$.


For a purely resistive circuit, $pf = 1$ *
 " " " inductive/capacitive, $pf = 0$

- For home appliances, we want pf to be as close to 1 as possible.

Ex:

a-) Calculate the average power and the reactive power at the terminals of the network shown in the figure below

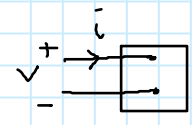$V = 100 \cos(\omega t + 15^\circ) \text{ V}$
 $i = 4 \sin(\omega t - 15^\circ) \text{ A.}$



- b-) State whether the network inside the box absorbs or delivers average power
 c-) State whether the network inside the box absorbs or delivers VAR's

Ans:

a-) Using "cos" as the reference,

$$i = 4 \sin(\omega t - 15^\circ) = 4 \cos(\omega t - 15^\circ - 90^\circ) \\ = 4 \cos(\omega t - 105^\circ) \text{ A.}$$

$$\Rightarrow \theta_v - \theta_i = 15^\circ - (-105^\circ) = 120^\circ$$

$$\Rightarrow P_{\text{avg}} = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) = \frac{100 \cdot 4}{2} \cos(120^\circ) = -100 \text{ W.}$$


$$Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i) = \frac{100 \cdot 4}{2} \sin(120^\circ) = 173.21 \text{ VAR's}$$

b-) Network inside the box delivers average power

c-) $Q > 0 \Rightarrow$ it is absorbing reactive power (inductive)

Ex:

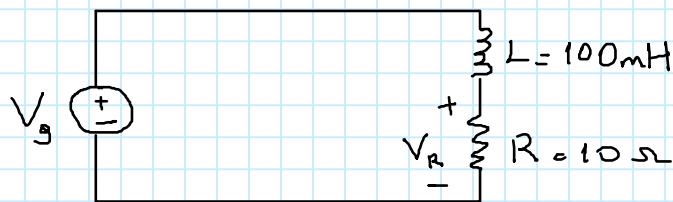For the following circuit, find the P_{avg} , Q .




$$V_g = 311 \cos(\omega t), \quad \omega = 2\pi f = 2\pi(50) = 100\pi \text{ rad/sec.}$$

Ans:

We can find the current and voltages in the circuit by using the phasor analysis.

The phasor domain circuit is given as:

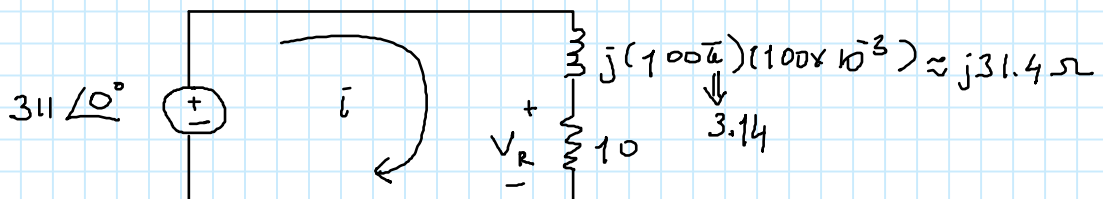

$$\bar{i} = \frac{\bar{V}_g}{Z_{total}} = \frac{311 \angle 0^\circ}{10 + j31.4} = 2.864 - j9 \text{ A} = 9.437 \angle -72.3^\circ = 9.437 \angle -72.3^\circ \text{ A}$$

$$\Rightarrow \theta = \theta_v - \theta_i = 0 - (-71^\circ) = 72.3^\circ \text{ (Inductive)}$$

$$\text{pf} = \cos(72.3^\circ) = 0.3$$

To find the real power:


$$P_{avg} = \frac{V_m I_m \cos(\theta_v - \theta_i)}{2} = ?$$

$$\bar{V}_R = \bar{i} \cdot R = 9.437 \angle -72.3^\circ \text{ V}$$


$$\Rightarrow P_{avg} = \frac{(9.437)(9.437)}{2} = 445 \text{ W}$$

$$P_{avg} = \frac{V_m I_m \cos(\theta_v - \theta_i)}{2}$$

↓
0

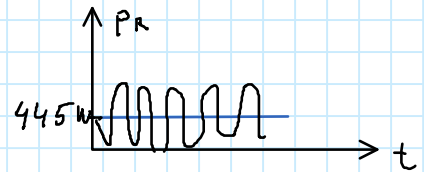

Alternatively,

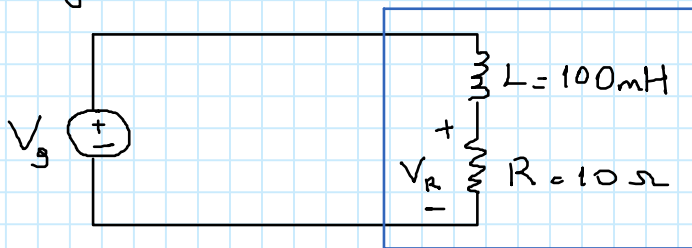

$$\bar{V}_g = 311 \angle 0^\circ, \bar{i} = 9.43 \angle -72.3^\circ$$

$$\theta = \theta_v - \theta_i = 72.3^\circ$$

$$\text{pf} = 0.3$$

$$P_{avg} = \frac{(311)(9.43)}{2} (0.3)$$

$$\cong 445 \text{ W}$$

Also,

$$Q = \frac{V_m I_m \sin(\theta)}{2} = \frac{(311)(9.43)}{2} \sin(72.3^\circ) = \frac{(311)(9.43)}{2} (0.9527)$$

$$= 1397 \text{ VAR}$$

$$\approx 1.4 \text{ kVAR}$$

RMS Value and Power Calculations -

$$V_{rms} = \frac{V_m}{\sqrt{2}}, \quad \bar{i}_{rms} = \frac{I_m}{\sqrt{2}}, \quad P_{avg} = \frac{V_m I_m}{2} \text{ (for a resistor)}$$

$$P_{avg} = V_{rms} \cdot \bar{i}_{rms}$$

Also,

$$P_{avg} = \frac{V_m^2}{2R} = \frac{I_m^2}{2} R = \frac{V_{rms}^2}{R} = \bar{i}_{rms}^2 \cdot R$$

Ex.

A sinusoidal voltage having a max amplitude of 625V is applied to the terminals of a 50Ω resistor. Find the average power delivered to the resistor.

Ans.

$$V_m = 625V, \quad V_{rms} = \frac{V_m}{\sqrt{2}} \approx \frac{V_m}{1.4} = 441.54V$$

$$\Rightarrow P_{avg} = \frac{V_{rms}^2}{R} = \frac{(441.54)^2}{50} = 3.9 \text{ kW.}$$

Alternatively

$$I_m = \frac{V_m}{R} = \frac{625}{50} = 12.5A. \quad \Rightarrow \bar{i}_{rms} = \frac{I_m}{\sqrt{2}} = 8.84A$$


$$\Rightarrow P_{avg} = \bar{i}_{rms}^2 \cdot R = (8.84)^2 (50) = 3.9 \text{ kW.}$$

- Complex Power -

Complex power is defined as


$$S = P_{avg} + jQ$$

In the complex plane:

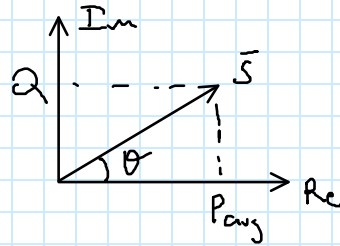

$$\theta = \theta_v - \theta_i$$

$$\tan \theta = \frac{Q}{P_{avg}}$$

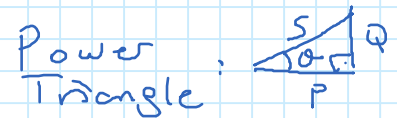

$$|S| = \text{Apparent power} = \sqrt{P_{avg}^2 + Q^2}$$

Ex:


An electrical load operates at $240 V_{rms}$. The load absorbs an average power of $8 kW$ at a lagging factor of 0.8

lagging p.f.

a-) calculate the complex power of the load.


b-) calculate the impedance of the load.

Ans:

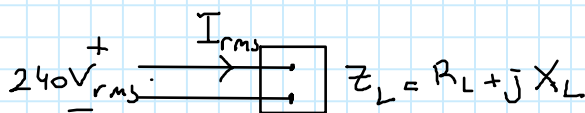

p.f. = 0.8 (lagging) $\theta_v - \theta_i > 0$ (inductive)
 $P_{avg} = 8 kW$

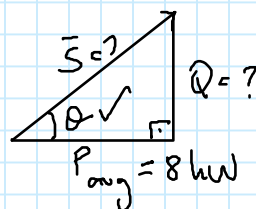a-) Let us draw the power triangle first.



$$\theta = \theta_v - \theta_i = ?$$

$$pf = \cos(\theta_v - \theta_i) = \cos \theta = 0.8$$

$$\cos \theta = 0.8 \Rightarrow \sin \theta = 0.6$$

From the power triangle.

$$P_{avg} = |\bar{S}| \cdot \cos \theta$$

Also, $Q = |\bar{S}| \cdot \sin \theta$

$$\Rightarrow |\bar{S}| = \frac{P_{avg}}{\cos \theta} = \frac{8000}{0.8} = 10 \text{ kVA.}$$

$$\text{and } Q = 10 \cdot \sin \theta \text{ kVAR} = 10 \cdot 0.6 \text{ kVAR's.} = 6 \text{ kVAR's.}$$

$$\Rightarrow \bar{S} = 8 \text{ kW} + j6 \text{ kVAR's}$$

$$b-) Z_L = ? \quad , \quad Z_L = \frac{V_{rms} \angle \theta_v}{I_{rms} \angle \theta_i} = \frac{V_{eff} \angle \theta_v}{I_{eff} \angle \theta_i}$$

$$Q = V_{eff} \cdot I_{eff} \cdot \sin \theta$$

\downarrow \downarrow \downarrow
 6 kVAR's 240V 0.6

$$\Rightarrow I_{eff} = 41.67 \text{ A.}$$

$$\cos \theta = 0.8$$

Thus,

$$Z_L = \frac{V_{eff} \angle \theta_v - \theta_i}{I_{eff}} = \frac{240 \angle \theta}{41.67} = 5.76 \angle 36.87^\circ$$

$$\Rightarrow Z_L = 4.608 + j3.456 \Omega.$$

$$R_L = 4.6 \Omega$$

$$\omega L = 3.456 \quad (\text{Taking } f = 50 \text{ Hz.})$$

$$\Rightarrow L = \frac{3.456}{100\pi} = 0.011 = 11 \text{ mH.}$$

- Power Calculations -

The complex power is $S = P + jQ$ (VA)

where

$$P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$$

$$Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i)$$

Then,

$$S = \frac{V_m I_m}{2} [\cos(\theta_v - \theta_i) + j \sin(\theta_v - \theta_i)]$$

$$= \frac{V_m I_m}{2} e^{j(\theta_v - \theta_i)} = \frac{V_m I_m}{2} \angle \theta_v - \theta_i = V_{eff} \cdot I_{eff} \angle \theta_v - \theta_i$$

Thus, $S = V_{\text{eff}} I_{\text{eff}} \angle(\theta_v - \theta_i)$, where $V_{\text{eff}} = V_{\text{rms}}$ and $I_{\text{eff}} = I_{\text{rms}}$.

Furthermore,

$$S = V_{\text{eff}} I_{\text{eff}} e^{j(\theta_v - \theta_i)} = \underbrace{V_{\text{eff}} e^{j\theta_v}}_{\bar{V}_{\text{eff}}} \cdot \underbrace{I_{\text{eff}} e^{-j\theta_i}}_{\bar{I}_{\text{eff}}^*} = \bar{V}_{\text{eff}} \cdot \bar{I}_{\text{eff}}^*$$

$$\Rightarrow S = \bar{V}_{\text{eff}} \cdot \bar{I}_{\text{eff}}^*$$

Alternatively,

$$S = \frac{1}{2} \cdot \bar{V} \cdot \bar{I}^*$$

Also,

$$Z = \frac{\bar{V}_{\text{eff}}}{\bar{I}_{\text{eff}}} \Rightarrow S = (Z \bar{I}_{\text{eff}}) \bar{I}_{\text{eff}}^* = |\bar{I}_{\text{eff}}|^2 Z \quad (\text{VAR})$$

$$I_{\text{eff}} e^{j\theta_i} \cdot I_{\text{eff}} e^{-j\theta_i}$$

or

$$S = |\bar{I}_{\text{eff}}|^2 Z = |\bar{I}_{\text{eff}}|^2 (R + jX) = \underbrace{|\bar{I}_{\text{eff}}|^2 R}_{P_{\text{avg}}} + j \underbrace{|\bar{I}_{\text{eff}}|^2 X}_{Q}$$

or

$$S = \frac{1}{2} |\bar{I}|^2 Z$$

Similarly,

$$S = \frac{|\bar{V}_{\text{eff}}|^2}{Z^*} = P_{\text{avg}} + jQ, \quad \text{where } P_{\text{avg}} = \frac{|\bar{V}_{\text{eff}}|^2}{R}$$

or

$$S = \frac{|\bar{V}|^2}{2Z^*} \quad \text{and } Q = \frac{|\bar{V}_{\text{eff}}|^2}{X}$$

Ex

Given $\bar{V} = 100 \angle 15^\circ$ (V) and $\bar{I} = 4 \angle -105^\circ$ (A) \Rightarrow Find S .

Ans

$$\text{Using } S = \frac{1}{2} \cdot \bar{V} \cdot \bar{I}^* = \frac{1}{2} (100 \angle 15^\circ) (4 \angle -105^\circ)^* = 200 \angle 15^\circ - (-105)^\circ$$

$$= 200 \angle 120^\circ$$


$$= -100 + j173.21 \text{ (VA)}$$

Then, $P_{\text{avg}} = -100 \text{ W}$ (source)

and $Q = 173.21 \text{ VARs}$.

EX:

Given the circuit.

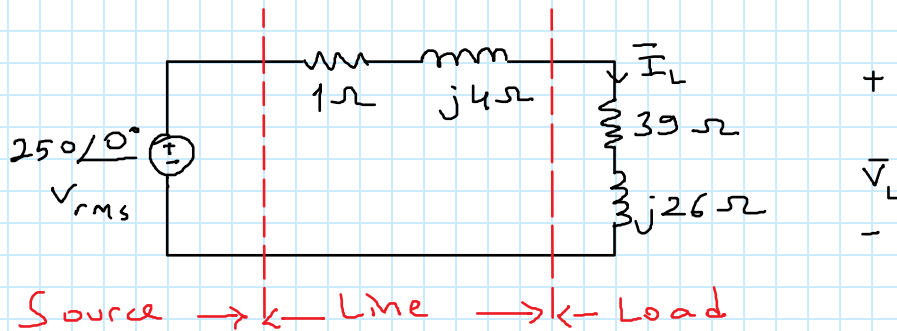

Calculate

- The load current \bar{I}_L and voltage \bar{V}_L
- The average and reactive power delivered to the load.
- The " " " " " " " "
- The " " " " " " " " supplied by the source.

Ans

$$a-) \bar{I}_L = \frac{\bar{V}_{source}}{Z_{total}} = \frac{250 \angle 0^\circ}{40 + j30} = 4 - j3 \text{ (A)} = 5 \angle -36.87^\circ \text{ (A)} (\underline{\underline{rms}}) \\ = \bar{I}_{eff}$$

$$\bar{V}_L = \bar{I}_L \cdot Z_L = (5 \angle -36.87^\circ) (39 + j26) = 234.36 \angle -3.18^\circ \text{ (V)}_{rms} \\ = 46.87 \angle 0.588 \\ = 46.87 \angle 33.7^\circ$$

$$b-) S = \bar{V}_{eff} \cdot \bar{I}_{eff}^* \Rightarrow S_L = \bar{V}_L \cdot \bar{I}_L^* = (234.36 \angle -3.18^\circ) (5 \angle 36.87^\circ) \\ = 975 + j650 \text{ VA}$$

Thus, the load absorbs average power of 975 W and reactive power of 650 VARs.

$$c-) \bar{P}_{avg, line} = |\bar{I}_{eff}|^2 R_{line} = (5)^2 (1) = 25 \text{ W.}$$

$$Q = |\bar{I}_{eff}|^2 X = (5)^2 (4) = 100 \text{ VARs.}$$

$$d-) S = \underbrace{(25 + j100)}_{S_{\text{Line}}} + \underbrace{(975 + j650)}_{S_L} \Rightarrow S_{\text{source}} = 1000 + j750 \text{ VA}$$

is supplied.

or

- HW 9 -

$$S_{\text{source}} = -1000 - j750 \text{ VA}$$

Introduction to the Laplace Transform -

The Laplace transform is defined as

$$\mathcal{L}\{f(t)\} = \int_0^{\infty} f(t) e^{-st} dt \quad (\text{one-sided unilateral Laplace Transform})$$

The operator $\mathcal{L}\{f(t)\}$ = Laplace transform of $f(t)$

Also,

$$F(s) = \mathcal{L}\{f(t)\} \quad \text{where } \mathcal{L} = \text{Laplace operator}$$

Some important functions are


$$s = \text{Laplace variable.} \\ = j\omega$$

→ Step Function:

It is defined as:

$$k \cdot u(t) = \begin{cases} k \cdot u(t) = 0, & t < 0 \\ k \cdot u(t) = 1, & t > 0 \end{cases}$$


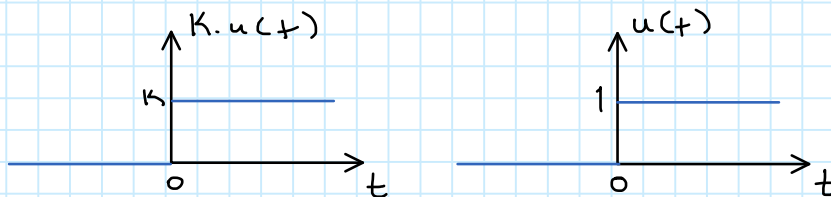
If $k=1$, then the step function is called "unit step function" ($u(t)$).



- It is not defined at $t=0$.

- Impulse Function = $\delta(t)$

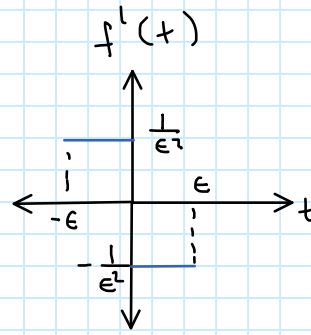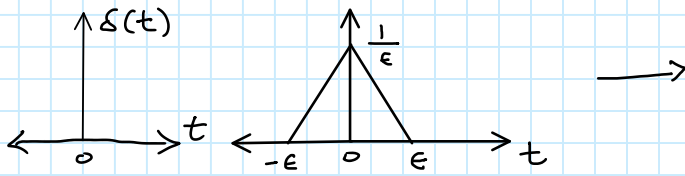$f(t) \approx \delta(t)$ as $\epsilon \rightarrow 0$



Functional Transforms:

$$\mathcal{L}\{u(t)\} = \int_0^{\infty} f(t) e^{-st} dt = \int_0^{\infty} 1 \cdot e^{-st} dt = \frac{e^{-st}}{-s} \Big|_0^{\infty} = 1.$$


$$\mathcal{L}\{e^{-at}\} = \int_0^{\infty} e^{-at} \cdot e^{-st} dt = \int_0^{\infty} e^{-(a+s)t} dt = \frac{1}{s+a}$$

$$\mathcal{L}\{\sin \omega t\} = \int_0^{\infty} \sin \omega t \cdot e^{-st} dt = \int_0^{\infty} \frac{e^{j\omega t} - e^{-j\omega t}}{2j} \cdot e^{-st} \cdot dt = \frac{\omega}{s^2 + \omega^2}$$

List of Laplace Transform Pairs.

$f(t)$	$F(s)$	$f(t) (t > 0^-)$	$F(s)$
$Kf(t)$	$KF(s)$	$\delta(t)$	1
$f_1(t) + f_2(t) - f_3(t) + \dots$	$F_1(s) + F_2(s) - F_3(s) + \dots$	$u(t)$	$\frac{1}{s}$
$\frac{df(t)}{dt}$	$sF(s) - f(0^-)$	t	$\frac{1}{s^2}$
$\frac{d^2f(t)}{dt^2}$	$s^2F(s) - sf(0^-) - \frac{df(0^-)}{dt}$	e^{-at}	$\frac{1}{s+a}$
$\frac{d^n f(t)}{dt^n}$	$s^n F(s) - s^{n-1}f(0^-) - s^{n-2}\frac{df(0^-)}{dt} - s^{n-3}\frac{d^2f(0^-)}{dt^2} - \dots - \frac{d^{n-1}f(0^-)}{dt^{n-1}}$	$\sin \omega t$	$\frac{\omega}{s^2 + \omega^2}$
$\int_0^t f(x) dx$	$\frac{F(s)}{s}$	$\cos \omega t$	$\frac{s}{s^2 + \omega^2}$
$f(t-a)u(t-a), a > 0$	$e^{-as}F(s)$	te^{-at}	$\frac{1}{(s+a)^2}$
$e^{-at}f(t)$	$F(s+a)$	$e^{-at} \sin \omega t$	$\frac{\omega}{(s+a)^2 + \omega^2}$
$f(at), a > 0$	$\frac{1}{a}F\left(\frac{s}{a}\right)$	$e^{-at} \cos \omega t$	$\frac{s+a}{(s+a)^2 + \omega^2}$
$tf(t)$	$-\frac{dF(s)}{ds}$		
$t^n f(t)$	$(-1)^n \frac{d^n F(s)}{ds^n}$		
$\frac{f(t)}{t}$	$\int_s^{\infty} F(u) du$		

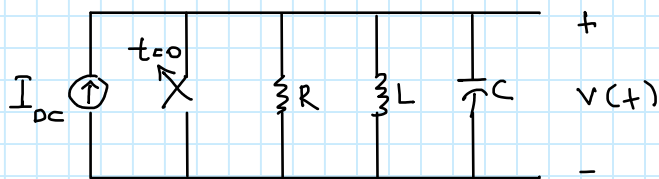Applying the Laplace Transform:
Consider the following circuit.



Given that the initial energy stored in the circuit is zero. Find $v(t)$ for $t \geq 0$.

Thus, this is a transient response problem of a parallel RLC circuit.

Now, let us see how we can solve this problem by the Laplace transform.

Node-voltage equation is.

$$\frac{v(t)}{R} + \frac{1}{L} \int_0^t v(x) dx + C \frac{dv(t)}{dt} = I_{DC} u(t)$$

- Take the Laplace transform of both sides

$$\frac{v(s)}{R} + \frac{1}{L} \frac{v(s)}{s} + C [s v(s) + v(0^+)] = I_{DC} \cdot \frac{1}{s}$$

where $v(s)$ is unknown and $R, L, C, v(0^+)$ and I_{DC} are known.

Then,

$$v(s) \left(\frac{1}{R} + \frac{1}{sL} + sC \right) = \frac{I_{DC}}{s}$$

or

$$v(s) = \frac{I_{DC}/C}{s^2 + \left(\frac{1}{RC}\right)s + \frac{1}{LC}}$$

In order to find $v(t)$, we need to find the "inverse transform" of $v(s)$, i.e.,

$$v(t) = \mathcal{L}^{-1} \{ v(s) \}$$

- Inverse Laplace Transform:

In general, we need to find the inverse Laplace transform of a function which has the following form:

$$F(s) = \frac{N(s)}{D(s)} = \frac{a_n s^n + a_{n-1} s^{n-1} + \dots + a_1 s + a_0}{b_m s^m + b_{m-1} s^{m-1} + \dots + b_1 s + b_0}, \quad m, n = \text{integers.}$$

If $m > n \Rightarrow F(s)$: proper

If $m \leq n \Rightarrow F(s)$: improper.

Partial Fraction Method for the Solution of proper $F(s)$:

Let us consider the following example

$$F(s) = \frac{s+6}{s(s+3)(s+1)^2}$$

Then, $D(s)$ has 4 roots: $s=0$, $s=-3$, $s=-1$ (two roots at $s=-1$)

The partial fraction form is

$$\frac{s+6}{s(s+3)(s+1)^2} = \frac{K_1}{s} + \frac{K_2}{s+3} + \frac{K_3}{(s+1)^2} + \frac{K_4}{(s+1)}$$

Then,

$$\mathcal{L}^{-1} \left\{ \frac{s+6}{s(s+3)(s+1)^2} \right\} = [K_1 + K_2 e^{-3t} + K_3 \cdot t e^{-t} + K_4 e^{-t}] u(t)$$

We need to find the coefficients K_1, K_2, K_3 and K_4 .

There are 4 cases of this problem.

The roots of $D(s)$ are either

- 1-) Real and distinct.
- 2-) Complex and distinct
- 3-) Real and repeated.
- 4-) Complex and repeated

1-) Real and Distinct Roots of $D(s)$:

Assume we have

$$F(s) = \frac{96(s+5)(s+12)}{s(s+8)(s+6)} = \frac{K_1}{s} + \frac{K_2}{s+8} + \frac{K_3}{s+6}$$

To find the value of K_1 , we multiply both sides by s , and evaluate the both sides at $s=0$

$$\left. \frac{96(s+5)(s+12)}{(s+8)(s+6)} \right|_{s=0} = K_1 + \cancel{\frac{K_2 s}{s+8}} + \cancel{\frac{K_3 s}{s+6}}$$

$$\frac{96 \cdot 5 \cdot 12}{8 \cdot 6} = K_1 \Rightarrow K_1 = 120$$

To find K_2 , multiply both sides by $(s+8)$ and evaluate both sides at $s=-8$.

$$K_2 = -72, \quad K_3 = 48.$$

Then,

$$f(t) = \mathcal{L}^{-1}\{F(s)\} = [120 - 72e^{-8t} + 48e^{-6t}]u(t)$$

2-) Complex and Distinct Roots of $D(s)$.

Consider

$$F(s) = \frac{100(s+3)}{(s+6)(s^2+6s+25)}$$

$$\underbrace{(s^2+6s+25)}_{(s+3-j4)(s+3+j4)}$$

$$\Rightarrow F(s) = \frac{K_1}{s+6} + \frac{K_2}{s+3-j4} + \frac{K_3}{s+3+j4}$$

Then,

$$K_1 = \left. \frac{100(s+3)}{(s^2+6s+25)} \right|_{s=-6} = \frac{100(-3)}{25} = -12$$

P58

Monday, May 10, 2021 11:03 AM

and

$$K_2 = \frac{100(s+3)}{(s+6)} \bigg|_{s=-3+j4} = 6 - j8 = 10e^{-j53^\circ}$$

and

$$K_3 = \frac{100(s+3)}{(s+6)} \bigg|_{s=-3-j4} = 6 + j8 = 10e^{j53^\circ}$$

Then,

$$f(t) = \mathcal{L}^{-1}\{F(s)\} = \left[-12e^{-6t} + 10e^{-j53^\circ} e^{-(3-j4)t} + 10e^{j53^\circ} e^{-(3+j4)t} \right] u(t)$$

Using the identity

$$\mathcal{L}^{-1}\left\{ \frac{k}{s+d-j\beta} + \frac{k^*}{s+d+j\beta} \right\} = 2|k| e^{-dt} \cos(\beta t + \theta)$$

$$\Rightarrow \mathcal{L}^{-1}\{F(s)\} = \left[-12e^{-6t} + 20e^{-3t} \cos(4t + 53^\circ) \right] u(t)$$

—o—

3-) Real and Repeated Roots of $D(s)$

Consider

$$F(s) = \frac{100(s+25)}{s(s+5)^3} = \frac{K_1}{s} + \frac{K_2}{(s+5)^3} + \frac{K_3}{(s+5)^2} + \frac{K_4}{(s+5)}$$

and

$$K_1 = \frac{100(s+25)}{(s+5)^3} \Big|_{s=0} = \frac{100(25)}{125} = 20.$$

- To find K_2 , multiply both sides by $(s+5)^3$, and evaluate at $s = -5$.

$$\Rightarrow K_2 = \frac{100(20)}{-5} = -400$$

- To find K_3 , multiply both sides by $(s+5)^3$, and then differentiate once with respect to s , and evaluate at $s = -5$.

$$\frac{d}{ds} \left[\frac{100(s+25)}{s} \right]_{s=-5} = \frac{d}{ds} \left[\frac{K_1(s+5)^3}{s} \right]_{s=-5} + \frac{d}{ds} [K_2]_{s=-5}$$

$$+ \frac{d}{ds} [K_3(s+5)]_{s=-5} + \frac{d}{ds} [K_4(s+5)^2]_{s=-5}$$

$$\Rightarrow K_3 = 100 \left[\frac{s - (s+25)}{s^2} \right]_{s=-5} = -100$$

-> To find K_4 , multiply both sides by $(s+5)^3$, and differentiate twice w.r.t s , and evaluate at $s = -5$

$$\Rightarrow K_4 = -20.$$

$$\Rightarrow \mathcal{L}^{-1}\{F(s)\} = [20 - 200t^2 e^{-5t} - 100t e^{-5t} - 20e^{-5t}] u(t)$$

4-) Complex and Repeated Roots

Consider

$$F(s) = \frac{768}{(s^2+6s+25)^2}$$

$$\underbrace{(s+3-j4)(s+3+j4)}_{(s+3-j4)(s+3+j4)}$$

$$F(s) = \frac{K_1}{(s+3-j4)^2} + \frac{K_2}{(s+3-j4)} + \frac{K_1^*}{(s+3+j4)^2} + \frac{K_2^*}{(s+3+j4)}$$

P60

Monday, May 10, 2021 11:34 AM

where

$$K_1 = \left. \frac{768}{(s+3-j4)^2} \right|_{s=-3+j4} = \frac{768}{(j8)^2} = -12.$$

and

$$K_2 = \frac{d}{ds} \left[\frac{768}{(s+3+j4)^2} \right]_{s=-3+j4} = \frac{2(768)}{(s+3+j4)^2} \bigg|_{s=-3+j4} = \frac{-2(768)}{(j8)^3}$$

$$\Rightarrow K_2 = -j3 = 3 \angle -90^\circ$$

$$K_1^* = -12, \quad K_2^* = -j3 = 3 \angle 90^\circ$$


$$\Rightarrow f(t) = \mathcal{L}^{-1}\{F(s)\} = [-24te^{-3t} \cos(4t) + 6e^{-3t} \cos(4t - 90^\circ)] u(t).$$

In summary, the compact formulations for all 4 cases are given below:

Nature of Roots	$F(s)$	$f(t)$
Distinct real	$\frac{K}{s+a}$	$Ke^{-at}u(t)$
Repeated real	$\frac{K}{(s+a)^2}$	$Kte^{-at}u(t)$
Distinct complex	$\frac{K}{s+\alpha-j\beta} + \frac{K^*}{s+\alpha+j\beta}$	$2 K e^{-\alpha t} \cos(\beta t + \theta)u(t)$
Repeated complex	$\frac{K}{(s+\alpha-j\beta)^2} + \frac{K^*}{(s+\alpha+j\beta)^2}$	$2t K e^{-\alpha t} \cos(\beta t + \theta)u(t)$



Ex

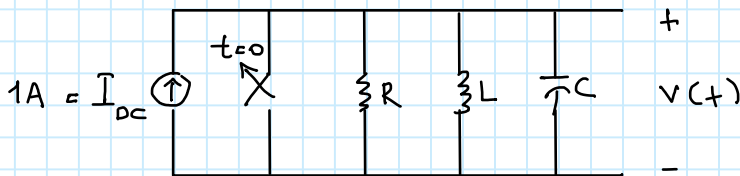

$$R = 1k\Omega, \quad L = 1mH, \quad C = 10\mu F.$$

$$v(s) = \frac{I_{oc}/C}{s^2 + \left(\frac{1}{RC}\right)s + \frac{1}{LC}} = \frac{1/10 \times 10^{-6}}{s^2 + \left(\frac{1}{10 \times 10^{-3}}\right)s + \frac{1}{10 \times 10^{-9}}}$$

or

$$V(s) = \frac{10^5}{\underbrace{s^2 + 100s + 10^8}_{(s+50-10000j)(s+50+10000j)}}$$

$$\Rightarrow V(s) = \frac{K_1}{s+50-10000j} + \frac{K_2}{s+50+10000j}$$

To find K_1 .

Multiply both sides by $(s^2 + 100s + 10^8)$ and evaluate at $s = -50 + 10000j$

$$10^5 = K_1(s+50+10000j) \Big|_{s=-50+10000j} + K_2(s+50-10000j) \Big|_{s=-50+10000j}$$

$$\Rightarrow K_1 = \frac{10^5}{20000j} = -5j = 5 \angle -90^\circ$$

$$K_2 = 5 \angle 90^\circ$$

$$\begin{aligned} v(t) &= \mathcal{L}^{-1}\{V(s)\} = 2|K_1| e^{-\alpha t} \cos(\beta t + \theta) \\ &= 10 e^{-50t} \cos\left(10000t - \frac{\pi}{2}\right) u(t) \text{ v.} \end{aligned}$$

Partial Fraction Expansion for Improper Rational Functions -

Consider

$$F(s) = \frac{s^4 + 13s^3 + 66s^2 + 200s + 300}{s^2 + 9s + 20}$$

After polynomial division

$$\begin{array}{r|l} s^4 + 13s^3 + 66s^2 + 200s + 300 & s^2 + 9s + 20 \\ \hline -(s^4 + 9s^3 + 20s^2) & s^2 + 4s + 10 \\ \hline 4s^3 + 46s^2 + 200s + 300 & \\ -(4s^3 + 36s^2 + 80s) & \\ \hline 10s^2 + 120s + 300 & \\ -(10s^2 + 90s + 200) & \\ \hline 30s + 100 & \end{array}$$

P62

Monday, May 17, 2021 9:37 AM

$$\Rightarrow F(s) = s^2 + 4s + 10 + \frac{30s + 100}{s^2 + 9s + 20} \xrightarrow{\text{Remainder}}$$

$$= \frac{30s + 100}{(s+4)(s+5)} = \frac{-20}{s+4} + \frac{50}{s+5}$$

Then,

$$f(t) = \frac{d^2 \delta(t)}{dt^2} + 4 \frac{d\delta(t)}{dt} + 10\delta(t) - (20e^{-4t} - 50e^{-5t})u(t)$$

Poles and Zeros of $F(s)$

Consider

$$F(s) = \frac{K(s+z_1)(s+z_2)\dots(s+z_n)}{(s+p_1)(s+p_2)\dots(s+p_m)}$$

- The roots of the denominator polynomial $-p_1, -p_2, \dots, -p_m$ are called "poles of $F(s)$ "
- The roots of the numerator polynomial $-z_1, -z_2, \dots, -z_n$ are called "zeros of $F(s)$ "


Ex

Given

$$F(s) = \frac{10(s+5)(s+3-j4)(s+3+j4)}{s(s+10)(s+6-j8)(s+6+j8)}$$

Show the zeros and poles on the z -plane.

Ans:

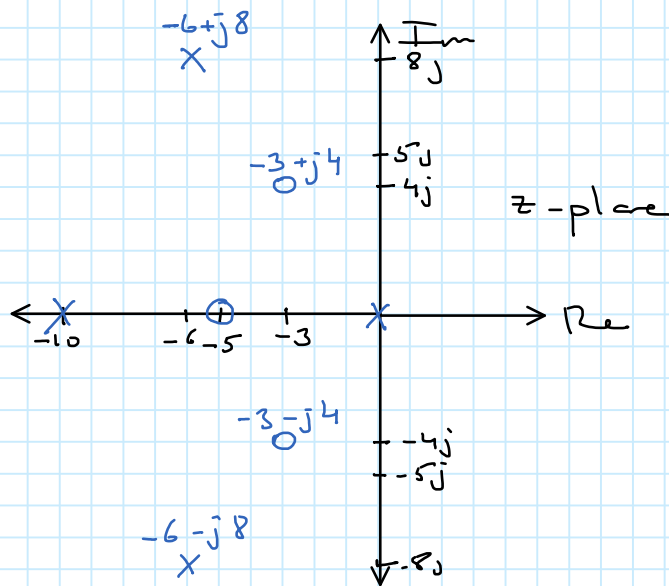

↓ HW 10 ↓

P63

Monday, May 17, 2021 9:54 AM

- Laplace Transform in Circuit Analysis - Circuit Elements in the s-domain:

Resistor

$$v = Ri \text{ (Ohm's law)}$$

Since R is constant, the Laplace transform of Ohm's law is $V = RI$ where $V = \mathcal{L}\{v\}$, $I = \mathcal{L}\{i\}$, $\mathcal{L}\{R\} = R$

Inductor

$v = L \frac{di}{dt}$ is given. Take the Laplace transform of both sides,


$$V = \mathcal{L}\{sI - i(0^-)\} = sLI - LI_0$$

or

$$I = \frac{V + LI_0}{sL} = \frac{V}{sL} + \frac{I_0}{s}$$

If $I_0 = \text{Initial current} = 0$, then
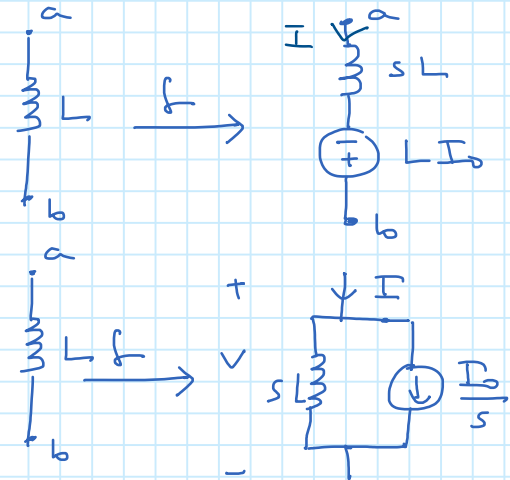
$$V = sLI \text{ where } \boxed{Z_L = sL} \text{ (}\Omega\text{)}$$



Capacitor

$i = C \frac{dv}{dt}$ is given. Take the Laplace transform of both sides,

$$I = C[sV - v(0^-)]$$

or



$$I = sCV - CV_0$$

or

$$V = \left(\frac{1}{sC}\right)I + \frac{V_0}{s}$$

If $V_0 = 0$, then,
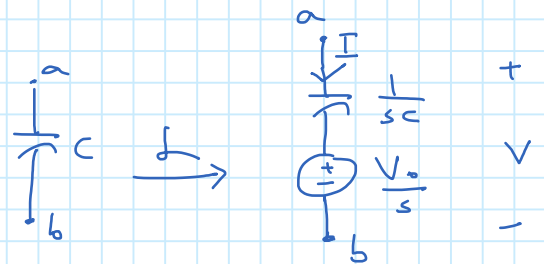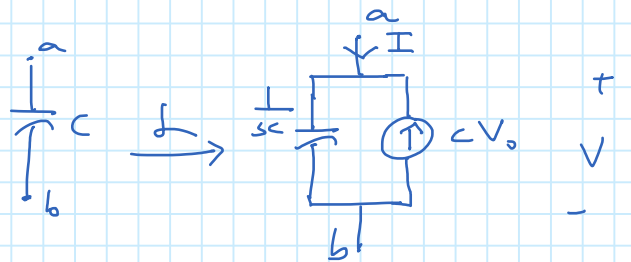
$$V = \left(\frac{1}{sC}\right)I \Rightarrow \boxed{Z_C = \frac{1}{sC}} \text{ (}\Omega\text{)}$$



Circuit Analysis in the s-domain:

$$V = Z I \text{ (in the s-domain)}$$


$$\sum I = 0$$

$\sum v = 0$ } Kirchhoff's laws

P64

Monday, May 17, 2021 10:20 AM

Ex:

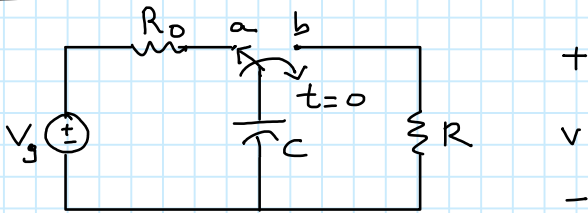


Find v for $t \geq 0$ using Laplace transform
Given

$$R_0 = 100\Omega, C = 10\mu\text{F}, R = 1\text{k}\Omega.$$


$$\text{Also, } V_g = 10\text{V (DC)}$$

Ans:

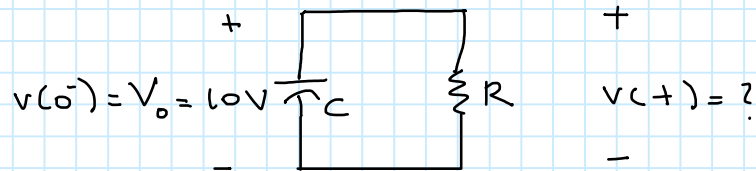- we have the natural response of an RC circuit.
- Let us find the initial capacitor voltage $V_0 = V_g = 10\text{V}$.
- The circuit for $t \geq 0$ is



- We convert the circuit into s-domain.

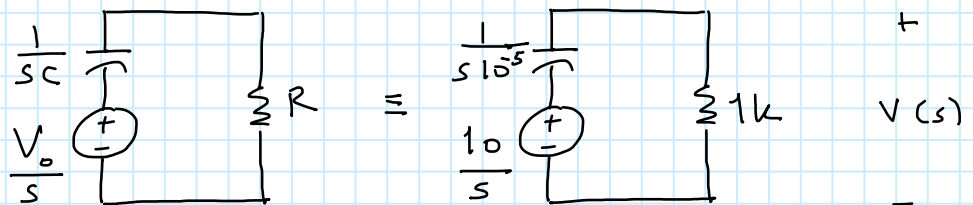


Using the voltage division

$$v(s) = \frac{10}{s} \cdot \frac{1\text{k}}{1\text{k} + \frac{10^5}{s}} = \frac{10}{s} \cdot \frac{1000s}{1000s + 10^5} = \frac{10000}{1000s + 10^5}$$


$$= \frac{10}{s + 100}$$

$$\Rightarrow v(t) = \mathcal{L}^{-1}\{v(s)\} = 10e^{-100t} u(t)$$

$$\tau = \frac{1}{100} = 10\text{ms}$$

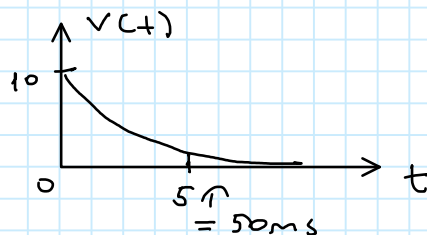

Ex


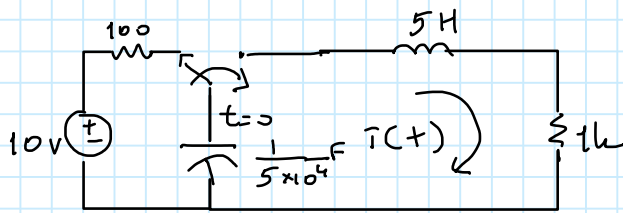


Find $i(t)$ for $t \geq 0$
using the Laplace transform

Ans:

- This is a natural response of a series RLC circuit.
- Initial conditions are $V_0 =$ Initial capacitor voltage $= 10V$.
- $I_0 =$ Initial inductor current $= 0$.

- The circuit in s-domain =

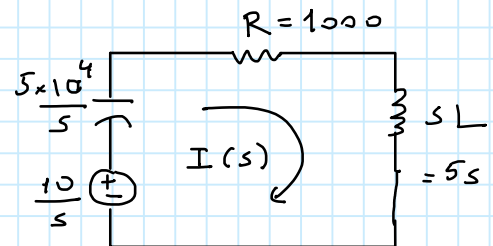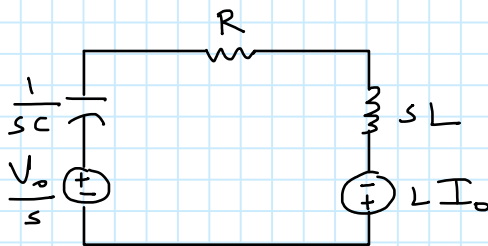

$$\Rightarrow I(s) = \frac{10/s}{\frac{1000}{1} + \frac{5s}{1} + \frac{5 \times 10^4}{s}} = \frac{10}{s} \cdot \frac{1}{5s^2 + 1000s + 5 \times 10^4}$$

$$= 10 \cdot \frac{1}{5s^2 + 1000s + 5 \times 10^4} \cdot (1/s)$$

$$= 2 \cdot \frac{1}{s^2 + 200s + 10^4}$$

$$= \frac{K_1}{(s+100)^2} + \frac{K_2}{s+100}$$

\Rightarrow Find K_1 and K_2 and find $\mathcal{L}^{-1}\{I(s)\}$.

$$\frac{2}{s^2 + 200s + 10^4} = \frac{K_1}{(s+100)^2} + \frac{K_2}{s+100}$$

$$\Rightarrow K_1 = 2, K_2 = 0.$$

$$i(t) = 2t e^{-100t} u(t)$$

e^{-at}	$\frac{1}{s+a}$
$\sin \omega t$	$\frac{\omega}{s^2 + \omega^2}$
$\cos \omega t$	$\frac{s}{s^2 + \omega^2}$
te^{-at}	$\frac{1}{(s+a)^2}$

- Transfer Function -

The transfer function is the s-domain ratio of the output (response) to the input (source)


If a circuit has multiple independent sources, we can find the transfer function for each source and use superposition (sum) to find the overall response to all sources

The transfer function is defined as

$$H(s) = \frac{Y(s)}{X(s)}$$

where $Y(s)$ Laplace transform of the output signal.
 $X(s)$ Laplace transform of the input signal

For example,

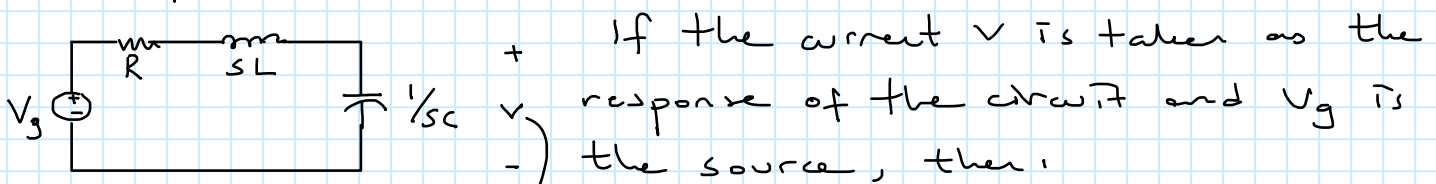

$$H(s) = \frac{Y(s)}{X(s)} = \frac{V(s)}{V_g(s)} \Rightarrow$$


where

$$V(s) = V_g(s) \frac{1/sC}{\underbrace{\frac{1}{sC} + sL + R}_{H(s)}}$$

$$\Rightarrow H(s) = \frac{1}{s^2LC + sRC + 1}$$

Ex:

Given the circuit

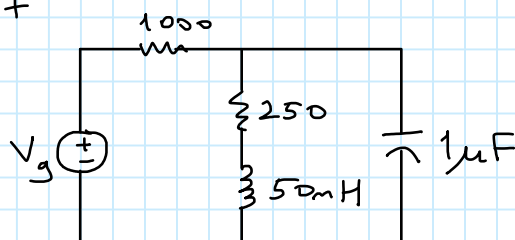


+ $V_g = 50t u(t)$
 Find $H(s)$.
 Find $V_o(t)$ using
 - $H(s)$.

P67

Monday, May 24, 2021 10:31 AM

Ans: s-domain circuit

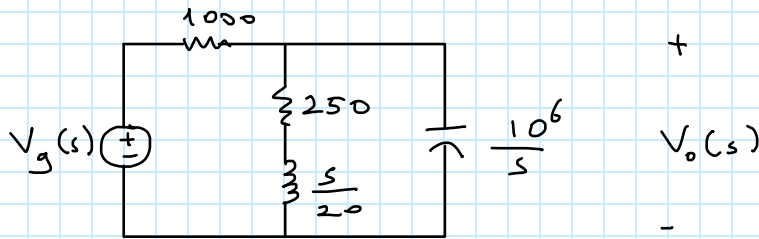

$H(s) = \frac{V_o(s)}{V_g(s)} \Rightarrow$ Using the voltage division

$$V_o(s) = V_g(s) \frac{\left(\frac{10^6}{s}\right) \parallel \left(250 + \frac{s}{20}\right)}{1000 + \left[\frac{10^6}{s} \parallel \left(250 + \frac{s}{20}\right)\right]}$$

$H(s)$

$$\Rightarrow H(s) = \frac{1000(s + 5000)}{s^2 + 6000s + 25 \times 10^6}$$

$$\Rightarrow V_o(s) = X(s) \cdot H(s) = \frac{50}{s^2} \cdot \frac{1000(s + 5000)}{s^2 + 6000s + 25 \times 10^6}$$

where $X(s)$:

$f(t)$		$f(s)$
te^{-at}		$\frac{1}{(s+a)^2}$

$$X(t) = 50t u(t)$$



$$\frac{50}{(s+0)^2} = \frac{50}{s^2}$$

$$V_o(s) = \frac{5\sqrt{5} \times 10^{-4} \angle -79.7^\circ}{s + 3000 + j4000} + \frac{10}{s^2} - \frac{4 \times 10^{-4}}{s}$$

$$\Rightarrow v_o(t) = \left[10\sqrt{5} \times 10^{-4} e^{-3000t} \cos(4000t + 79.7^\circ) + 10t - 4 \times 10^{-4} \right] u(t)$$

Frequency Selective Circuits (Filters)

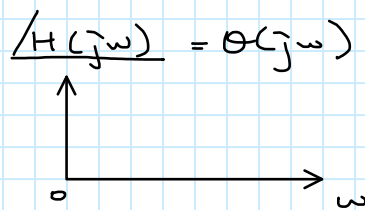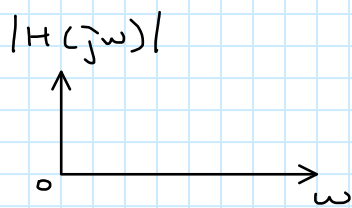- Frequency selective circuit means that when the input frequency changes the output changes
- Filter analysis is done by using the transfer function $H(s)$
- We replace the variable $s = j\omega$, and obtain $H(j\omega)$ as a complex expression.
- Then, we plot




- These 2 plots are called the "Bode Plots"

There are 4 types of frequency response characteristics:

1-) Low-Pass Filter (LPF)

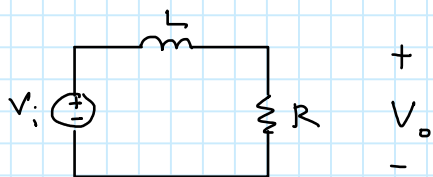- This circuit passes low frequencies, and blocks (filters out) high frequencies
- We can implement a LPF from a serial RL circuit as:



The transfer function is:

$$H(s) = \frac{R}{R + sL} \quad \frac{(1/L)}{(1/L)}$$

$$\Rightarrow H(s) = \frac{R/L}{s + R/L} \quad (\text{Transfer func. in } s\text{-domain})$$

Now, replace $s = j\omega$.

$$H(j\omega) = \frac{R/L}{j\omega + \frac{R}{L}} \quad (\text{Transfer function in frequency domain})$$

P69

Monday, May 24, 2021 10:58 AM

Let us find

$$|H(j\omega)| = \frac{|R/L|}{|j\omega + \frac{R}{L}|}$$

$$\frac{R}{L} + j\omega = a + jb \Rightarrow |a + jb| = \sqrt{a^2 + b^2}$$

$$\Rightarrow |H(j\omega)| = \frac{R/L}{\sqrt{\omega^2 + (\frac{R}{L})^2}}$$

and

$$\theta(j\omega) = \angle H(j\omega) = ?$$

$$\text{where } H(j\omega) = \frac{R/L}{j\omega + \frac{R}{L}}$$

$$\frac{a + jb}{c + jd} = \frac{|a + jb| \cdot e^{j \tan^{-1}(\frac{b}{a})}}{|c + jd| \cdot e^{j \tan^{-1}(\frac{d}{c})}}$$

$|H(j\omega)|$

$$= |H(j\omega)| \cdot e^{j \left[\tan^{-1} \frac{b}{a} - \tan^{-1} \left(\frac{d}{c} \right) \right]}$$

$$\angle H(j\omega) = \theta(j\omega)$$

Thus, for this circuit (LFF)

$$\angle H(j\omega) = \theta(j\omega) = \tan^{-1} \left(\frac{\omega}{\frac{R}{L}} \right) - \tan^{-1} \left(\frac{\omega}{\frac{R}{L}} \right)$$

$$\Rightarrow \theta(j\omega) = -\tan^{-1} \left(\frac{\omega L}{R} \right)$$

—o—

P70

Monday, May 24, 2021 11:33 AM

Thus, we have the following Bode plots


$$|H(j\omega)| = \frac{R/L}{\sqrt{\omega^2 + (\frac{R}{L})^2}}$$

At $\omega = 0$

$$|H(j\omega)| = 1$$

At $\omega = \infty$

$$|H(j\omega)| = 0$$

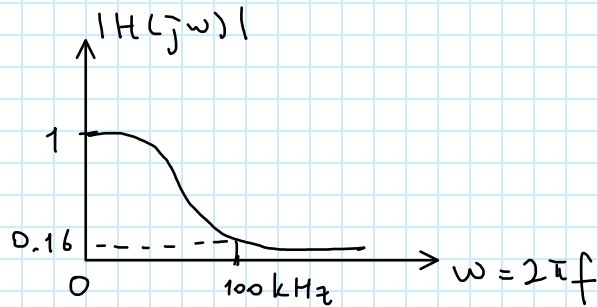



For $\theta(j\omega) = -\tan^{-1}\left(\frac{\omega L}{R}\right)$

At $\omega = 0$

$$\theta(j\omega) = 0$$

At $\omega = \infty$

$$\theta(j\omega) = -\frac{\pi}{2}$$

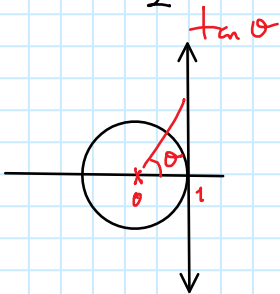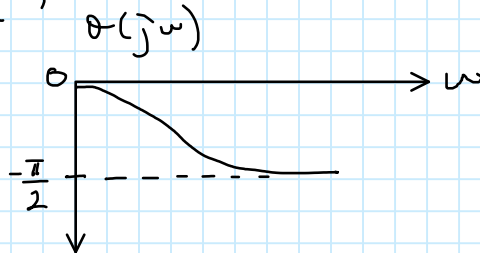

→ Half power frequency

Cut-off Frequency (Corner Frequency or -3dB frequency).

- It is defined as the frequency when $|H(j\omega)| = \frac{1}{\sqrt{2}} = 0.707$.

Ex.

Find the cut-off frequency of the series RL-LPF.

Ans!

$$|H(j\omega)| = \frac{R/L}{\sqrt{\omega_c^2 + (\frac{R}{L})^2}} = \frac{1}{\sqrt{2}}$$


Take the square of both sides,

$$\frac{R^2/L^2}{\omega_c^2 + (\frac{R}{L})^2} = \frac{1}{2} \Rightarrow 2(\frac{R}{L})^2 = \omega_c^2 + (\frac{R}{L})^2$$


$$\omega_c^2 = (\frac{R}{L})^2$$

$$\Rightarrow \omega_c = \frac{R}{L} \text{ or } f_c = \frac{1}{2\pi} \frac{R}{L} \text{ (Hz)}$$

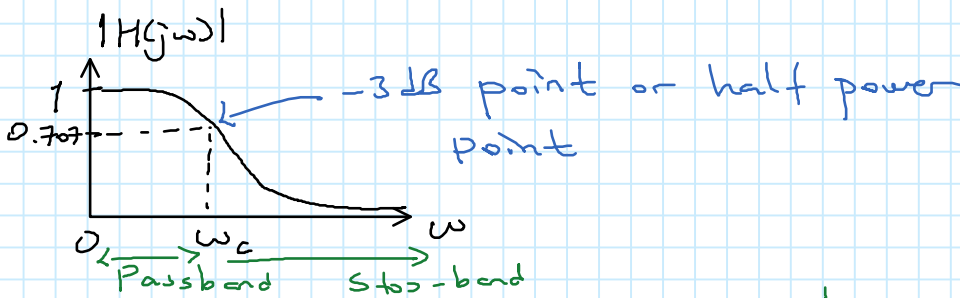- Why do we equate to $\sqrt{2}$? or why is the corner frequency is called -3dB frequency?



Ideal case.

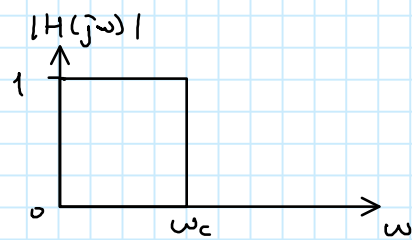

- Power at the output = $\frac{V_{out}^2}{R}$, Power at the input = $\frac{V_{in}^2}{R}$


- When $V_{in} = 1V$, $P_{in} = \frac{1}{R}$, and when $V_{out} = \frac{1}{\sqrt{2}}$, $P_{out} = \frac{1}{2R}$

$$dB = 10 \log_{10} \frac{P_{out}}{P_{in}}$$

$$dB = 10 \log_{10} (\frac{V_o}{V_{in}})^2 = 20 \log_{10} (\frac{V_o}{V_{in}})$$
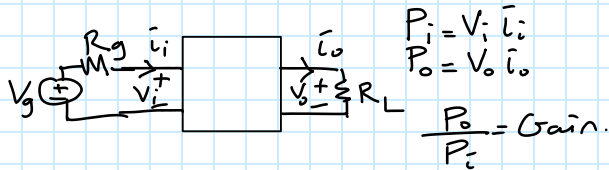
$$\Rightarrow \text{At } \omega_c, P_{out} = \frac{1}{2} P_{in}$$





Decibel (dB):

$$\text{Gain in dB} = 10 \log \frac{P_o}{P_i}$$

If the gain, $G = 100$

$$\Rightarrow G_{dB} = 10 \log_{10} 100 = 10 \log_{10} 10^2 = 20 \log_{10} 10 = 20 \text{ dB}$$

If P_i is not given, $P_i = P_{ref} = 1 \text{ W}$.

$$G_{dB} = 10 \log_{10} \frac{P_{out}}{1} = 10 \log_{10} P_{out}$$

(dBm):

$$G_{dBm} = 10 \log_{10} \frac{P_{out}}{1 \text{ mW}} = 10 \log_{10} P_o \times 10^3$$

$$= 10 \log_{10} P_o + 10 \log_{10} 10^3$$

$$\Rightarrow G_{dBm} = G_{dB} + 30$$

Ex:

Find the decibel and milli-decibel of the following power gains?

a-) $G = 1000$

b-) $G = 10^{-6}$

Ans:

a-) $G_{dB} = 10 \log_{10} 10^3 = 30 \text{ dB} \Rightarrow G_{dBm} = 60 \text{ dBm}$

b-) $G_{dB} = -60 \text{ dB} \Rightarrow G_{dBm} = -30 \text{ dBm}$


Ex:

A mobile phone has a sensitivity of $S = -120 \text{ dBm}$.

What does this imply?

Ans:

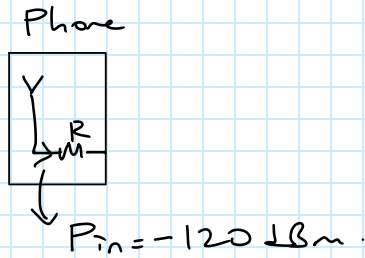Sensitivity is the received power by the phone.



The power in Watts is

$$P_{in \text{ dBm}} = P_{in \text{ dB}} + 30$$

$$P_{in \text{ dBm}} = -120 = P_{in \text{ dB}} + 30$$

$$\Rightarrow P_{in \text{ dB}} = -150$$


By definition,

$$P_{in \text{ dB}} = 10 \log_{10} \frac{P_{in}}{1}$$

$$-150 = 10 \log_{10} P_{in} \Rightarrow P_{in} = 10^{-15} \text{ W} = 0.001 \text{ pW}$$

$$-15 = \log_{10} P_{in}$$

Also,

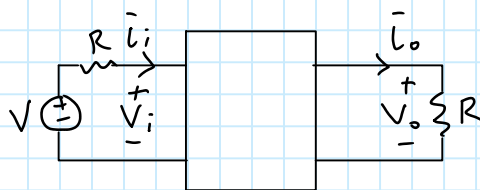


$$G = \frac{P_o}{P_i}, \quad G_{\text{dB}} = 10 \log_{10} \frac{P_o}{P_i} = 10 \log_{10} \frac{V_o^2/R}{V_i^2/R} = 10 \log_{10} \left(\frac{V_o}{V_i} \right)^2$$

$$G_{\text{dB}} = 20 \log_{10} \frac{V_o}{V_i}$$

2-) High-Pass Filter (HPF)

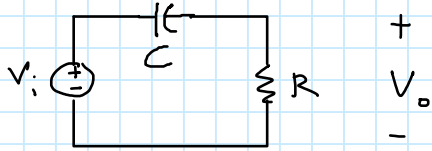- This circuit passes high frequencies, and blocks (filters out) low frequencies
- We can implement an HPF from a serial RC circuit as:



The transfer function is.

$$H(s) = \frac{R}{R + \frac{1}{sC}} = \frac{R}{\frac{1 + sRC}{sC}} = \frac{sRC}{1 + sRC}$$

$$= \frac{sRC \cdot (1/RC)}{1 + sRC \cdot (1/RC)} = \frac{s}{s + \frac{1}{RC}}$$

Replace $s = j\omega \Rightarrow H(j\omega) = \frac{j\omega + 0}{j\omega + \frac{1}{RC}}$


$$|H(j\omega)| = \frac{\omega}{\sqrt{\omega^2 + \left(\frac{1}{RC}\right)^2}}$$

$$H(j\omega) = \frac{\omega \cdot e^{j(\tan^{-1} \frac{\omega}{0})}}{\sqrt{\omega^2 + \left(\frac{1}{RC}\right)^2} \cdot e^{j(\tan^{-1} \omega RC)}} \Rightarrow \sigma(j\omega) = \tan^{-1}(\infty) - \tan^{-1}(\omega RC)$$

$$\sigma(j\omega) = 90^\circ - \tan^{-1}(\omega RC)$$


Bode Plots:

$$|H(j\omega)| = \frac{\omega}{\sqrt{\omega^2 + (\frac{1}{RC})^2}}$$


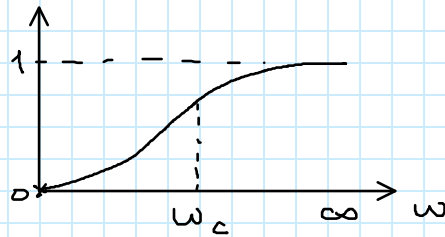


where $\omega_c = \frac{1}{RC}$ and $f_c = \frac{1}{2\pi RC}$
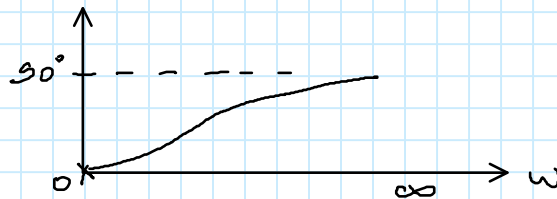
$$\phi(j\omega) = 90^\circ - \tan^{-1}\left(\frac{1}{\omega RC}\right)$$




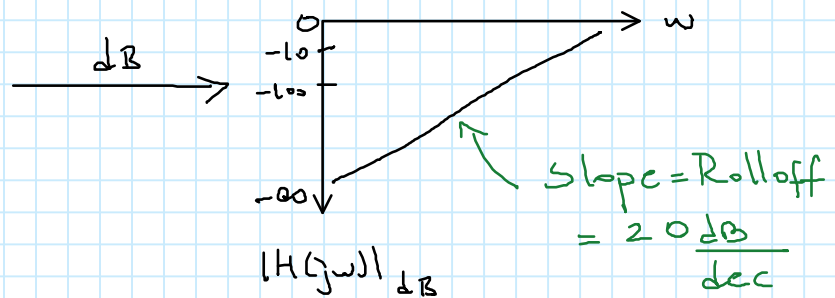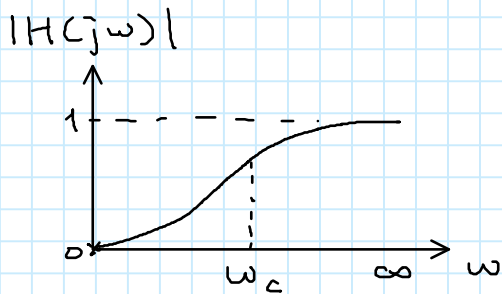- When drawing Bode plots, the axes are taken as decibels.





dec = decade = 10

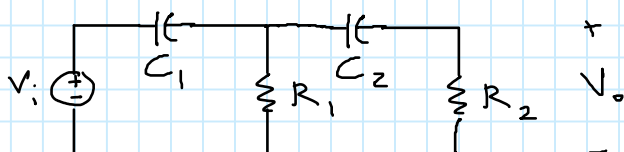- Roll-off is an indicator of filter selectivity
- With every degree of a filter roll-off increases by $20 \frac{dB}{dec}$




Roll-off = $\frac{40 dB}{dec}$

3-) Band-pass Filter (BPF)

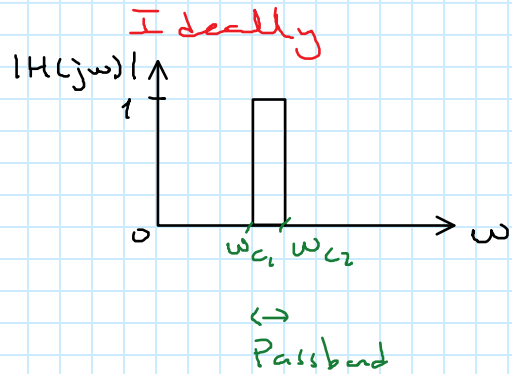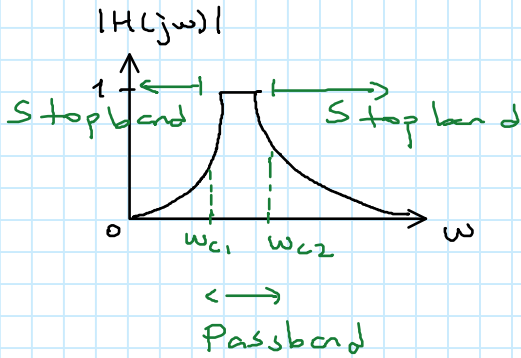

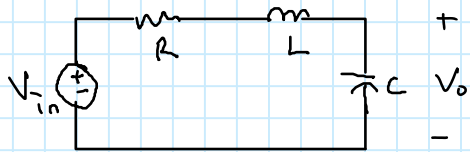- Implementation can be done by using LPF and HPF in series.
 or using an RLC circuit
 For a series RLC circuit:



$$H(s) = \frac{\left(\frac{R}{C}\right)s}{s^2 + \left(\frac{R}{L}\right)s + \left(\frac{1}{LC}\right)}$$

$$|H(jw)| = \frac{w(R/C)}{\left[\left(\frac{1}{LC} - w^2\right)^2 + \left[w\left(\frac{R}{L}\right)\right]^2\right]^{1/2}}$$

$$\theta(jw) = 90^\circ - \tan^{-1} \left(\frac{w(R/L)}{\left(\frac{1}{LC} - w^2\right)} \right)$$

HW#10

1-) In Proteus, generate 3 voltage signals at 3 frequencies and sum them.

$f_1 =$ Sine wave at $f = 1 \text{ kHz}$.

$f_2 =$ " " at $f = 5 \text{ kHz}$

$f_3 =$ " " " $f = 15 \text{ kHz}$.

Amplitudes are 1V.

a-) Use a LPF to pass f_1 only. Show $|H(jw)|$.


b-) Use a HPF to " f_3 only. Show $|H(jw)|$.

c-) Use a BPF to pass f_2 only. " " "

Use the filters with # of poles = 3, 5, 10.


- Electrical Energy Distribution -

ELEKTRİĞİN TAŞINMASI

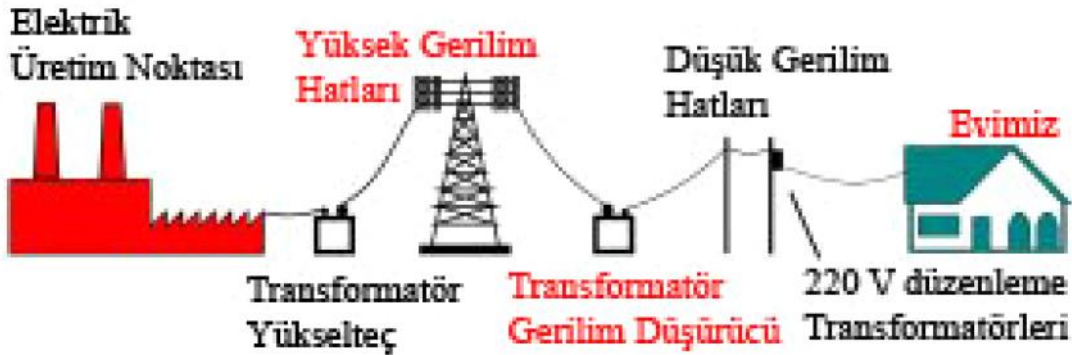

Consumer


Consumer:

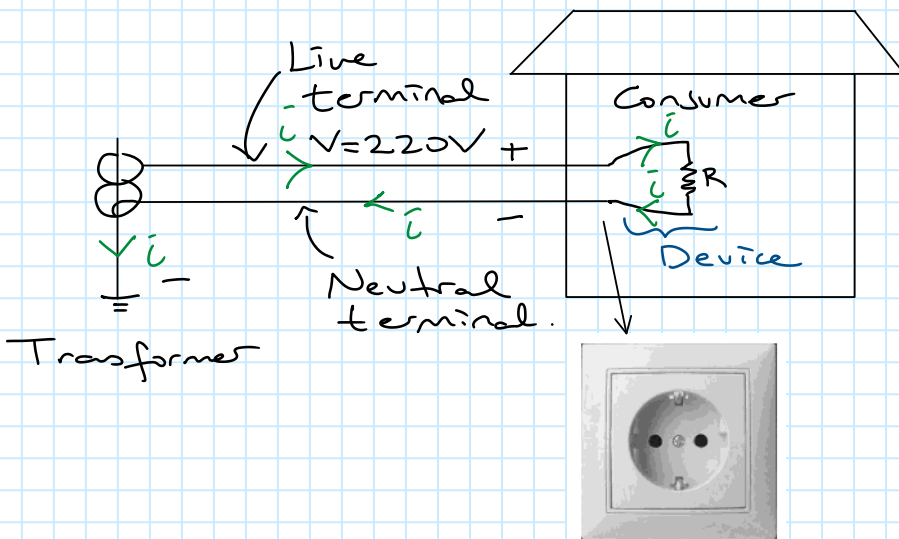

Live terminal = Phase terminal


Electric Shock:

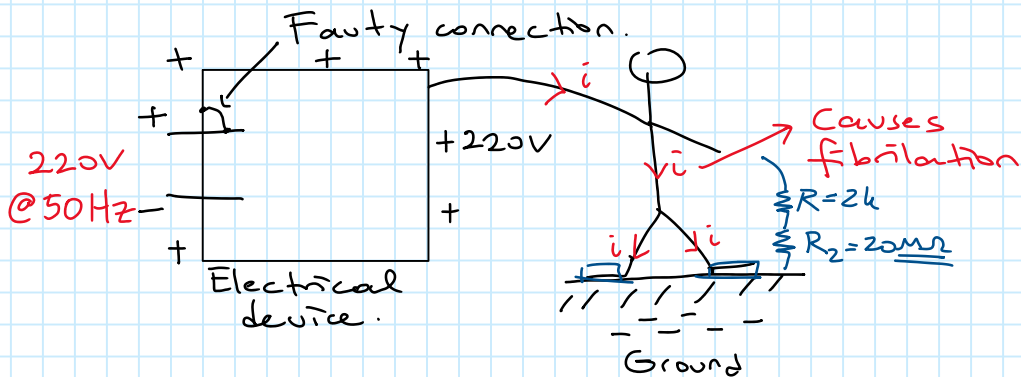Current passing through human body. It usually occurs as follows:




Fibrillation: The heart stops beating.
 $I_{amp} \geq 30mA$ always poses the risk of fibrillation.

- Risk of Fibrillation -

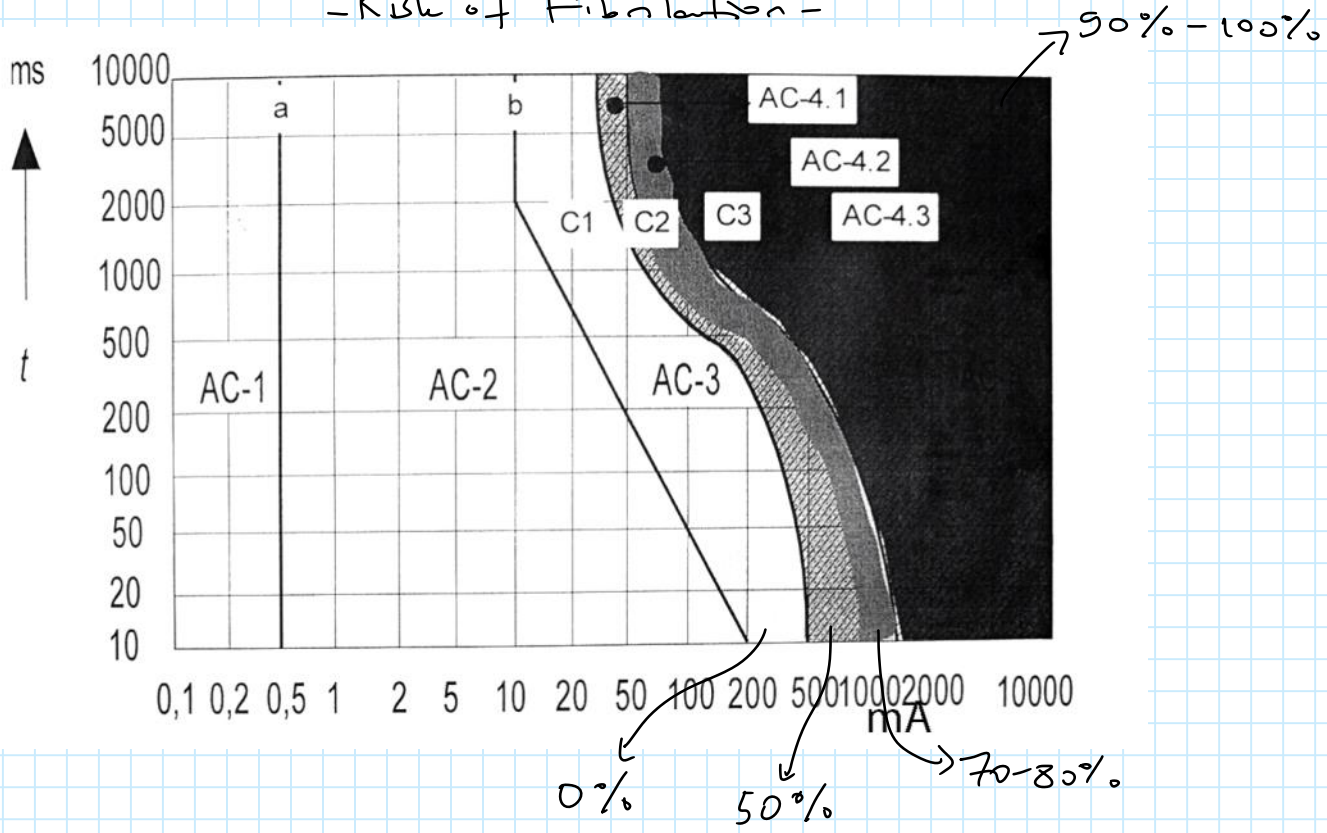

$R_{human} \approx 2k\Omega$, If $V = 220V$
 $\Rightarrow \bar{i} = \frac{V}{R} = \frac{220V}{2200} = 0.1 = 100mA$

Vücutun direnci

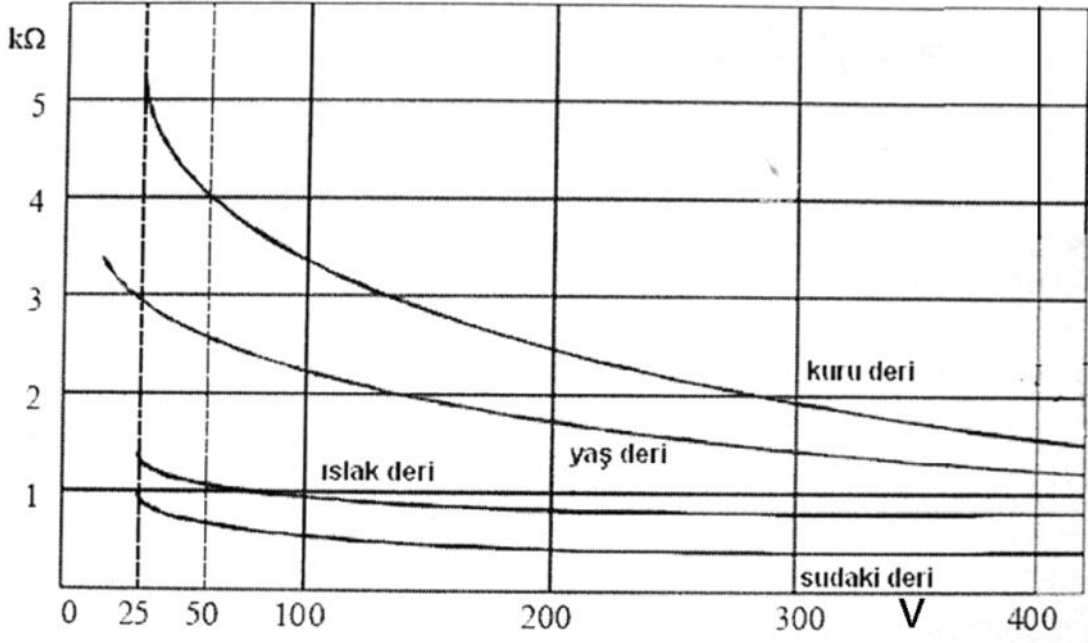




Precautions:

- 1-) Cutting-off the voltage source.
- 2-) Isolation
- 3-) Grounding:


Fuses: Switch



Fuses.

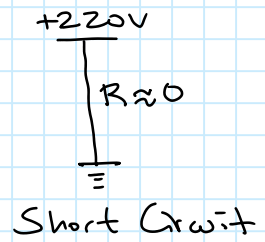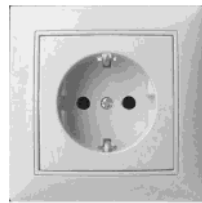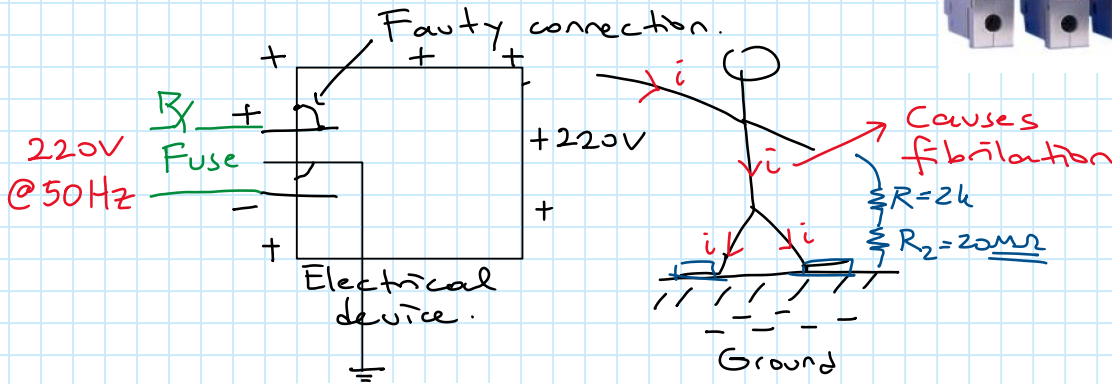


Direct Contact Scenario:

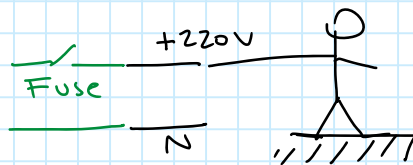

Leakage Current Fuses:

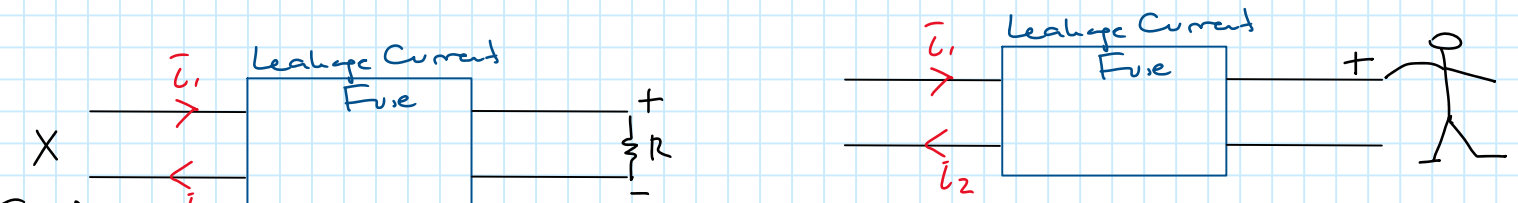The Major difference of Leakage current fuses for the standard fuses is that they protect from a direct contact electric shock as well.



If $i_1 - i_2 \geq 25\text{mA}$ (or 30mA)
It blows.


Final Exam:

1-) Online.

2-) Calculator is allowed. Phone and computer use is not allowed.

3-) From the notes you may study the examples on P66 and

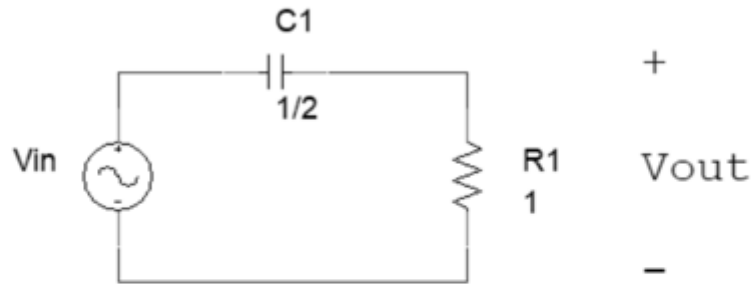Given the following circuit (zero initial conditions)



Answer questions 1-5.

1-) What type of filter is this circuit ?

a-) LPF

b-) HPF

c-) BPF

d-) BRF

2-) Find its transfer function ?

a-) $H(s) = \frac{s}{s+2}$

b-) $H(s) = \frac{1}{s+2}$

c-) $H(s) = \frac{2}{1+s}$

d-) $H(s) = \frac{1}{1+s/2}$

3-) Find the angle of the transfer function ?

a-) $\theta = -\tan^{-1} \omega/2$

b-) $\theta = -\tan^{-1} 2\omega$

c-) $\theta = \tan^{-1} \frac{\omega}{2} - \tan^{-1} \omega/2$

d-) $\theta = -\tan^{-1} \omega - \tan^{-1} 2\omega$

4-) Find the cut-off frequency ω_c (rad/sec) ?

a-) 0

b-) 1

c-) 2

d-) 1/2

5-) Find $|H(j\omega)|$ at $\omega = 2$ rad/sec ?

a-) $\sqrt{2}$

b-) $2\sqrt{2}$


c-) 1/2

d-) $1/\sqrt{2}$

Note: This example is in test format. Your question will be in Text format.

- Final Exam Preparation -

1-)

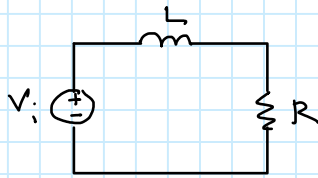


- + Find $H(s) = ?$
- Find the type of the filter
- Find $|H(j\omega)| = ?$
- Find $\angle H(j\omega) = ?$
- Find the corner freq?

Ans:

Step 1: Find the transfer function.

$$H(s) = \frac{V_o(s)}{V_i(s)}$$

In s-domain

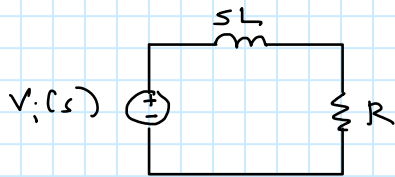

$$\Rightarrow H(s) = \frac{V_o(s)}{V_i(s)}$$

$$\Rightarrow V_o(s) = V_i(s) \cdot \frac{R}{R + sL}$$

$$\Rightarrow H(s) = \frac{R}{sL + R} \left(\frac{1}{L} \right) = \frac{R/L}{s + R/L} \leftarrow \text{Proper form.}$$

Step 2: Replace $s = j\omega$ and obtain the $H(j\omega)$

$$H(j\omega) = \frac{R/L}{R/L + j\omega}$$

Step 3: Obtain polar form for $H(j\omega)$

$$H(j\omega) = \frac{R/L e^{j0}}{\sqrt{\omega^2 + \left(\frac{R}{L}\right)^2} e^{j \tan^{-1} \frac{\omega}{R/L}}}$$

Step 4:

Obtain $|H(j\omega)|$ and $\angle H(j\omega)$


$$|H(j\omega)| = \frac{R/L}{\sqrt{\omega^2 + \left(\frac{R}{L}\right)^2}}, \quad \angle H(j\omega) = \left(0 - \tan^{-1} \frac{\omega L}{R} \right)$$

Type of the filter:

$$|H(j\omega)| = \frac{R/L}{\sqrt{\omega^2 + \left(\frac{R}{L}\right)^2}}$$

Put $\omega = 2\pi f = 0$, $|H(j\omega)| = 1$

Put $\omega = \infty$, $|H(j\omega)| = 0$

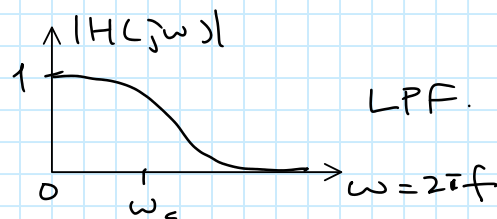


Corner Frequency:


$$|H(j\omega)| = \frac{R/L}{\sqrt{\omega^2 + \left(\frac{R}{L}\right)^2}} = \frac{1}{\sqrt{2}}$$

$$\frac{R^2/L^2}{\omega_c^2 + \frac{R^2}{L^2}} = \frac{1}{2}$$

$$2 \frac{R^2}{L^2} = \omega_c^2 + \frac{R^2}{L^2}$$

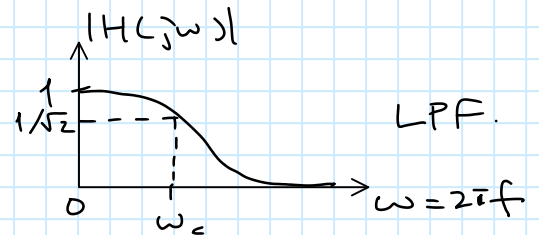
$$\Rightarrow \omega_c = \frac{R}{L} \Rightarrow f_c = \frac{1}{2\pi} \frac{R}{L} \text{ (Hz)}$$



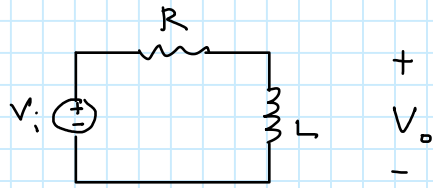

Solve this filter.

Ans:

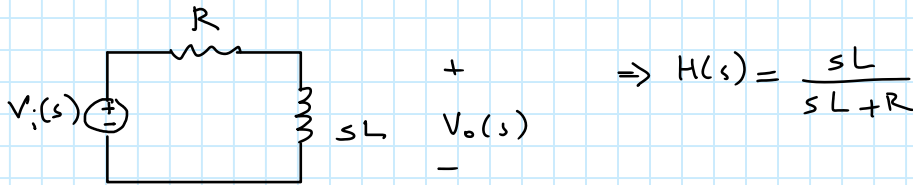

Proper form: $H(s) = \frac{sL}{sL + R} \left(\frac{1}{L}\right) = \frac{s}{s + R/L}$

$$H(j\omega) = \frac{0 + j\omega}{j\omega + R/L}$$

or

$$H(j\omega) = \frac{\omega e^{j\tan^{-1}\infty}}{\sqrt{\omega^2 + \left(\frac{R}{L}\right)^2} e^{j\tan^{-1}\frac{\omega}{R/L}}}$$

$|H(j\omega)|$

Then,

$$|H(j\omega)| = \frac{\omega}{\sqrt{\omega^2 + \left(\frac{R}{L}\right)^2}}, \quad \angle H(j\omega) = \tan^{-1}\infty - \tan^{-1}\frac{\omega L}{R}$$


$$= \frac{\pi}{2} - \tan^{-1}\frac{\omega L}{R}$$

Type of the filter:

$$|H(j\omega)| = \frac{\omega}{\sqrt{\omega^2 + \left(\frac{R}{L}\right)^2}}$$

Put $\omega = 0$, $|H(j\omega)| = 0$

Put $\omega = \infty$, $|H(j\omega)| = 1$

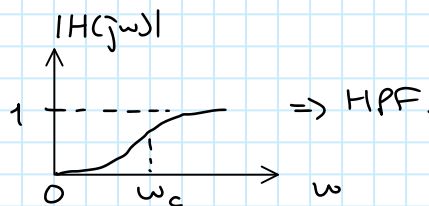


Corner Frequency:

$$|H(j\omega)| = \frac{\omega}{\sqrt{\omega^2 + \left(\frac{R}{L}\right)^2}} = \frac{1}{\sqrt{2}}$$

$$\frac{\omega_c^2}{\omega_c^2 + \left(\frac{R}{L}\right)^2} = \frac{1}{2} \Rightarrow \cancel{\omega_c^2} = \cancel{\omega_c^2} + \left(\frac{R}{L}\right)^2$$

$$\Rightarrow \omega_c = \frac{R}{L}, \quad f_c = \frac{1}{2\pi} \frac{R}{L}$$


3-)

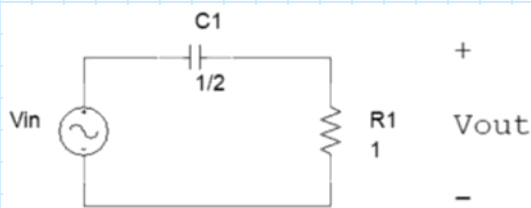

Analyze this filter.

Ans:

In s-domain

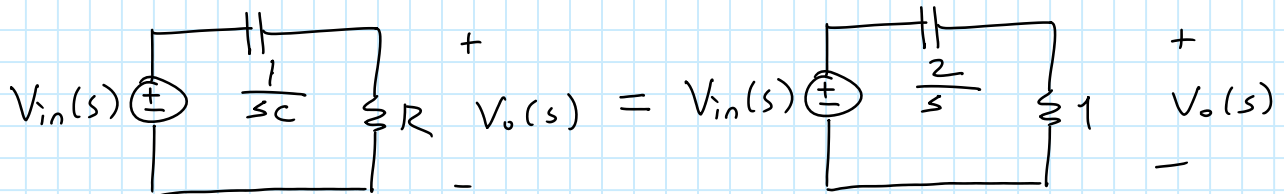

$$\Rightarrow H(s) = \frac{V_o(s)}{V_{in}(s)} = \frac{1}{1 + \frac{2}{s}} = \frac{1}{\frac{s+2}{s}} = \frac{s}{s+2}$$

Then,

$$H(j\omega) = \frac{j\omega}{j\omega + 2}$$

In polar form,

$$H(j\omega) = \frac{\omega e^{j\frac{\pi}{2}}}{\sqrt{\omega^2 + 2^2} e^{j\arctan \frac{\omega}{2}}}$$

Then,

$$|H(j\omega)| = \frac{\omega}{\sqrt{\omega^2 + 4}}, \quad \angle H(j\omega) = \frac{\pi}{2} - \arctan \frac{\omega}{2}$$

The cut-off freq:

$$|H(j\omega)| = \frac{\omega}{\sqrt{\omega^2 + 4}} = \frac{1}{\sqrt{2}}$$

$$\frac{\omega_c^2}{\omega_c^2 + 4} = \frac{1}{2} \Rightarrow 2\omega_c^2 = \omega_c^2 + 4$$


$$\omega_c^2 = 4$$

$$\omega_c = 2 \text{ rad/s.}$$

4-

Ex:

Given the circuit

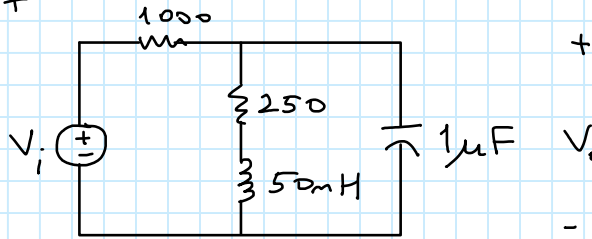


$V_g = 50t u(t)$

Find $H(s)$.

Find $V_o(t)$ using

$H(s)$.

Ans:

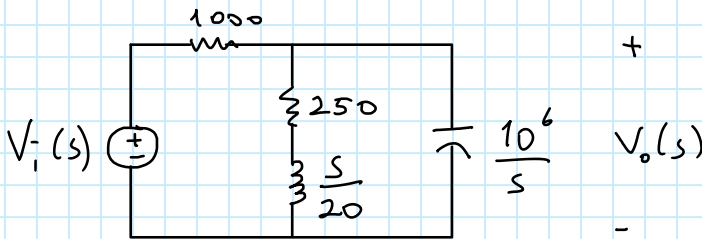

$$\left(\frac{10^6}{s}\right) \parallel \left(250 + \frac{s}{20}\right) = \frac{10^6}{s} \times \frac{5000+s}{20} = \frac{5 \times 10^9 + 10^6 s}{20s}$$

$$= \frac{10^6}{s} + \frac{5000+s}{20} = \frac{20 \times 10^6 + s^2 + 5000s}{20s}$$

$$= \frac{10^6 s + 5 \times 10^9}{s^2 + 5000s + 2 \times 10^7}$$

$$H(s) = \frac{10^6 s + 5 \times 10^9}{s^2 + 5000s + 2 \times 10^7} = \frac{10^6 s + 5 \times 10^9}{s^2 + 5000s + 2 \times 10^7} \times \frac{1000}{1000}$$

$$= \frac{10^6 s + 5 \times 10^9}{s^2 + 5000s + 2 \times 10^7} + 1000 = \frac{10^6/s + 5 \times 10^9 + 1000s^2 + 5 \times 10^6 s + 2 \times 10^{10}}{s^2 + 5000s + 2 \times 10^7}$$


$$\frac{10^6 s + 5 \times 10^9}{1000s^2 + 6 \times 10^6 s + 25 \times 10^9} \left(\frac{1}{1000}\right)$$

$$= \frac{10^3 s + 5 \times 10^6}{s^2 + 6000s + 25 \times 10^6} = \frac{1000(s + 5000)}{s^2 + 6000s + 25 \times 10^6}$$


P86

Monday, June 5, 2023 9:54 AM

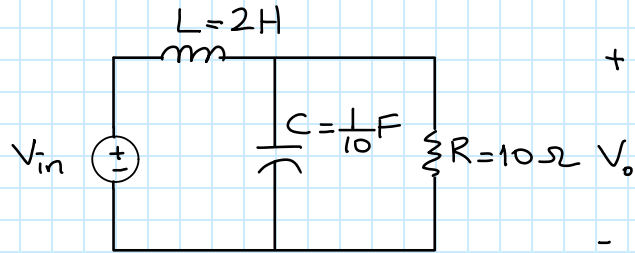1. Find the transfer function $H(s)$ for the following circuit.




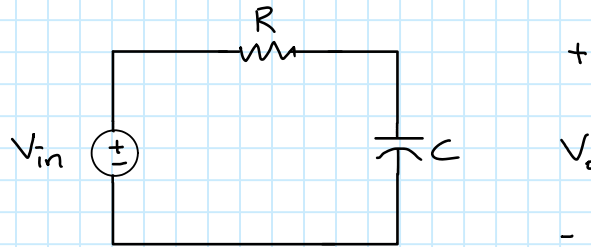2. For the filter circuit shown below, find
 - a. the expression for the transfer function, $H(j\omega)$.
 - b. the type of this filter.
 - c. the expression for the cut-off frequency (corner frequency).
 - d. the phase expression of the transfer function.




Answers:

1-) In s -domain,

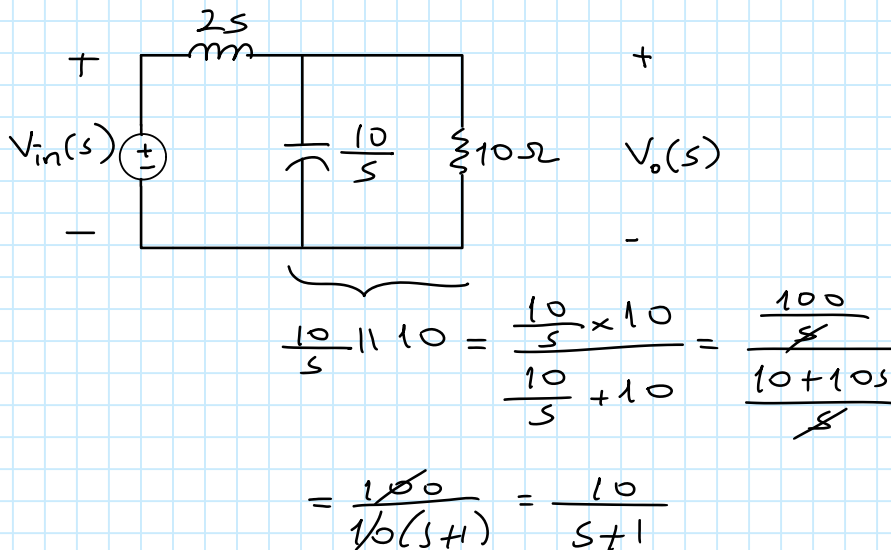

$$\Rightarrow H(s) = \frac{\frac{10}{s+1}}{2s + \frac{10}{s+1}} = \frac{\frac{10}{s+1}}{\frac{2s^2 + 2s + 10}{s+1}} = \frac{10}{2s^2 + 2s + 10} = \frac{5}{s^2 + s + 5}$$

2-) In s -domain,

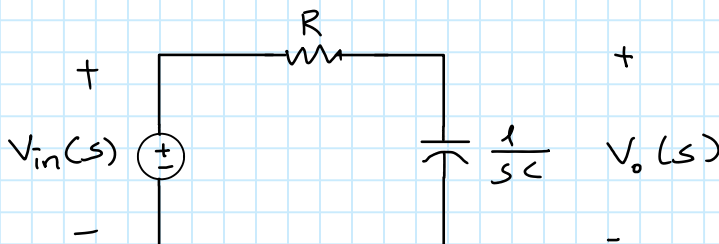

$$\Rightarrow H(s) = \frac{\frac{1}{sC}}{\frac{1}{sC} + R} = \frac{\frac{1}{sC}}{\frac{1 + sRC}{sC}} = \frac{1}{1 + sRC} = \frac{1/RC}{s + 1/RC}$$

Then

$$H(j\omega) = \frac{1/RC}{j\omega + 1/RC}$$

In polar form,

$$H(j\omega) = \frac{1/RC}{\sqrt{\omega^2 + \left(\frac{1}{RC}\right)^2}} e^{-\tan^{-1} \frac{\omega}{1/RC}}$$

Then,

$$|H(j\omega)| = \frac{1/RC}{\sqrt{\omega^2 + \left(\frac{1}{RC}\right)^2}}$$

$$\angle H(j\omega) = -\tan^{-1} \omega RC.$$

The corner frequency:

$$\frac{1/RC}{\sqrt{\omega^2 + \left(\frac{1}{RC}\right)^2}} = \frac{1}{\sqrt{2}}$$

$$\frac{\left(\frac{1}{RC}\right)^2}{\omega_c^2 + \left(\frac{1}{RC}\right)^2} = \frac{1}{2} \Rightarrow \cancel{\left(\frac{1}{RC}\right)^2} = \omega_c^2 + \cancel{\left(\frac{1}{RC}\right)^2}$$

$$\omega_c^2 = \left(\frac{1}{RC}\right)^2$$

$$\omega_c = \frac{1}{RC} \Rightarrow f_c = \frac{1}{2\pi RC} \text{ Hz}$$